



UNM LEARN



David Kirby

3

[Course Home](#) [Module 3](#) **Take Test: Quiz 3.3**

## Take Test: Quiz 3.3

### Test Information

Description

Instructions

Multiple Attempts This test allows multiple attempts.

Force Completion This test can be saved and resumed later.

### QUESTION 1

1 points

Saved

For the RLC series circuit with applied voltage  $v(t)$ , which of the following

best describes why  $\begin{bmatrix} v_c(t) \\ v(t) \end{bmatrix}$  cannot be a state vector?

- ☐ The applied voltage  $v(t)$  is an output.
- ☐ The applied voltage  $v(t)$  provides the same information as  $v_c(t)$ .
- ☒ The applied voltage  $v(t)$  is an input.
- ☐ Three elements, not two, are needed to fully specify the state.

### QUESTION 2

1 points

Saved

The state equation for the RLC series circuit was derived from which of the following (more than one may be correct)?

- ☐ The differential equations that arose from Newton's law.
- ☐ The circuit equation that arose from Kirchoff's current law.
- ☐ The definition of the voltage drop across the resistor.
- ☒ The circuit equation that arose from Kirchoff's voltage law.

### QUESTION 3

1 points

Saved

The output equation from the RLC series circuit was derived from which of the following (more than one may be correct)?

- ☐ The circuit equation that arose from Kirchhoff's voltage law.
- ☐ The definition of the output as the voltage across the inductor.
- ☐ The output equation always employs  $C = \begin{bmatrix} 1 & 0 \end{bmatrix}$ .
- ☒ The definition of the output as the voltage across the capacitor.

### QUESTION 4

1 points

Saved

Is it possible to have an output equation  $y(t) = v_c(t) + 3$ ?

🚩 Question Completion Status:



- ☐ the equation is a linear combination of the state and the input.
- ☒ No, because only the state and the input can appear on the right-hand side of the output equation.
- ☐ No, because  $v_c(t)$  is not an element of the state.

*Click Save and Submit to save and submit. Click Save All Answers to save all answers.*

Save All Answers

Save and Submit

