

ECE 322L

Electronics 2

02/20/20- Lecture 9



Amplifiers with active loads

Multi-stage amplifiers

Updates and overview

- Homework 4 is online
- Lab 5: practice lab for your design-project
- Single-stage IC MOSFET amplifiers-Amplifiers with active loads (Neamen 4.7.4)
Multi-stage MOSFET amplifiers (Neamen 4.8.1).

NMOS amplifier with enhancement load

  



Q-point

$$A_{vo} = \frac{-g_{m1}}{g_{m2}} = \frac{2\sqrt{K_1}\sqrt{I_D}}{2\sqrt{K_2}\sqrt{I_D}} = \sqrt{\frac{K_1}{K_2}} = \frac{\sqrt{(W/L)_1}}{\sqrt{(W/L)_2}}$$

Gain

Possible issues with this configuration??

NMOS amplifier with enhancement load

  


Q-point

$$A_{vo} = \frac{-g_{m1}}{g_{m2}} = \frac{2\sqrt{K_1}\sqrt{I_D}}{2\sqrt{K_2}\sqrt{I_D}} = \sqrt{\frac{K_1}{K_2}} = \frac{\sqrt{(W/L)_1}}{\sqrt{(W/L)_2}}$$



Gain

- Q-point is not stable against temperature and variation of transistor parameters
- Gain is limited as it is not practical to make transistors very different in size on the same chip


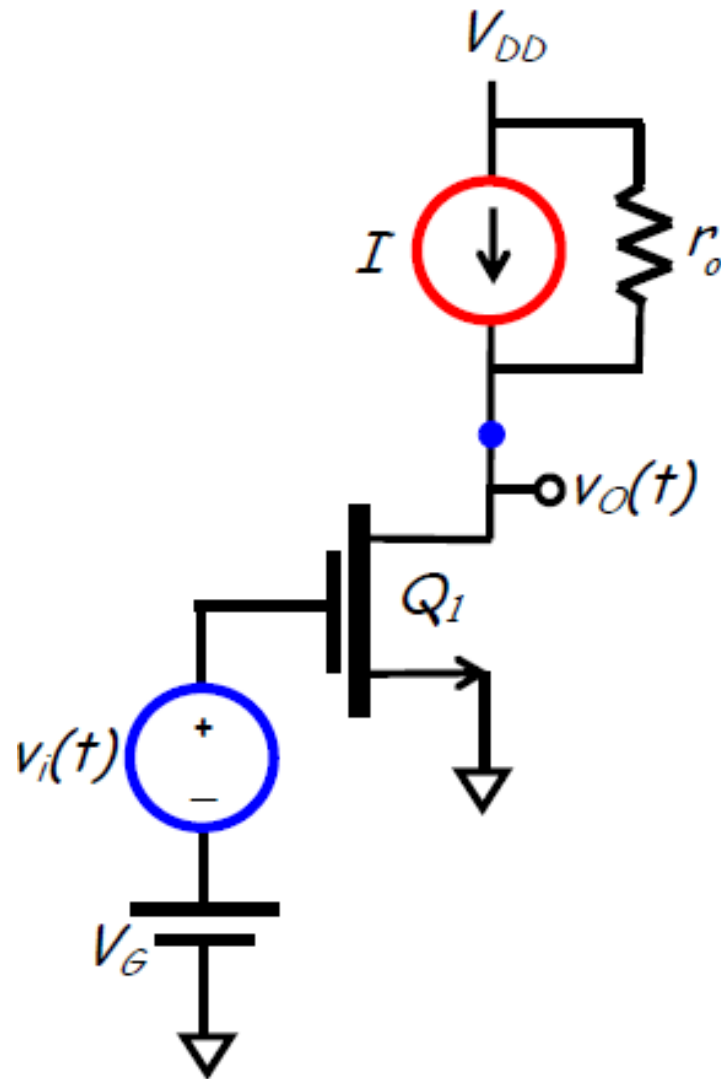
NMOS amplifier using a real current source as load



Current source: IC Implementation

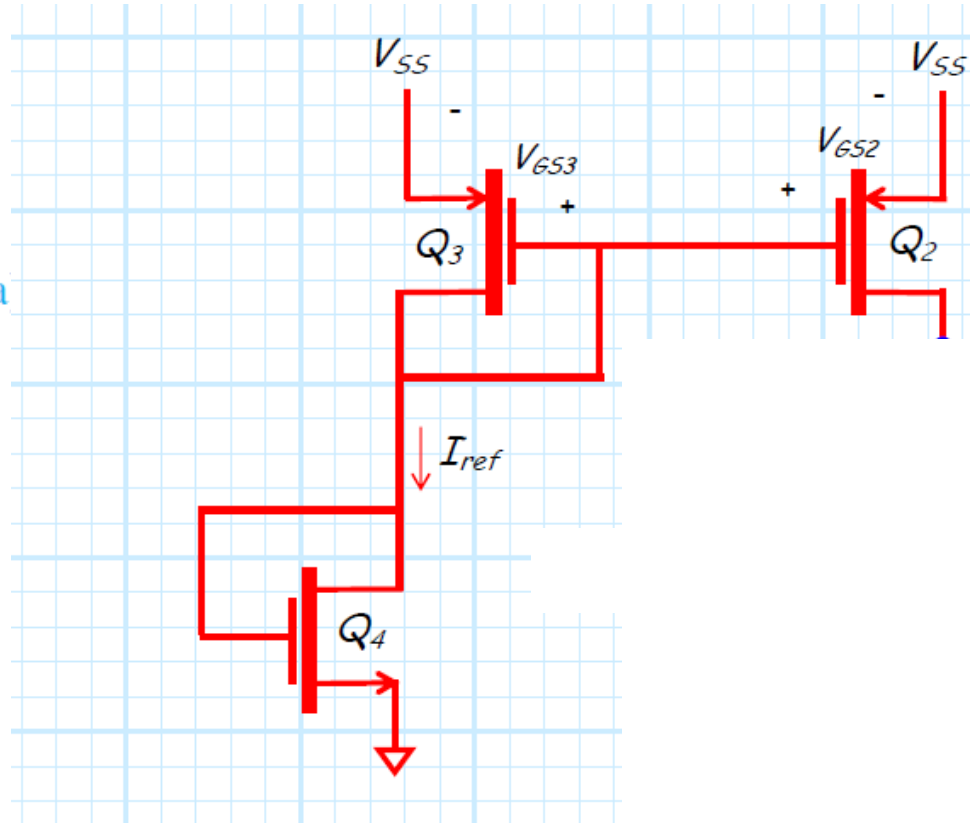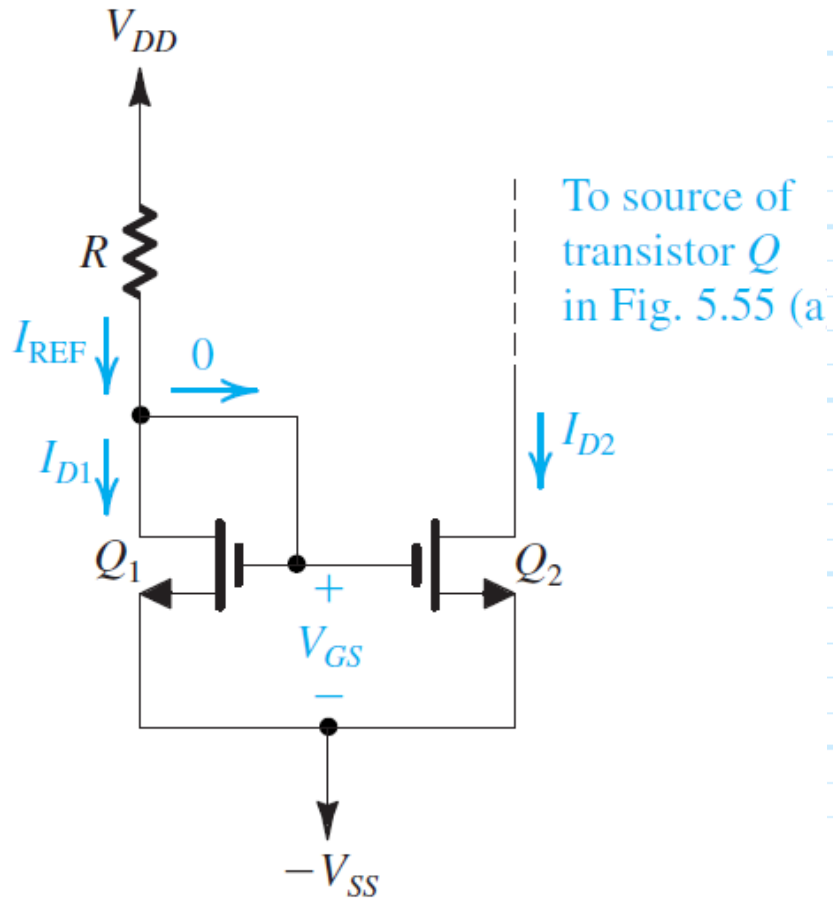

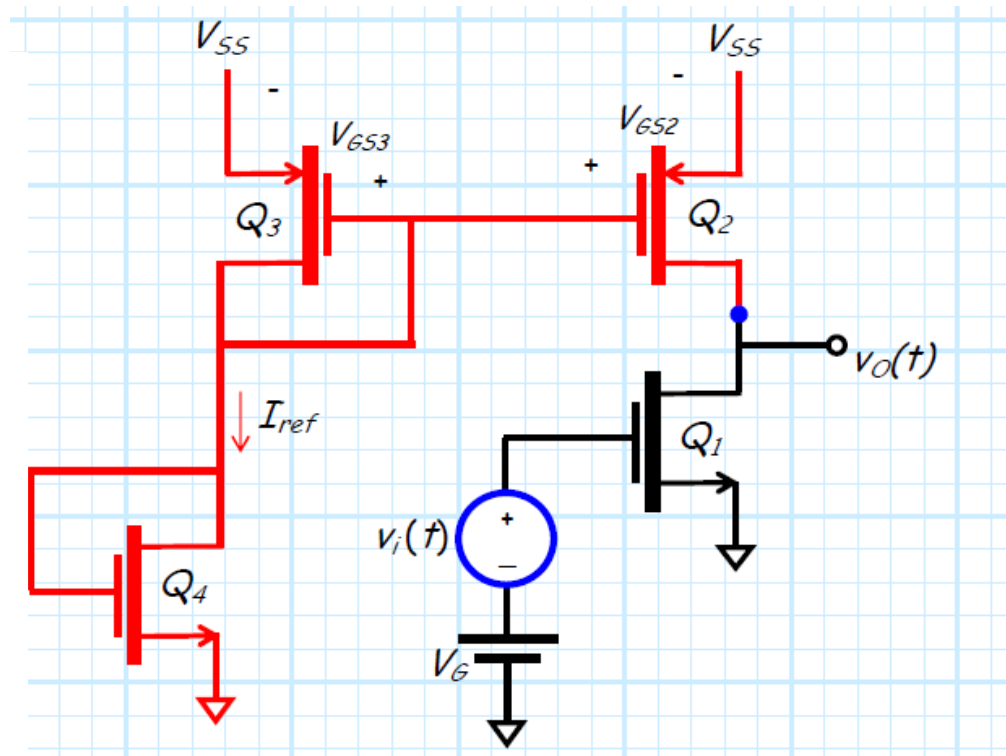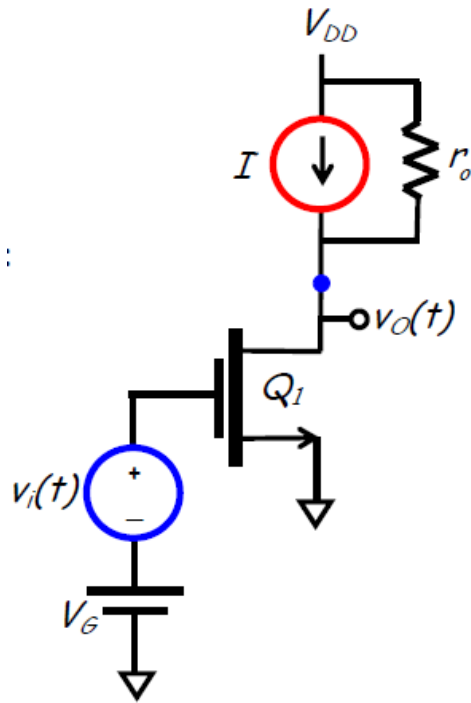
CMOS amplifier using a current source as load



- In ICs the current source is implemented by a current mirror
- r_o is then the output resistance of the current mirror as seen by Q_1

CMOS amplifier using a current source as load


DC circuit

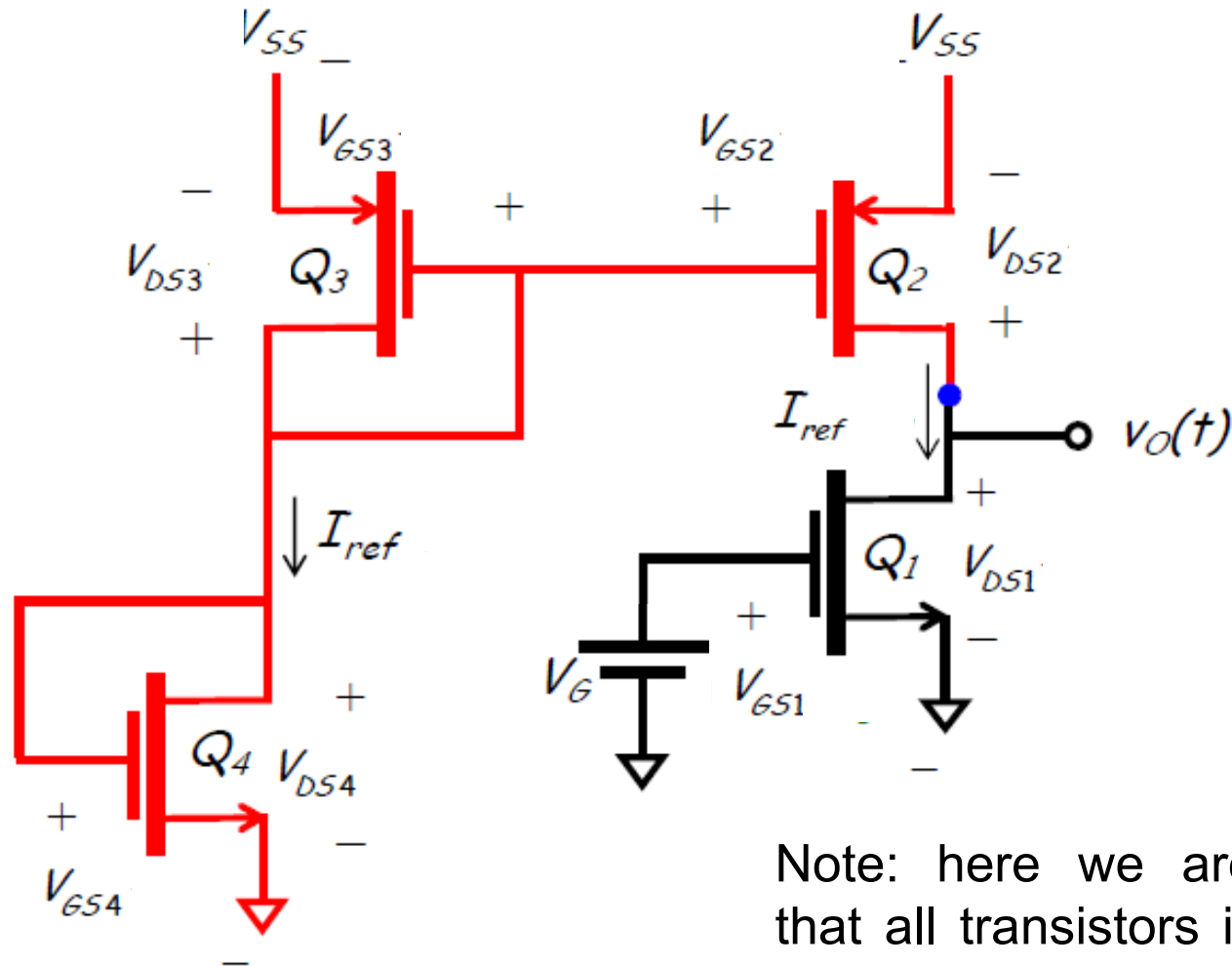


Note: here we are assuming that all transistors in the circuit are identical.

CMOS amplifier using a current source as load


AC circuit

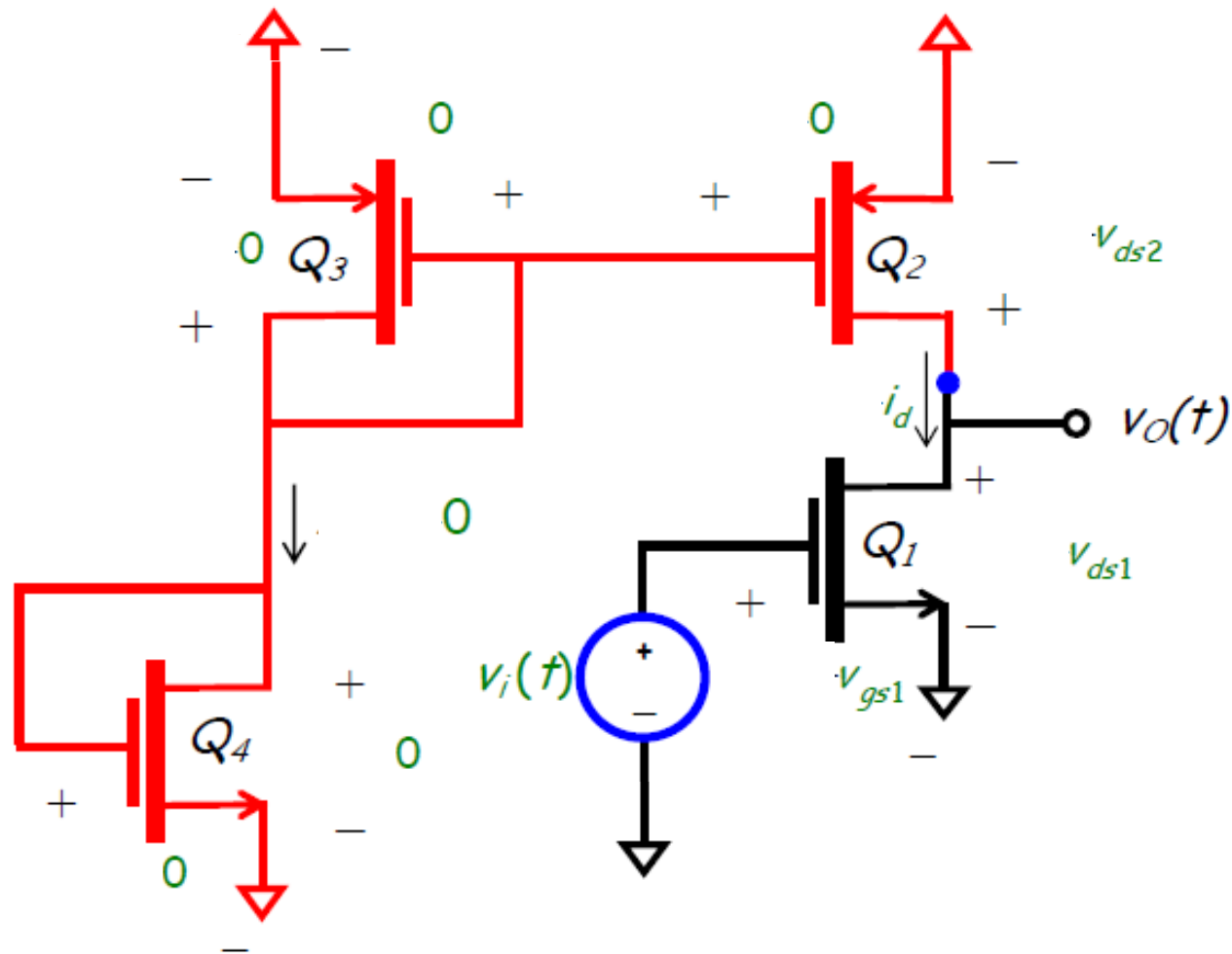


Small-signal Model of the Current Mirror

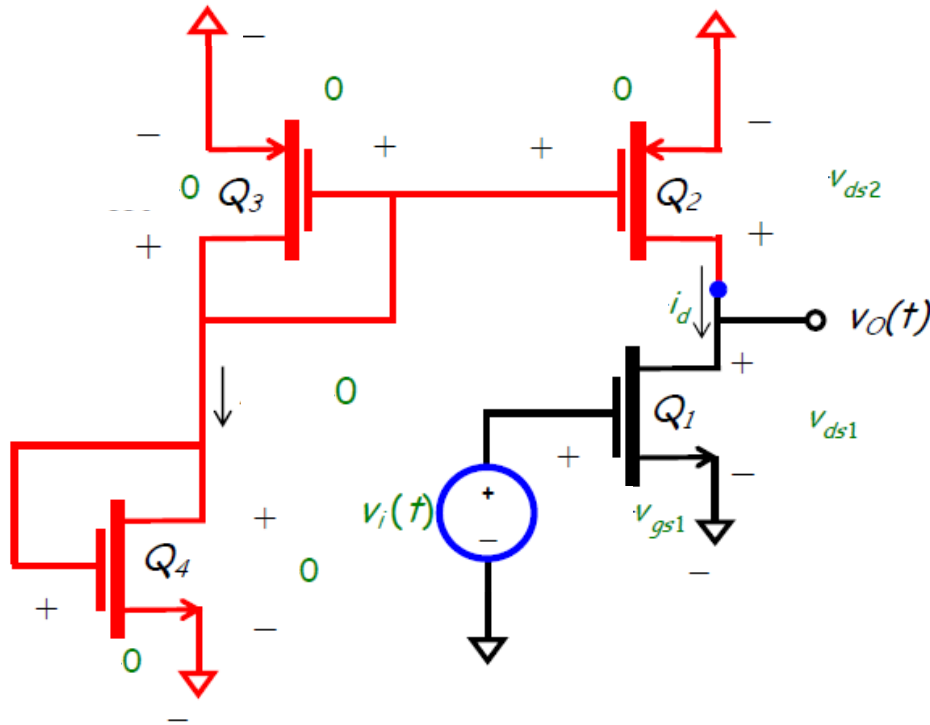

 
Equivalently, the small-signal PMOS model is:



 Thus for $v_{gs2}=0$, the small-signal model becomes:




Or, simplifying further:

 


CMOS amplifier using a current source as load



And so **this** circuit:

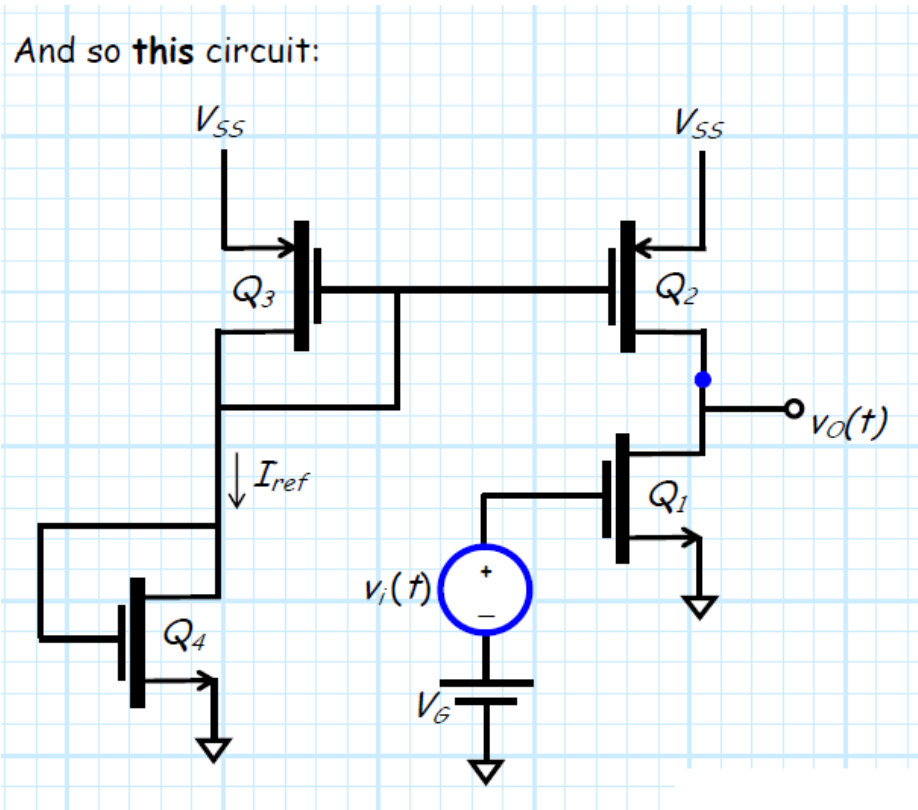

is equivalent to **this** circuit:

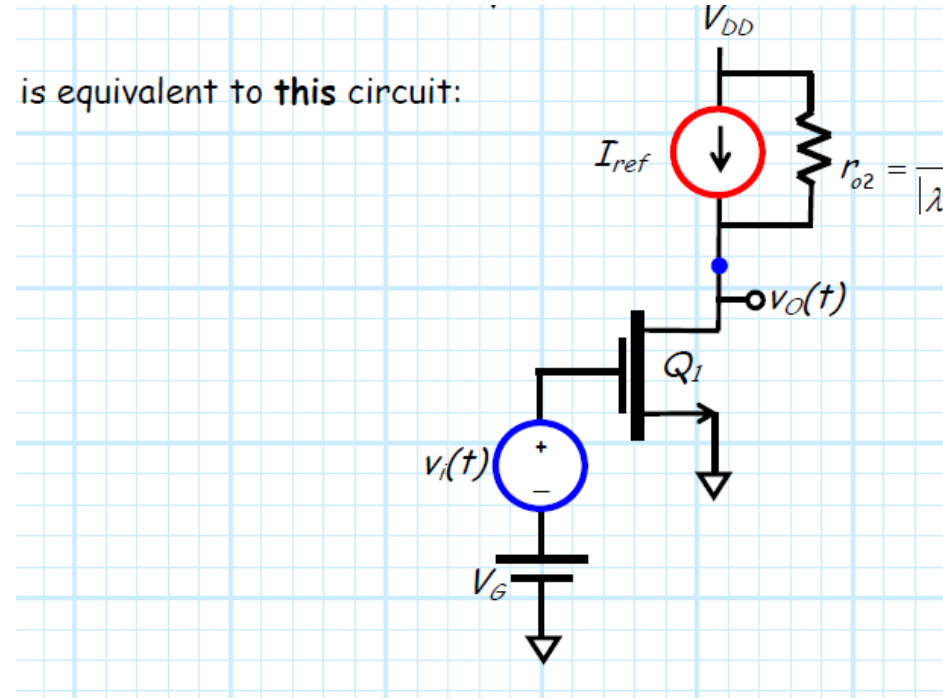

  CMOS amplifier using a current source as load



$$R_i = \infty$$

$$R_o = r_{o1} \parallel r_{o2}$$

$$A_o = -g_{m1}(r_{o1} \parallel r_{o2})$$


Note **this** result is **far different** (i.e., larger) than the result when using the **enhancement load** for R_D :

$$A_{vo} = -\sqrt{\frac{K_1}{K_2}}$$

However, we find that the **output** and **input** resistances of this amplifier are the **same** as with the enhancement load:


MOS Amplifiers Using a current source as load

Common source

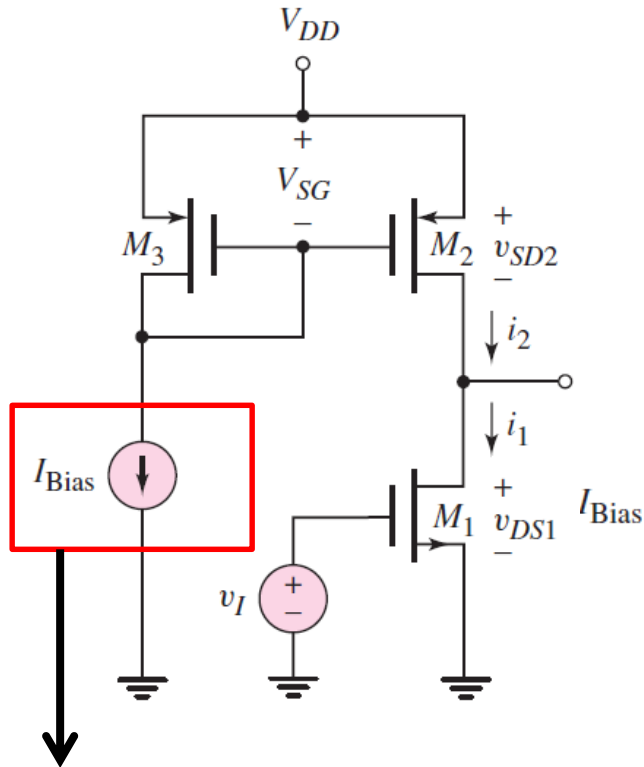


It can be any FET based network which fixes a current

Common gate

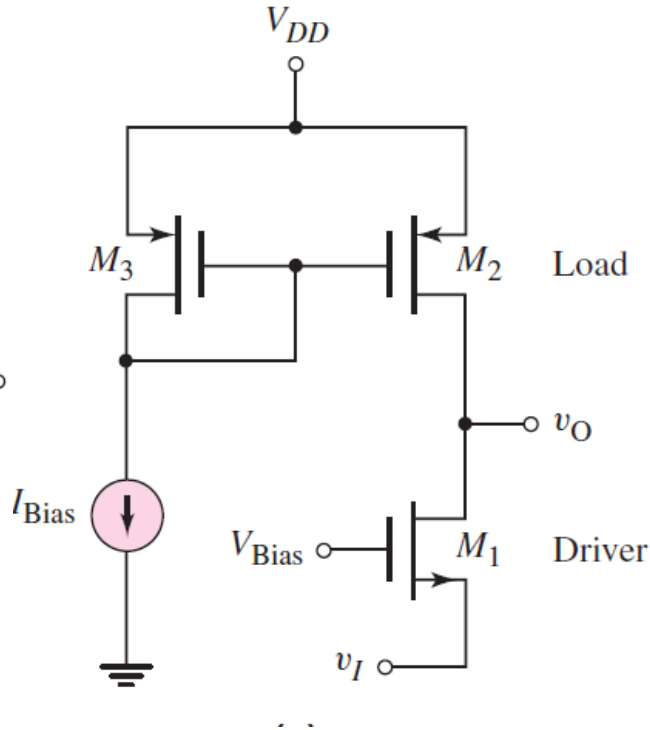


Common drain

 

Multi-stage amplifiers


Why do we need them?

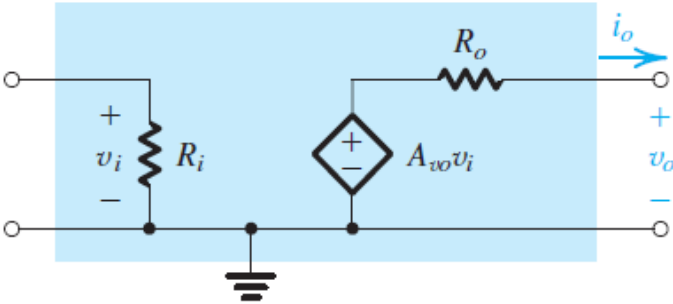Type	Circuit Model	Gain Parameter	Ideal Characteristics
Voltage Amplifier		Open-Circuit Voltage Gain $A_{vo} \equiv \left. \frac{v_o}{v_i} \right _{i_o=0} \quad (\text{V/V})$	$R_i = \infty$ $R_o = 0$
<u>Common Source</u>	<u>Common Gate</u>	<u>Source Follower</u>	
<ul style="list-style-type: none">• Large $A_v < 0$• Infinite R_{in}• Moderate R_o	<ul style="list-style-type: none">• Large $A_v > 0$• Small R_{in}• Moderate R_o	<ul style="list-style-type: none">• $0 < A_v \leq 1$• Infinite R_{in}• Small R_o	


All the amplifiers that we know of have at least one attractive feature but also at least one sub-optimal feature

Multi-stage amplifiers

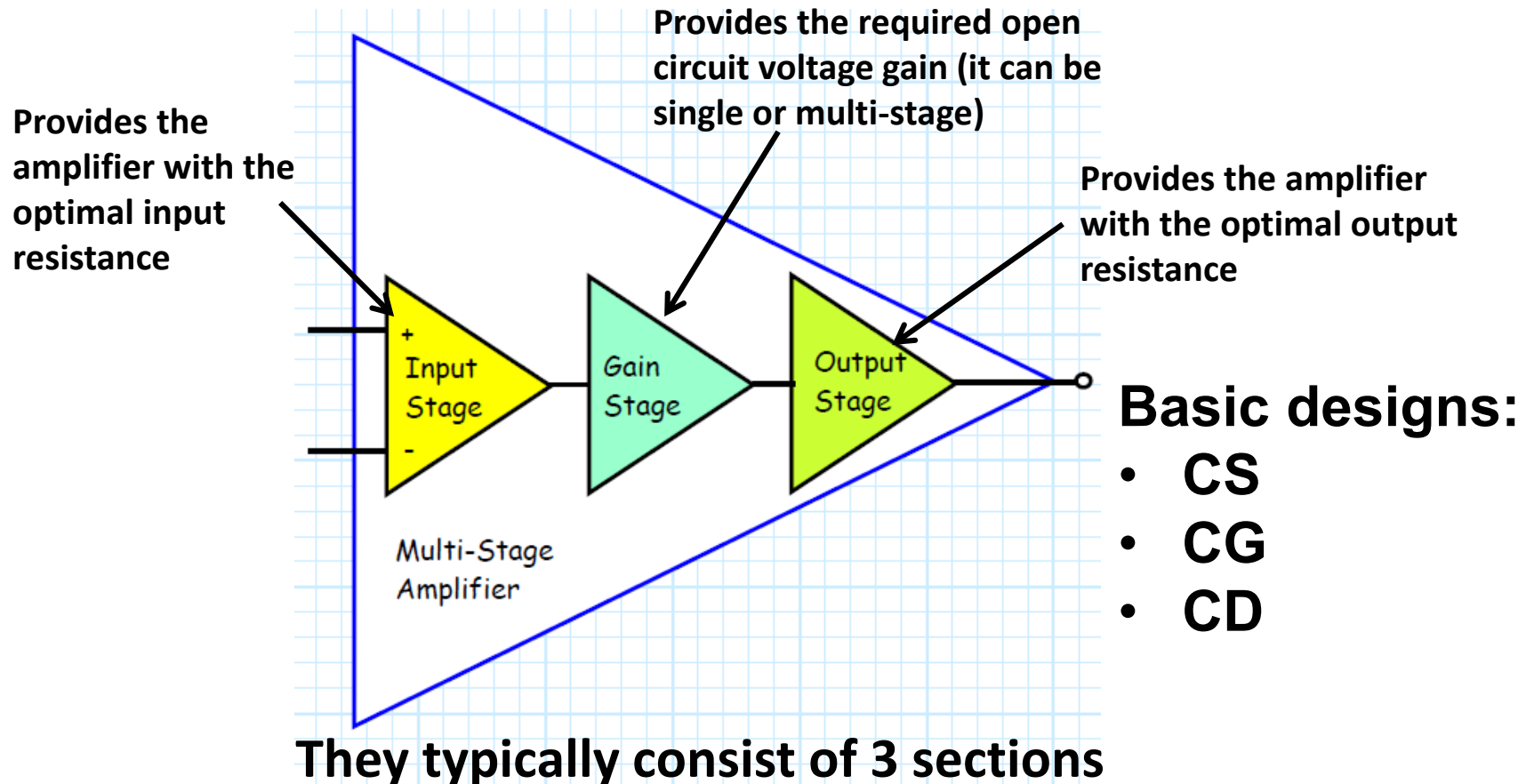Multi-stage amplifiers combine basic designs in such a way that they take advantage of the attractive characteristic and compensate for the sub-optimal features of each design.




Multi-stage amplifiers

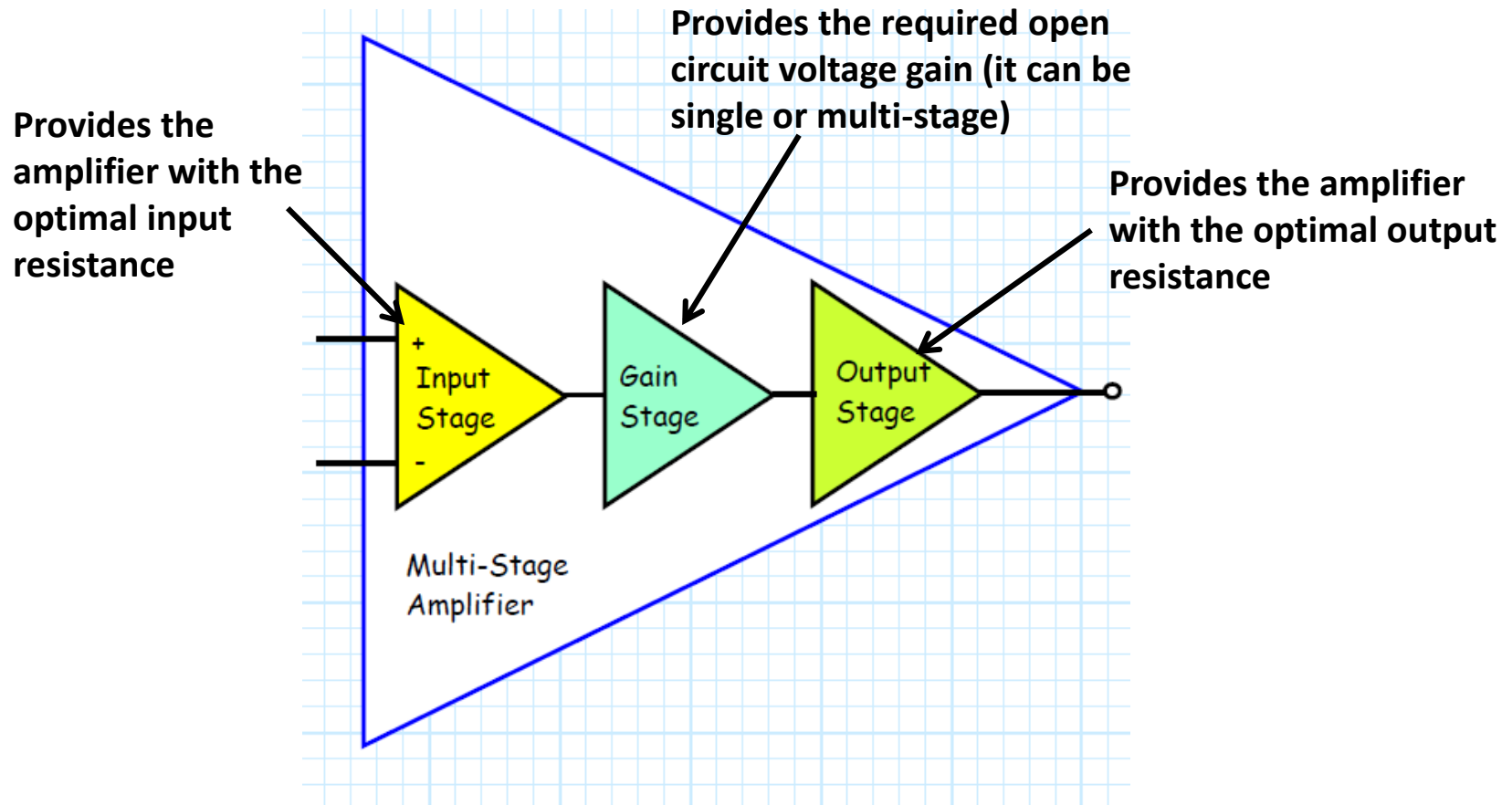


It is important to understand which basic configurations to select per each stage, and how placing two basic configurations in series affects their performance.

Multi-stage amplifiers

 

Cascade amplifier

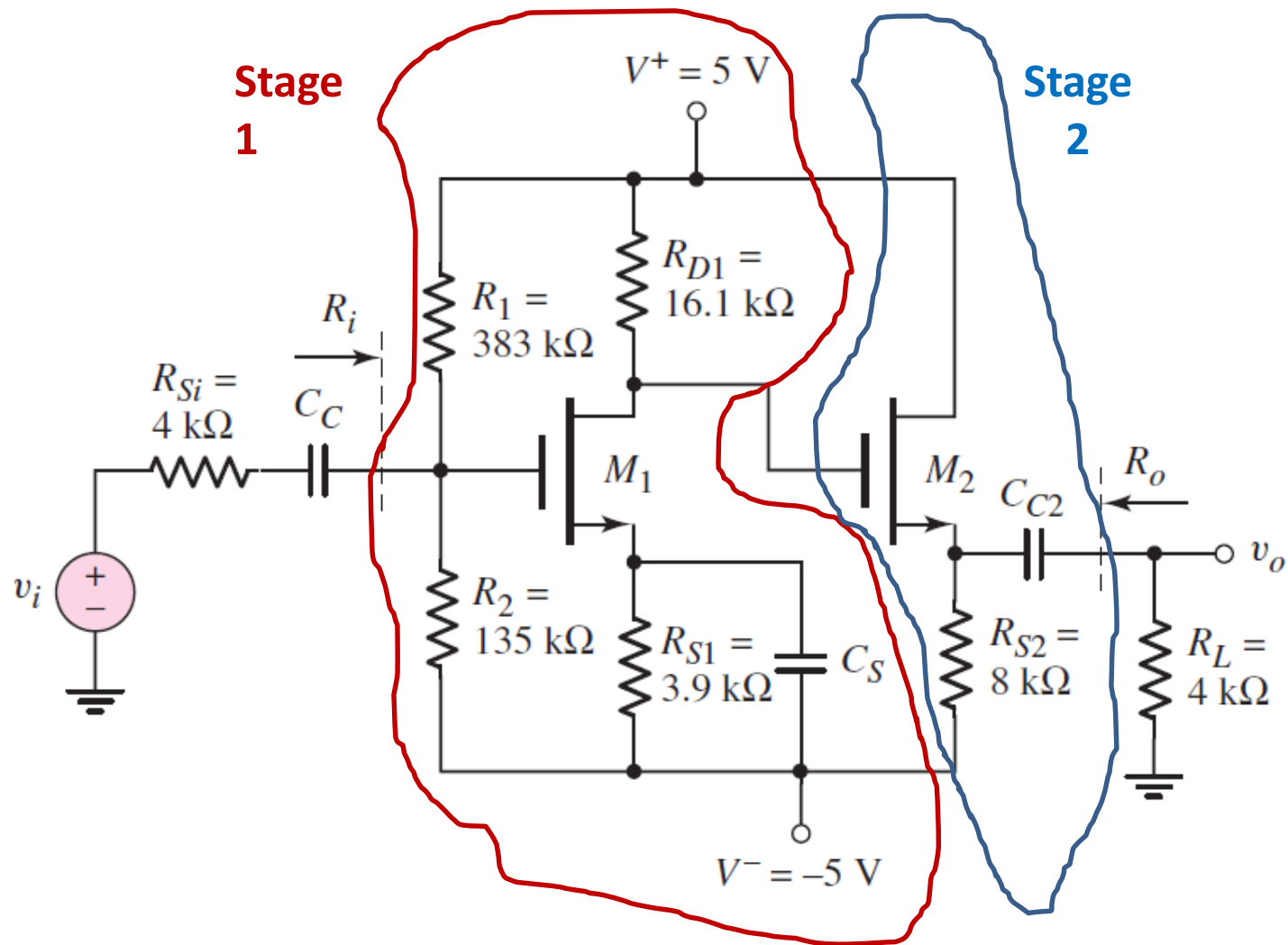

In-class problem

- 4.68 The transistor parameters in the circuit in Figure P4.68 are $V_{TN1} = 0.6$ V, $V_{TP2} = -0.6$ V, $K_{n1} = 0.2$ mA/V², $K_{p2} = 1.0$ mA/V², and $\lambda_1 = \lambda_2 = 0$. The circuit parameters are $V_{DD} = 5$ V and $R_{in} = 400$ k Ω . (a) Design the circuit such that $I_{DQ1} = 0.2$ mA, $I_{DQ2} = 0.5$ mA, $V_{DSQ1} = 2$ V, and $V_{SDQ2} = 3$ V. The voltage across R_{S1} is to be 0.6 V. (b) Determine the small-signal voltage gain $A_v = v_o/v_i$.


 


Figure P4.68

In addition determine the input and output resistance.

At home compare the characteristics of the two stages as isolated with the characteristics of the cascade amplifier

In-class problem, solution

 

$$R_{S1} = \frac{V_{S1}}{I_{D1}} = \frac{0.6}{0.2\text{mA}} = 3\text{K}\Omega \quad R_{D1} = \frac{V_{DD} - V_{D1}}{I_{D1}} \quad V_{D1} = V_{DS} + V_{S1} = 2 + 0.6 = 2.6\text{V}$$

$$R_{D1} = \frac{5 - 2.6}{0.2\text{mA}} = 12\text{K}\Omega$$

Assuming M_1 in saturation: $I_{D1} = K_n (V_{GS1} - V_{TN})^2 \Rightarrow 0.2\text{mA} = 0.2\text{mA} (V_{GS1} - 0.6)^2$

$$V_{GS1} = 1.6\text{V}$$

$$V_{G1} = V_{GS1} + V_{S1} = 1.6 + 0.6 = 2.2\text{V} \quad V_{G1} = \frac{R_2 V_{DD}}{R_1 + R_2} = \frac{R_1 // R_2}{R_1} \cdot V_{DD}$$

$$R_1 = R_1 // R_2 = 400\text{K}\Omega \Rightarrow \frac{400\text{K} \cdot 5}{R_1} = 2.2\text{V} \Rightarrow R_1 = 909\text{K}\Omega$$

$$\frac{909\text{K} \cdot R_2}{R_2 + 909\text{K}} = 400\text{K}\Omega \Rightarrow R_2 = 714\text{K}\Omega$$

$$V_{DS1} > V_{GS1} - V_{TN} \quad (\text{Saturation assumption is verified})$$

Assuming M_2 in saturation: $I_{D2} = K_p (V_{SG2} + V_{TP})^2 \Rightarrow 0.5\text{mA} = 1\text{mA} (V_{SG2} + 0.6)^2$


$$V_{SG2} = 1.307\text{V} \quad V_{S2} = V_{D1} + V_{SG2} = 2.6 + 1.307 = 3.907\text{V}$$

$$R_{S2} = \frac{V_{DD} - V_{S2}}{I_{D2}} = \frac{5 - 3.907}{0.5\text{mA}} = 2.2\text{K}\Omega$$


$$R_{D2} = \frac{V_{D2}}{I_{D2}} \quad V_{D2} = V_{S2} - V_{SD2} = 3.907 - 3 = 0.907\text{V} \quad R_{D2} = \frac{0.907}{0.5\text{mA}} = 1.8\text{K}\Omega$$

$$V_{SD2} > V_{SG2} + V_{TP} \quad (V_{SD2} = 3\text{V}; V_{SG2} = 1.307\text{V}; V_{TP} = -0.6)$$

In-class problem, solution

 

SMALL-SIGNAL MODEL

 

$$R_i = R_1 // R_2 = 400 \text{ k}\Omega$$


$$A_v = \frac{v_o}{v_i} \quad v_o = g_{m2} v_{gs2} R_{D2} \quad v_{gs2} = g_{m1} v_{gs1} R_{D1}$$

$$v_{gs1} = v_i \quad v_o = g_{m1} g_{m2} R_{D1} R_{D2}$$

$$g_{m1} = 2 \sqrt{K_n I_{D1}} = 2 \sqrt{0.2 \text{ mA} \cdot 0.2 \text{ mA}} = 0.4 \text{ mA/V}$$

$$g_{m2} = 2 \sqrt{K_p I_{D2}} = 2 \sqrt{1 \text{ mA} \cdot 0.5 \text{ mA}} = 1.414 \text{ mA/V}$$
 
$$A_v = (0.4 \text{ mA/V})(1.414 \text{ mA/V})(12 \text{ k}\Omega)(1.8 \text{ k}\Omega) = 12.3$$



$$R_o = \frac{v_x}{i_x} = \frac{1}{g_{m2}} // R_{D2} = 500 \Omega$$

Overview of lecture 10

- Cascode amplifiers (Neamen 4.8.2)
- The Bipolar Junction Transistor (BJT):
Structure, Operating regions, DC analysis,
Load lines (Neamen-From 5.1.1 to 5.1.5)