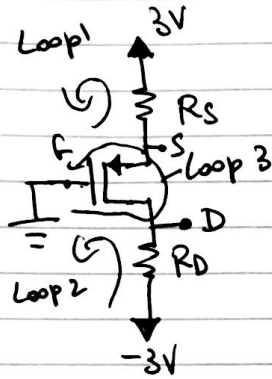


ECE 322L-Spring 2020-Homework 1

Solution



$$I_{DQ} = 60 \mu\text{A}$$

$$V_{SDQ} = 2.5 \text{ V}$$

$$V_{TP} = -0.4 \text{ V}$$

$$K_p = 30 \mu\text{A/V}^2$$

(a) Designing the circuit is equivalent to determine the values of R_S and R_D to obtain the desired Q point.

Assume the desired Q point lays in the saturation region: $I_{DQ} = K_p (V_{SGQ} + V_{TP})^2$ $V_{SGQ} > |V_{TP}|$ and $V_{SDQ} > V_{SGQ} + V_{TP}$

$$I_{DQ} = 60 \mu\text{A} = 30 \mu\text{A} (V_{SGQ} - 0.4)^2 \Rightarrow$$

$$\Rightarrow V_{SGQ} = 1.814 \text{ V}$$

$$V_{SGQ} > |V_{TP}| \quad V_{SD, \text{set}} = 2.214 \text{ V} \Rightarrow V_{SDQ} > V_{SD, \text{set}}$$

The saturation assumption is verified.

Using a KVL at loop 1 (see circuit diagram), we obtain

$$I_{DQ} = \frac{3 - V_{SGQ}}{R_S} = 0.060 \text{ mA} \Rightarrow \frac{3 - 1.814}{R_S} = 0.060 \text{ mA} \Rightarrow$$

$$\Rightarrow R_S = \frac{3 - 1.814}{0.060 \text{ mA}} = 19.77 \text{ k}\Omega$$

Similarly using a KVL at loop 2, we obtain

$$V_D - R_D I_{DQ} - (-3) = 0$$

$$R_D = \frac{V_D - (-3)}{I_{DQ}}$$

$$R_D = 38.57 \text{ k}\Omega$$

$$V_D = V_{SGQ} - V_{SDQ} = 1.814 - 2.5 = -0.686 \text{ V}$$

$$(V_D + V_{SDQ} = V_{SGQ})$$

(KVL @ Loop 3)

$$|V_{TP}| (+5\%) = 0.4 + |V_{TP}| \cdot 0.05 = 0.4 + 0.4 \cdot 0.05 = 0.4 + 0.02 = 0.42V$$

$$k_p (-5\%) = 30 \mu - k_p \cdot 0.05 = 30 \mu - 30 \cdot 0.05 \mu = 30 \mu - 1.5 \mu = 28.5 \mu A/V^2$$

Considering the KVL at loop 1 and using the transistor equations (assuming that the transistor remain in saturation), we obtain

$$3 = I_D R_S + V_{SG} = 0.0285 \mu (V_{SG})^2$$

$$3 = I_D R_S + V_{SG} = 0.0285 \mu (V_{SG}^2 - 0.84 V_{SG} + 0.1764)(19.77) + V_{SG}$$

The equation above yields $V_{SG} = 1.849V$

I_D becomes then

$$I_D = 28.5 \mu (1.849 - 0.42)^2 = 58.2 \mu A$$

$$V_{SD} = 6 - I_D (R_S + R_D) = 6 - (0.0582 \mu)(19.77 + 38.57k) = 2.605V$$

V_{SD} is still larger than $V_{SD, sat} = V_{SG} + V_{TP}$. Thus the assumption of the transistor remaining in saturation is correct.