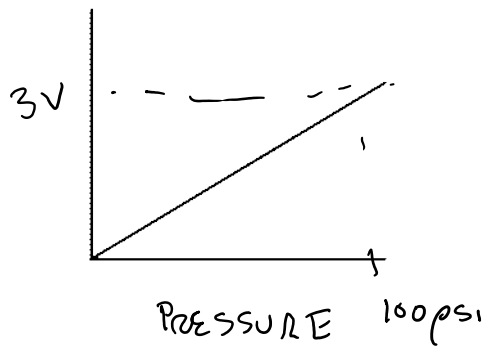


# Lecture 22 - Analog to Digital Conversion



Wednesday, April 22, 2020 2:37 PM



SAMPLE


1024 POSSIBLE VALUES
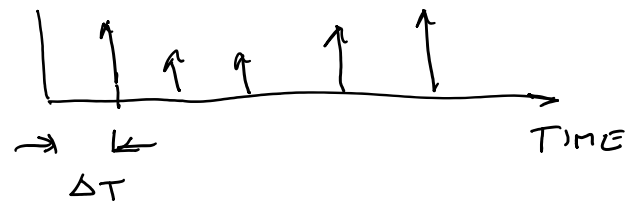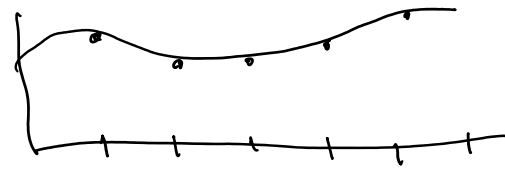
$$\frac{100}{1024} = 0.097 \text{ psi/bit}$$



ISSUES W/ SAMPLING

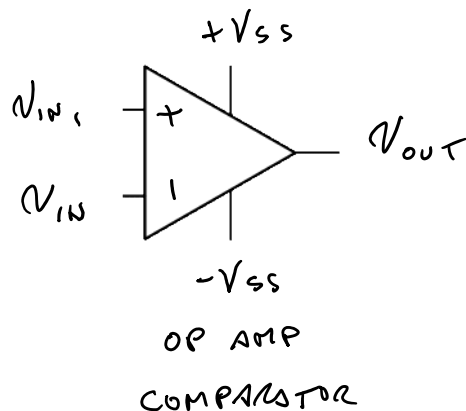- ① QUANTIZATION
- ② SAMPLING RATE
- ③ JITTER
- ④ ALIASING



$$V_{IN1} > V_{IN2} \quad V_{OUT} = +V_{SS}$$


$$V_{IN2} > V_{IN1} \quad V_{OUT} = -V_{SS}$$

OP AMPS


$$Z_{IN} = \infty$$

$$Z_{OUT} = 0$$


$$A_V = \infty$$

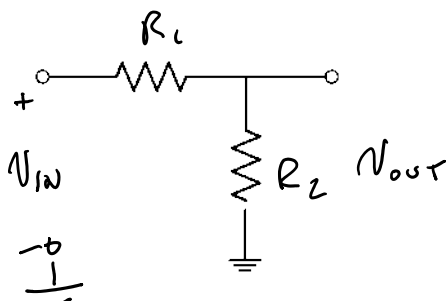
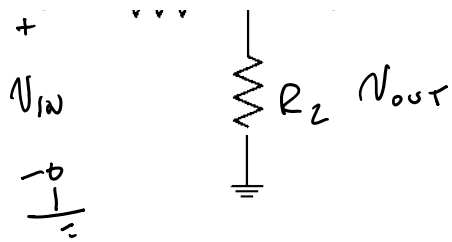
$$V_{OUT} = \frac{V_{IN} R_2}{R_1 + R_2}$$



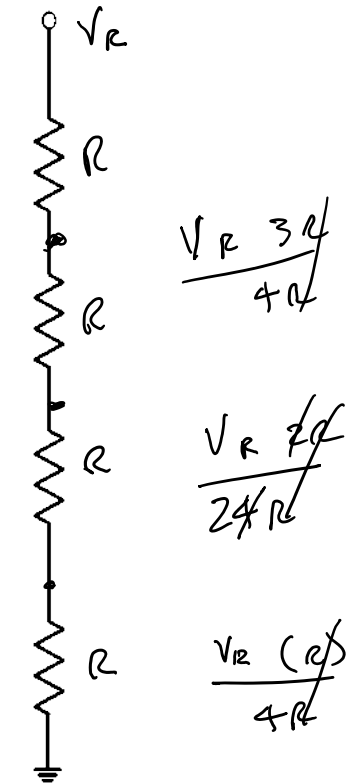
$$V_{out} = \frac{V_{in} R_2}{R_1 + R_2}$$



MAX ERROR

$$\frac{V_R}{4} \cdot \epsilon$$

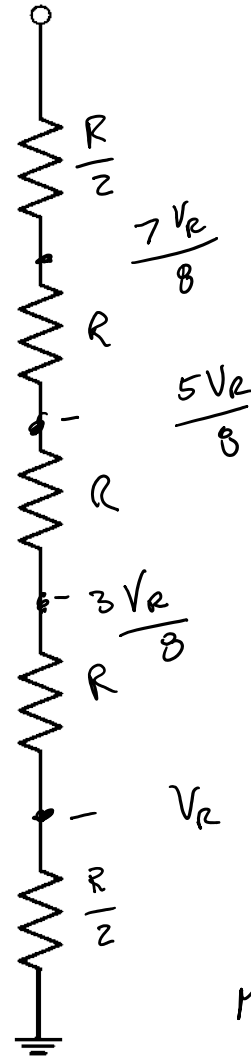

$$V_R \cdot \frac{R}{2} \cdot \frac{1}{4R} = \frac{V_R}{8}$$

$$\text{MAX ERROR } \frac{V_R}{8} - \epsilon$$

# 3bit Flash ADC

DIRECT  
CONVERSION  
OR  
"FLASH"  
ADC


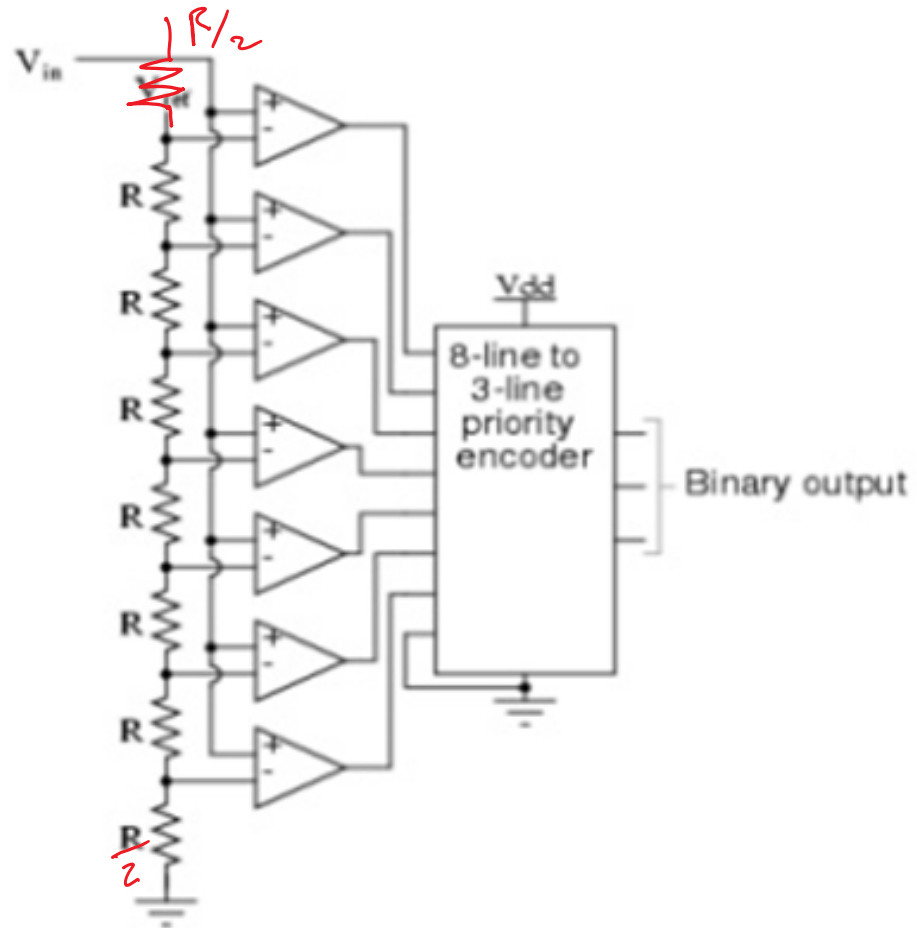



Fig 1.2 Block Diagram of Flash ADC [17]

## DIGITAL TO ANALOG CONVERTER

LET  $V_{REF} = 15V$

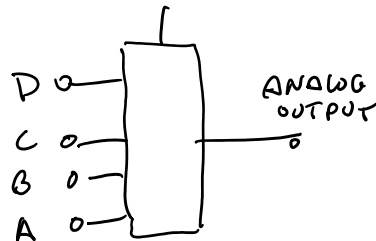


D	C	B	A	$V_{OUT}$
0	0	0	0	0
0	0	0	1	1V
0	0	1	0	2V
0	0	1	1	3V
				⋮
1	1	1	1	15V

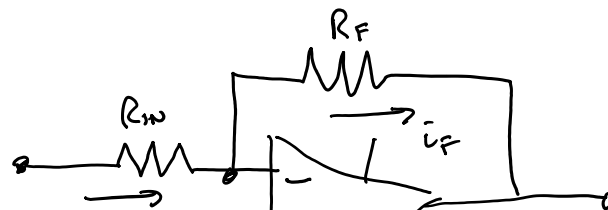


$$Z_{IN} = \infty$$

$$i_{IN} = \frac{V_{IN}}{R_{IN}}$$

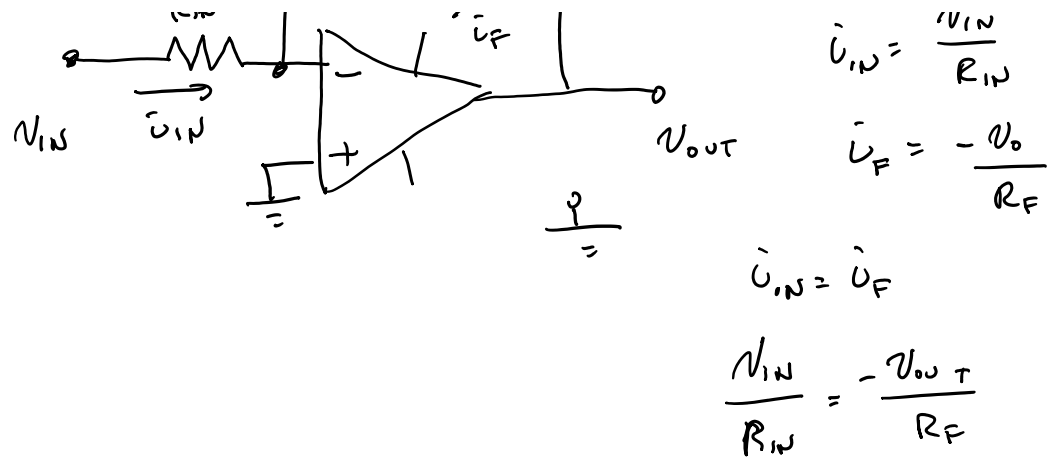
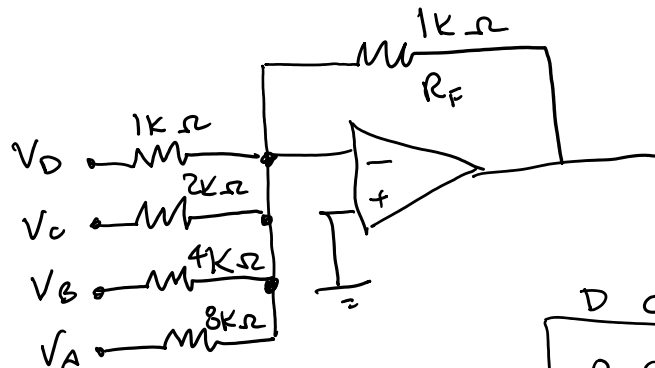
$$Gain = \frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_{IN}}$$



$$V_x = 0 \text{ or } 5V$$

D	C	B	A	V <sub>OUT</sub>
0	0	0	0	0
0	0	0	1	-0.62V
0	0	1	0	-1.25
0	0	1	1	-1.875
1	1	1	1	-9.375

## SUCCESSIVE APPROXIMATION

- ① COUNTING - REGISTER COUNTS FROM ZERO UNTIL OP AMP COMPARATOR OUTPUT GOES FROM HIGH TO LOW

\*\* VARIABLE CONVERSION TIME

- ② BIT-WISE - START WITH MSB AND WORK TOWARDS LSB  
CONSTANT CONVERSION TIME.


## REAL-LIFE SIGNALS CHANGE WITH TIME

WE NEED TO KEEP  $V_{IN}$  DURING THE CONVERSION PROCESS

WE MAKE A COPY OF THE SIGNAL

1. R

WE MAKE A COPY OF THE SIGNAL

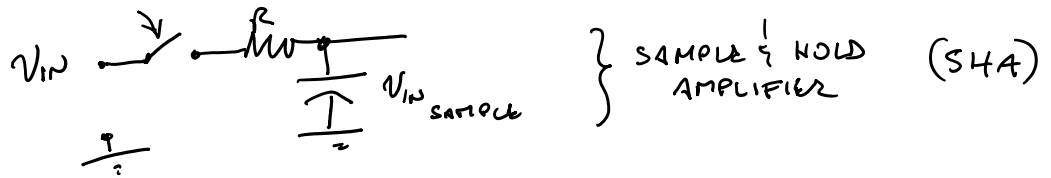

### ADC Conceptual Configuration

