

# ECE 322L

## Electronics 2



02/27/20- Lecture 11

DC analysis of BJT-based circuits

---
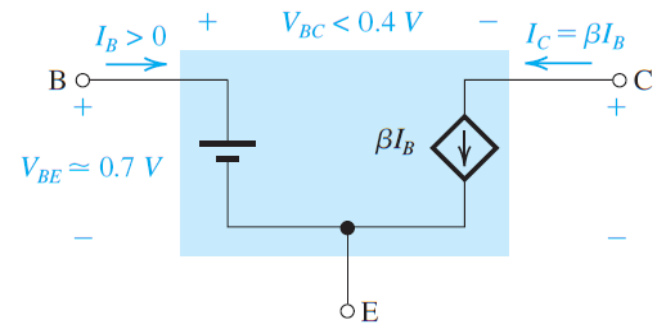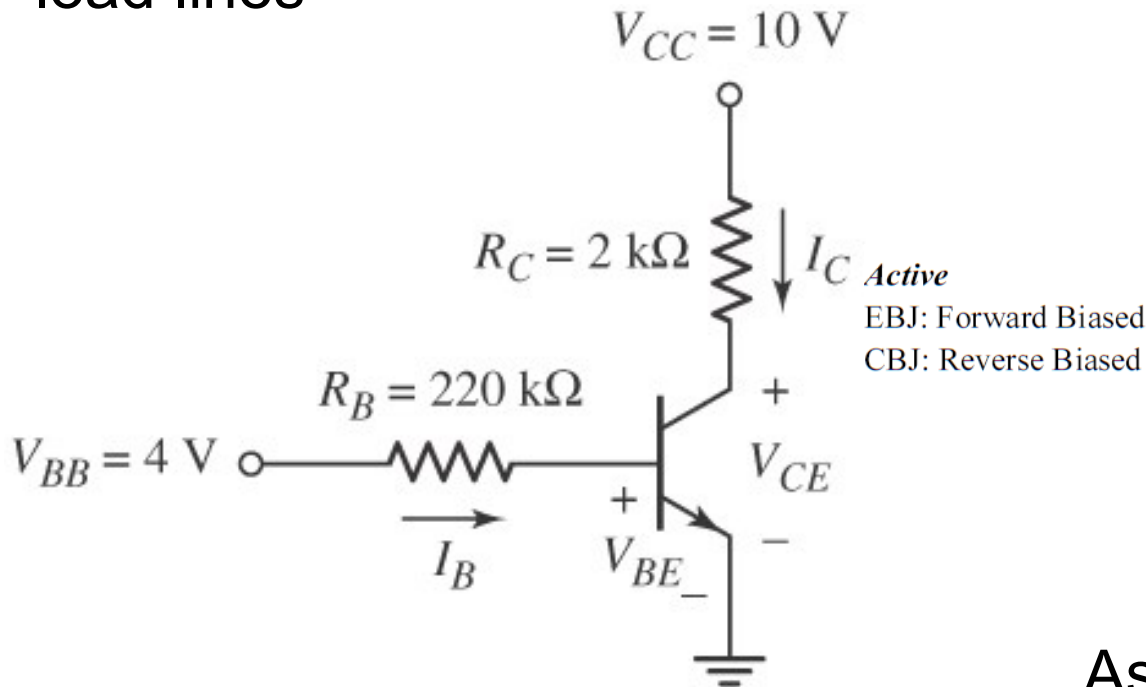
# In-class problem 1

The transistor parameters are  $V_{BE}(\text{on}) = 0.7\text{V}$ ,  $V_{CE}(\text{sat}) = 0.2\text{V}$  and  $\beta = 200$ . Calculate  $I_C$ ,  $I_B$ ,  $I_E$  and  $V_{CE}$ . Sketch the input and output load lines




Assume the BJT is in active mode.

$$V_{CE} > V_{CE}(\text{sat}) \quad V_{BE} = V_{BE}(\text{on}), \quad I_B > 0, \quad \text{and} \quad I_C = \beta I_B$$
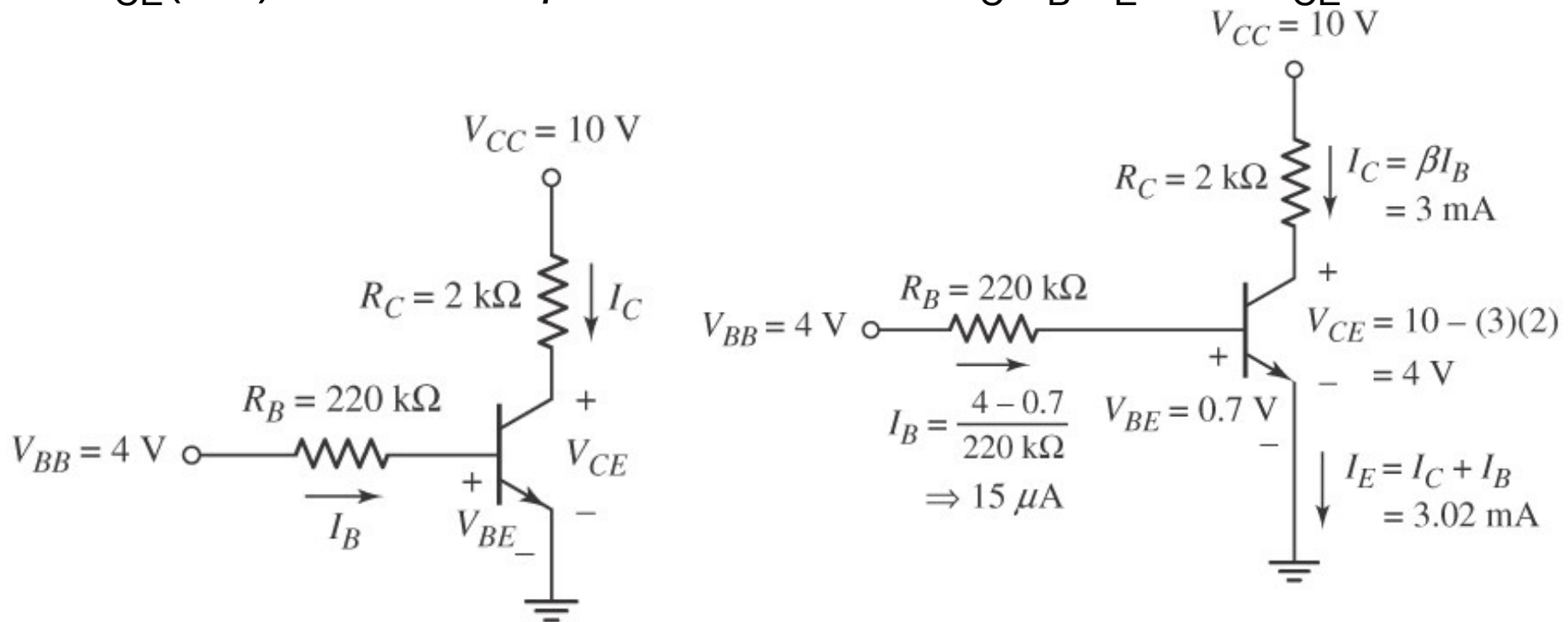
# In class-Problem 1-Solution




The transistor parameters are  $V_{BE}(\text{on}) = 0.7\text{V}$ ,  $V_{CE}(\text{sat}) = 0.2\text{V}$  and  $\beta = 200$ . Calculate  $i_C$ ,  $i_B$ ,  $i_E$  and  $V_{CE}$ .



Assume the BJT is in active mode.


$$V_{CE} > V_{CE}(\text{sat}) \quad V_{BE} = V_{BE}(\text{on}), \quad I_B > 0, \quad \text{and} \quad I_C = \beta I_B$$

# In class-Problem1-Solution

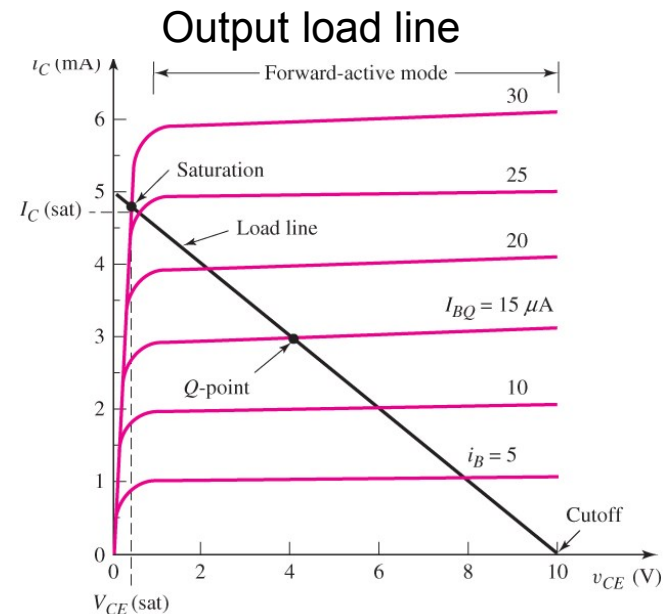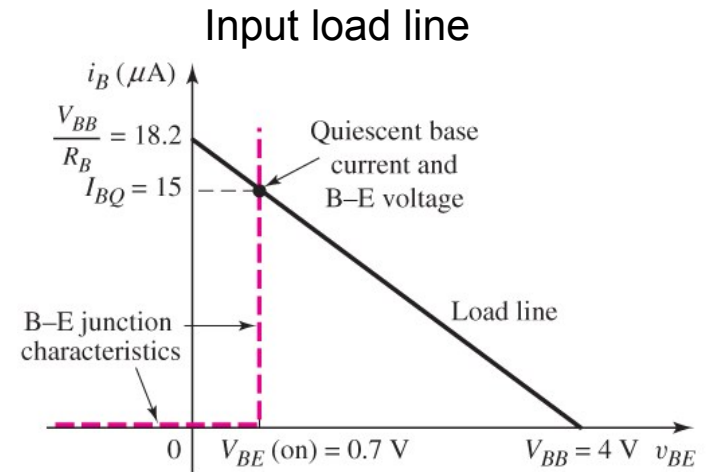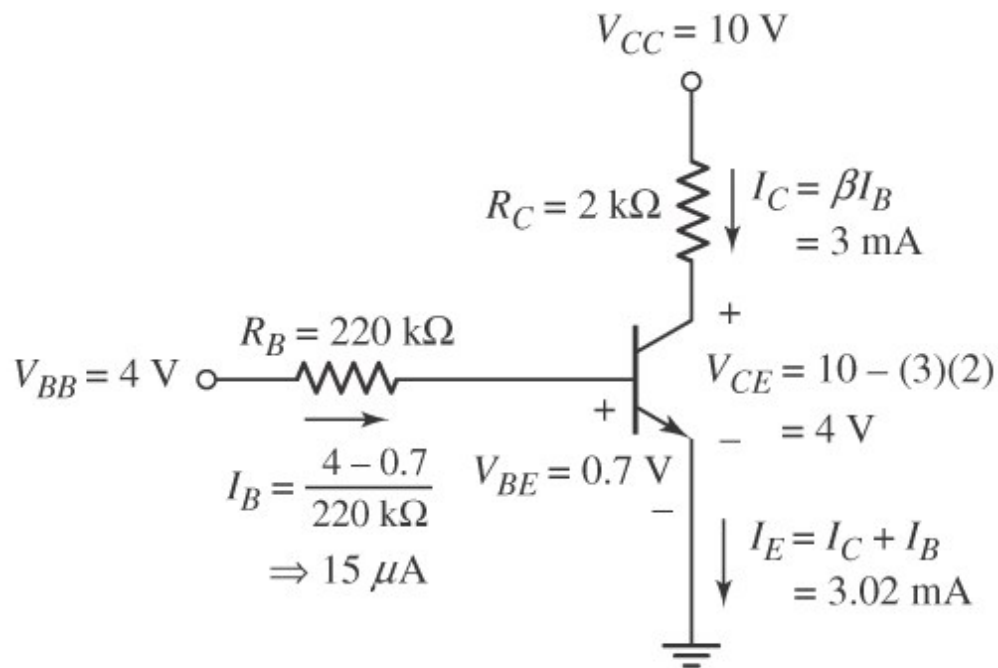

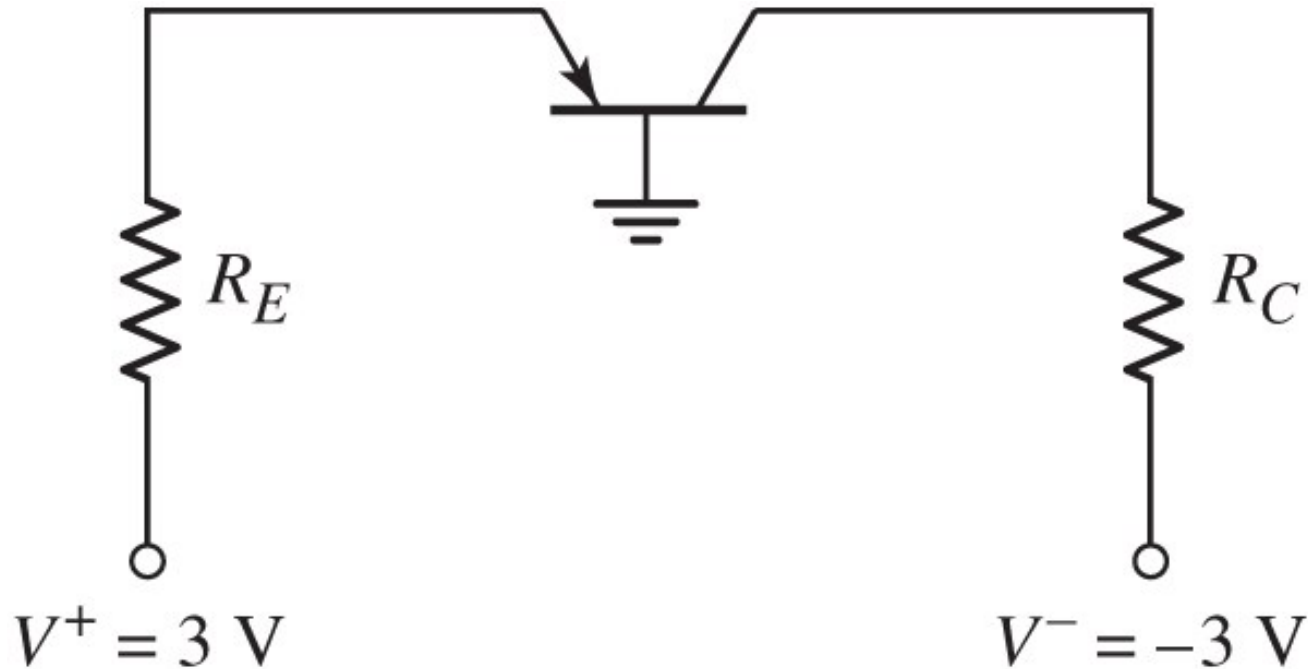
# In-class problem 2

Consider the circuit below. Find the value of  $R_E$  and  $R_C$  such that  $I_{EQ}=0.125\text{mA}$  and  $V_{ECQ}=2.2\text{V}$ . The transistor parameters are  $\beta=110$  and  $V_{EB}(\text{on}) = 0.7\text{V}$ . Do not assume  $I_{EQ}=I_{CQ}$ .


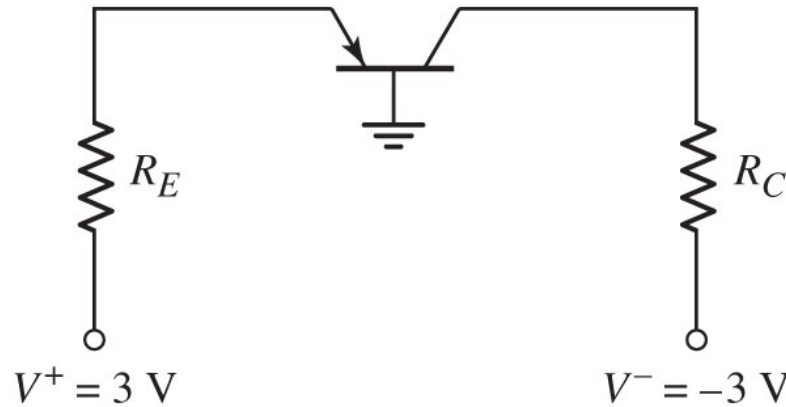
# In-class problem 2, solution

Consider the circuit below. Find the value of  $R_E$  and  $R_C$  such that  $I_{EQ}=0.125\text{mA}$  and  $V_{ECQ}=2.2\text{V}$ . The transistor parameters are  $\beta=110$  and  $V_{EB}(\text{on}) = 0.7\text{V}$ . Do not assume  $I_{EQ}=I_{CQ}$ .



$$I_{EQ} = \frac{V^+ - V_{EB}(\text{on})}{R_E} \Rightarrow R_E = \frac{3 - 0.7}{0.125} = 18.4 \text{ k}\Omega$$

$$V_C = V_{EB}(\text{on}) - V_{ECQ} = 0.7 - 2.2 = -1.5 \text{ V}$$

$$I_{CQ} = \left( \frac{\beta}{1 + \beta} \right) I_{EQ} = \left( \frac{110}{111} \right) (0.125) = 0.1239 \text{ mA}$$

$$R_C = \frac{V_C - V^-}{I_{CQ}} = \frac{-1.5 - (-3)}{0.1239} = 12.1 \text{ k}\Omega$$

# In-class problem 3

- D5.40 (a) The circuit shown in Figure P5.40 is to be designed such that  $I_{CQ} = 0.5 \text{ mA}$  and  $V_{CEQ} = 2.5 \text{ V}$ . Assume  $\beta = 120$ . Sketch the load line and plot the  $Q$ -point. (b) Pick standard values of resistors that are close to the designed values. Assume that the standard resistor values vary by  $\pm 10$  percent. Plot the load lines and  $Q$ -point values for the maximum and minimum values of  $R_B$  and  $R_C$  values (four  $Q$ -point values).


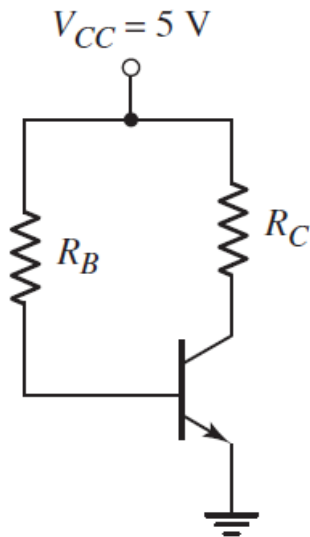


Figure P5.40

<https://www.daycounter.com/Calculators/Standard-Resistor-Value-Calculator.phtml>

# In-class problem 3, solution

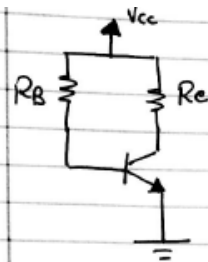

$$I_{CQ} = 0.5 \mu A \quad V_{CEQ} = 2.5 V$$

$$\beta = 120$$

$$V_{CC} = 5 V$$

$$V_{CEQ} > V_{CE,sat}$$


(a) KVL @ the output loop:  $V_{CC} - R_C I_{CQ} - V_{CEQ} = 0$   
 $R_C = \frac{5 - 2.5}{0.5 \mu A} = 5 k\Omega \Rightarrow R_C = 5.1 k\Omega$

$$I_{BQ} = \frac{0.5}{120} = 0.00417 \mu A = 4.17 \mu A$$

KVL @ the input loop:  $V_{CC} - R_B I_{BQ} - V_{BE(on)} = 0$

$$R_B = \frac{5 - 0.7}{0.00417 \mu A} = 1032 k\Omega \Rightarrow R_B = 1 M\Omega$$

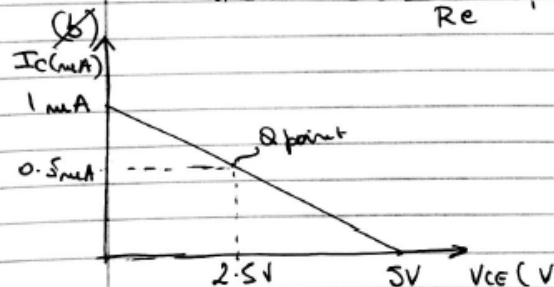Load line:  $I_C = \frac{V_{CC} - V_{CE}}{R_C}$ ,  $V_{CE} = 0 \Rightarrow I_C = \frac{V_{CC}}{R_C}$ ,  $I_C = 0 \Rightarrow V_{CE} = V_{CC}$



(b) The two new load lines can be easily sketched considering that the point for  $I_C = 0$  will remain at  $V_{CE} = V_{CC}$  in both cases. On the other hand, the other extreme of the load line will move to



# In-class problem 3, solution

$$\frac{V_{CC}}{R_C + 0.1 R_C} = \frac{5}{5.61k} = 0.891 \mu A$$

$$\frac{V_{CC}}{R_C - 0.1 R_C} = \frac{5}{4.59k}$$

$$= 1.09 \mu A$$

$$\frac{V_{CC}}{R_C - 0.1 R_C} = \frac{5}{4.59k}$$

Case 1:  $R_B + 10\%$   $R_C + 10\%$

$$R_B = 1M (1.1) = 1.1M\Omega \quad R_C = 5.61k\Omega$$

$$I_{BQ} = \frac{5 - 0.7}{1.1M} = 3.91 \mu A \Rightarrow I_{CQ} = \beta I_{BQ} = 0.463 \mu A$$

$$V_{CEQ} = V_{CC} - R_C I_{CQ} = 5 - 5.61k \cdot 0.463 \mu = 2.37V$$

Case 2:  $R_B - 10\%$   $R_C + 10\%$

$$R_B = 1.0M (0.9) = 0.9M\Omega \quad R_C = 5.61k\Omega$$

$$I_{BQ} = \frac{5 - 0.7}{0.9} = 4.78 \mu A \Rightarrow I_{CQ} = \beta I_{BQ} = 0.573 \mu A$$

$$V_{CEQ} = V_{CC} - R_C I_{CQ} = 5 - 5.61k \cdot 0.573 \mu = 1.78V$$

Case 3:  $R_B + 10\%$   $R_C - 10\%$

$$R_B = 1.1M\Omega \quad R_C = 4.59k\Omega$$

$$I_{BQ} = 3.91 \mu A \quad I_{CQ} = 0.463 \mu A$$

$$V_{CEQ} = 5 - 4.59k \cdot 0.463 \mu = 2.85V$$

Case 4:  $R_B - 10\%$   $R_C - 10\%$

$$R_B = 0.9M\Omega \quad R_C = 4.59k\Omega$$

$$I_{BQ} = 4.78 \mu A \Rightarrow I_{CQ} = 0.573 \mu A$$

$$V_{CEQ} = 2.37V$$

# In-class problem 3, solution

