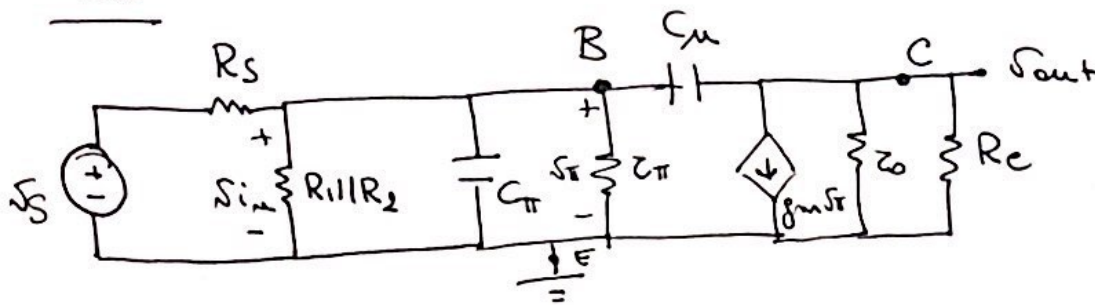


MILLER EFFECT IN DIFFERENT CONFIGURATIONS

CE




C_μ : Capacitor between the input and the output

$$C_{Hi} = C_\mu (1 - A_V) \quad A_V < 0 \text{ and large}$$

$$C_{Ho} = C_\mu \left(1 - \frac{1}{A_V}\right) \quad \text{Miller effect is significantly reducing the GBW product.}$$


CB

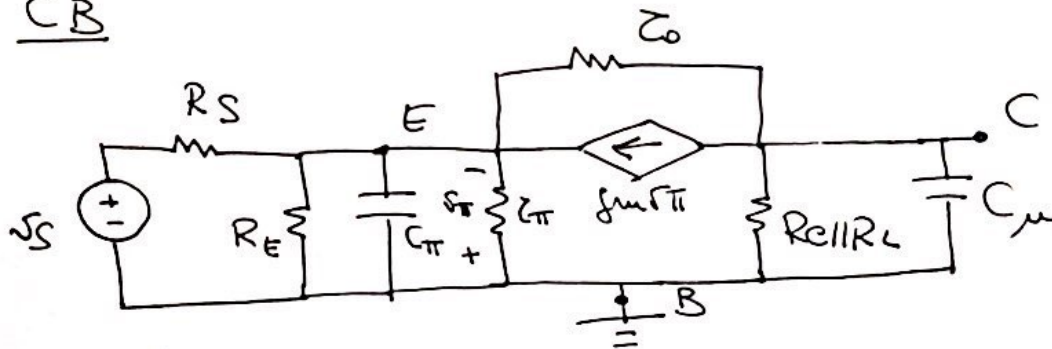

$A_V > 0$ and large

However, there is no capacitor between the input and the output. Thus the Miller effect doesn't affect the GBW product.

CC

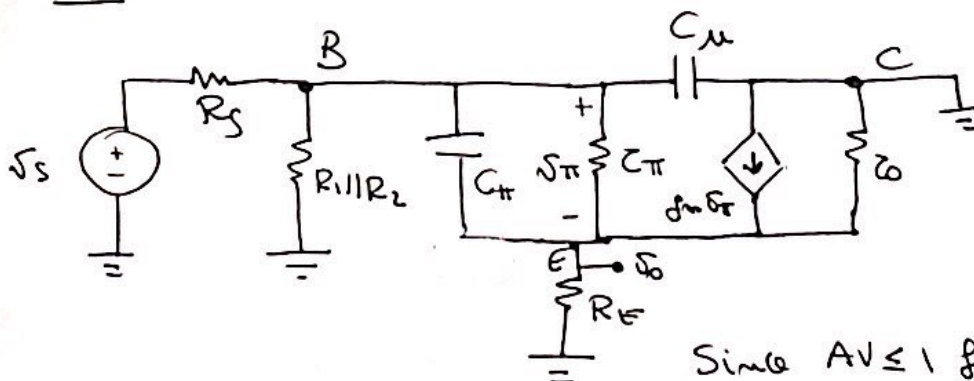

C_π is the capacitor between the input and the output.

Thus

$$C_{Hi} = C_\pi (1 - A_V)$$

$$C_{Ho} = C_\pi \left(1 - \frac{1}{A_V}\right)$$

Since $A_V \leq 1$ for a CC, the GBW ~~is~~ is not reduced due to the Miller effect.