
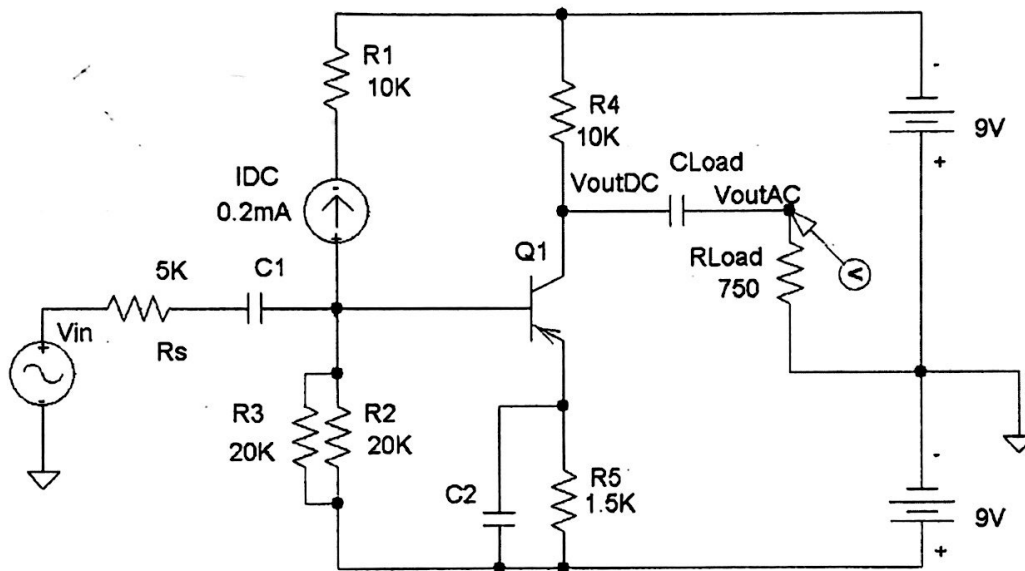

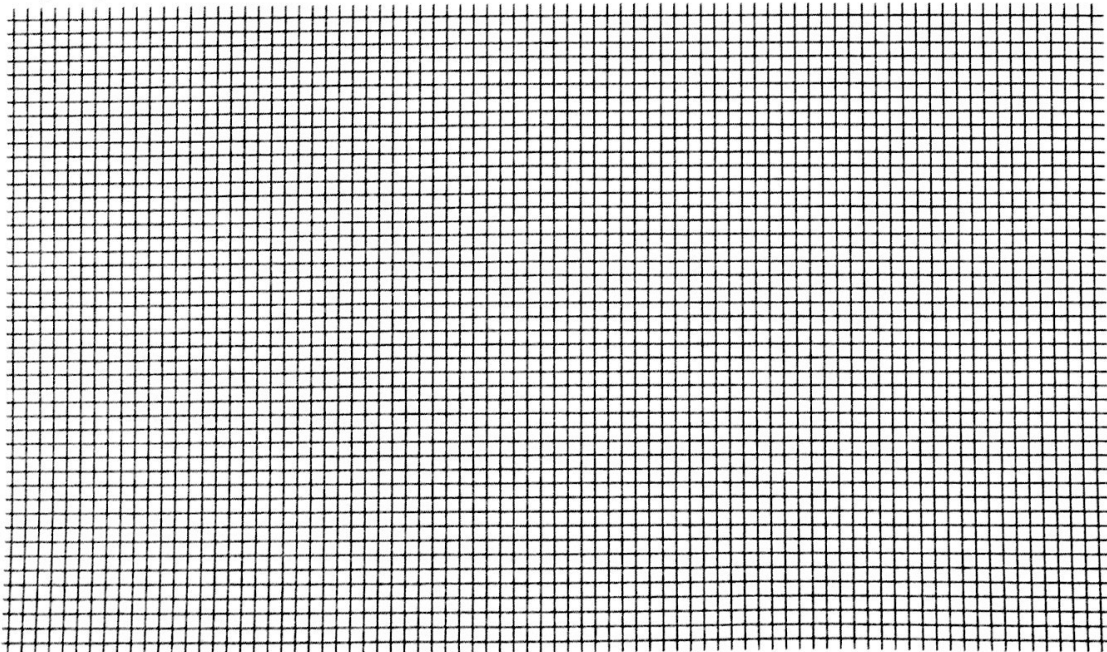
## Problem 1

For the circuit below:  $V_{EB(on)}=0.64\text{ V}$ ,  $\beta=200$ ,  $V_A=100\text{ V}$ ,  $V_{inAC} = 1\text{ mV}$  amplitude (i.e.,  $2\text{ mV}$  peak to peak sinusoidal signal) at  $1\text{ KHz}$ .



Given the above input voltage,  $V_{inAC}$ , sketch and accurately label a plot the output waveforms  $V_{out}$  on the graph paper provided on the next page. You may assume all capacitors are very large values and are thus, AC shorts.




## Problem 2

For the circuit below:  $V_{TN}=0.5\text{ V}$ ,  $K'_n=100\text{ }\mu\text{A/V}^2$ ,  $\lambda=0.1\text{ V}^{-1}$ ,  $W=0.18\text{ }\mu\text{m}$ ,  $L=5\text{ }\mu\text{m}$ ,  $V_{inAC} = 1\text{ mV}$  amplitude (i.e., 2m V peak to

(a) Identify the configuration for the first and the second stage.

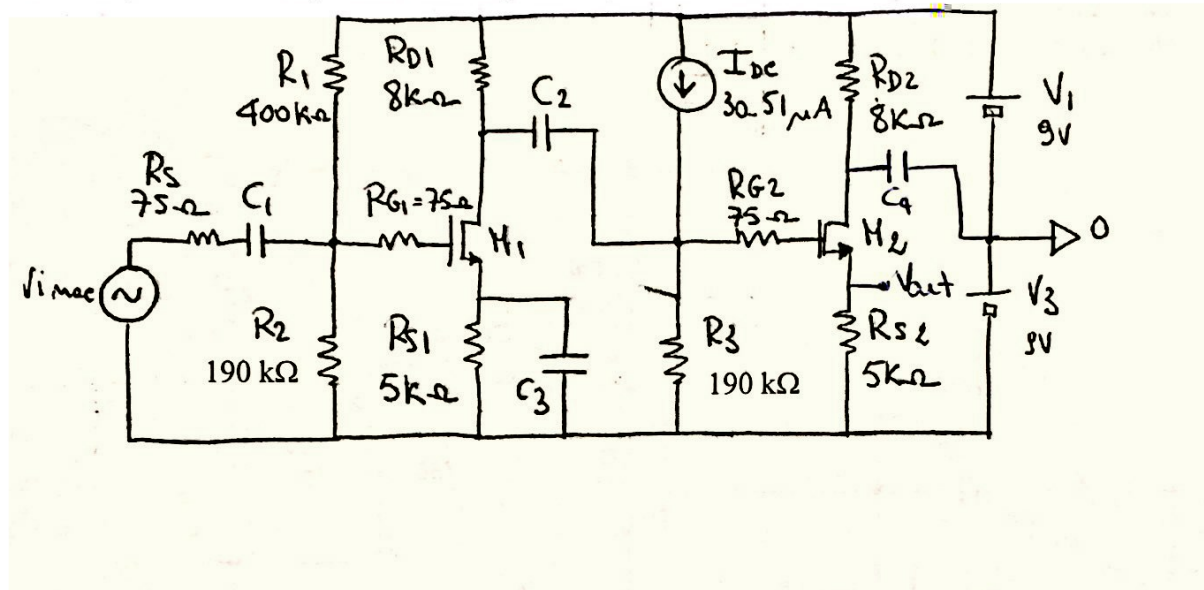
(b) Calculate the total small-signal voltage gain.

You may assume all capacitors are large enough to act as short-circuits in ac.



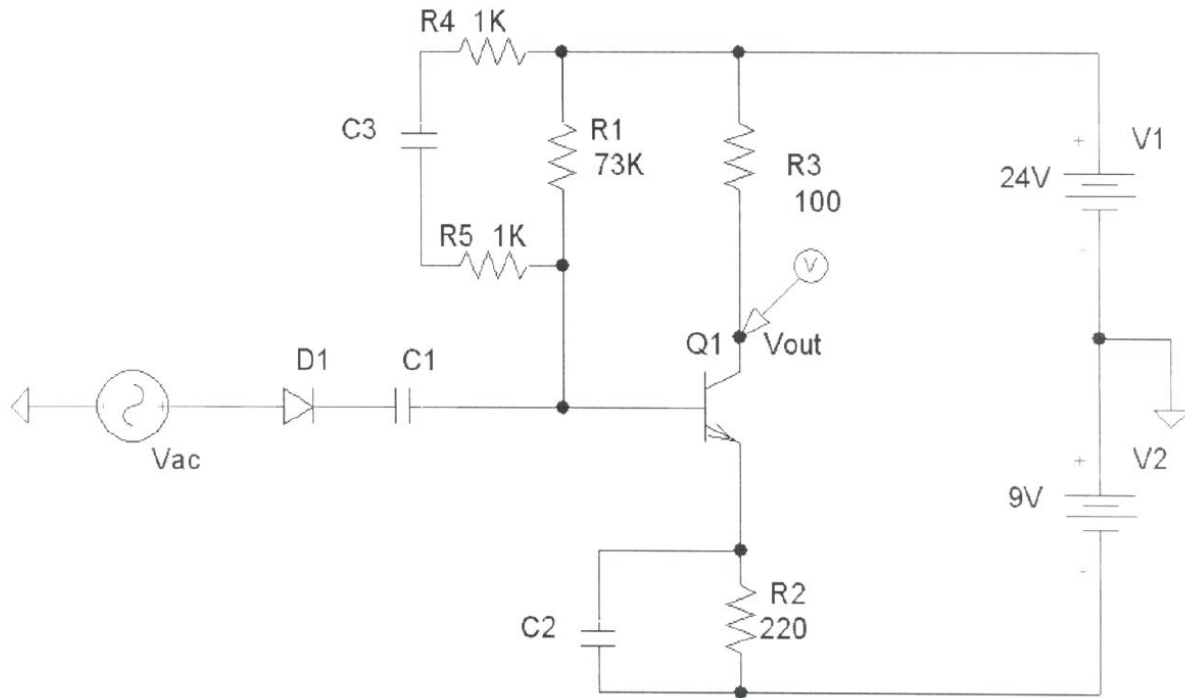
### Problem 3

For the circuit below  $r_{\text{diode}}=1\text{k}\Omega$ ,  $\beta=100$ ,  $V_A=15\text{ V}$ ,  $V_{\text{inAC}} = 1\text{ mV}$  amplitude (i.e.,  $2\text{ mV}$  peak to peak sinusoidal signal) at  $1\text{ KHz}$ .




Given the above input voltage,  $V_{\text{inAC}}$ , sketch and accurately label a plot of the output waveform  $V_{\text{out}}$  on the graph paper provided below. Replace the diode with the resistor  $r_{\text{diode}}$  in the small-signal analysis. Assume the turn on voltages for all forward biased junctions are  $0.7\text{ V}$ . You may assume all capacitors are very large values and are thus, AC shorts.

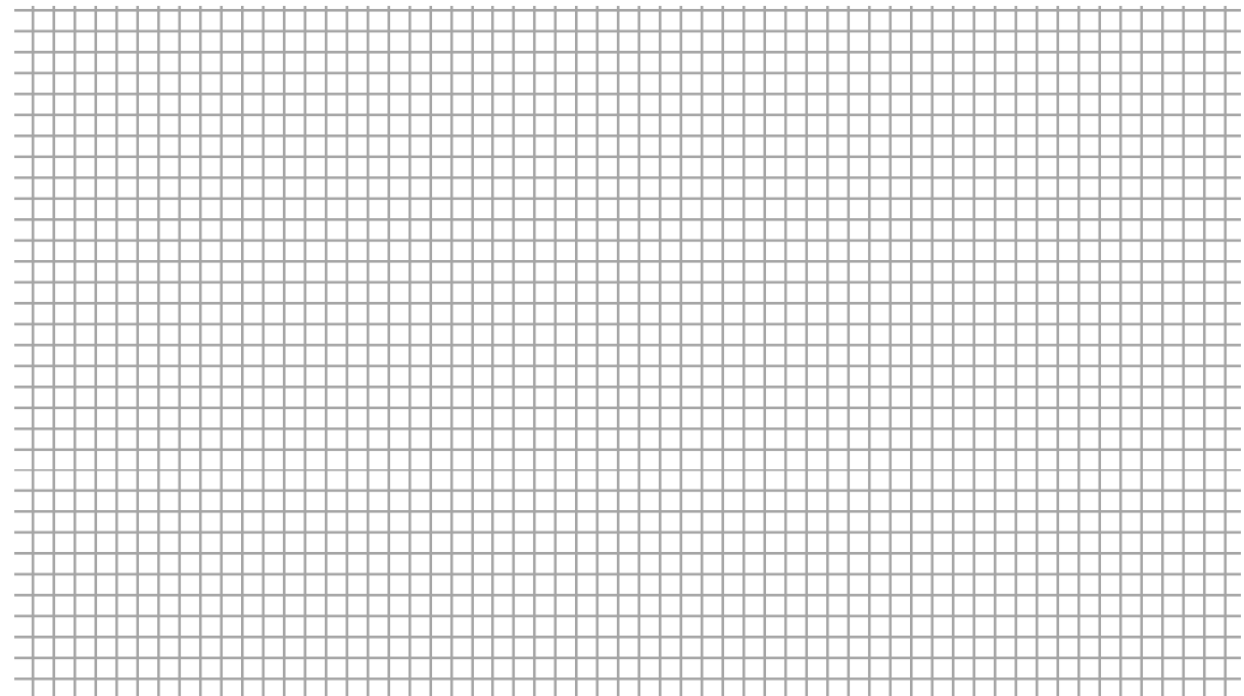
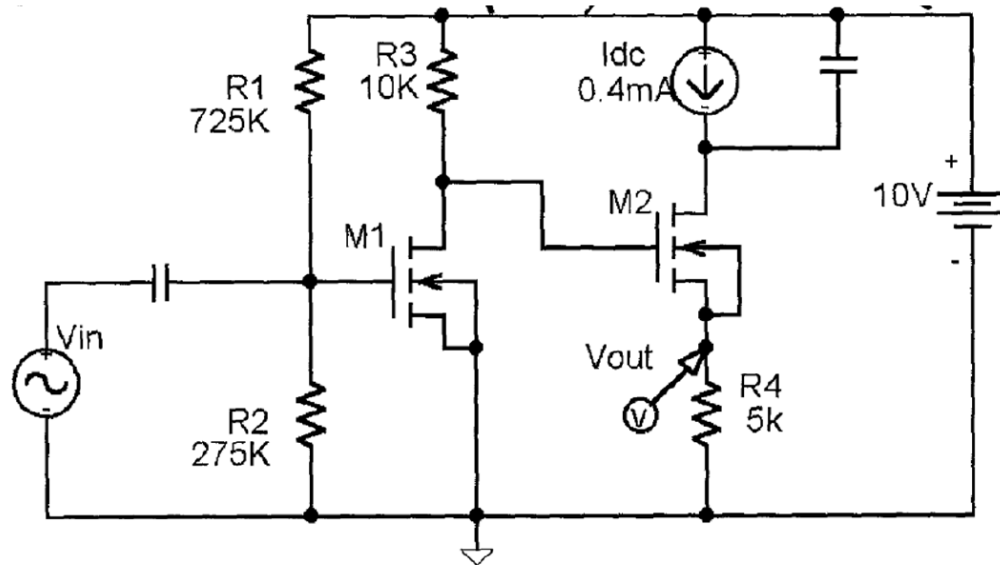
### Problem 4

For the circuit below:  $V_{TN}=1\text{ V}$ ,  $K_n=125\text{ }\mu\text{A/V}^2$ ,  $\lambda=0.1\text{ V}^{-1}$ ,  $V_{inAC} = 1\text{ mV}$  amplitude (i.e., 2m V peak to peak sinusoidal signal) at 1 KHz. M1 and M2 are nominally identical transistors



- (a) Identify the configuration for the first and the second stage.
- (b) Calculate the total small-signal voltage gain.