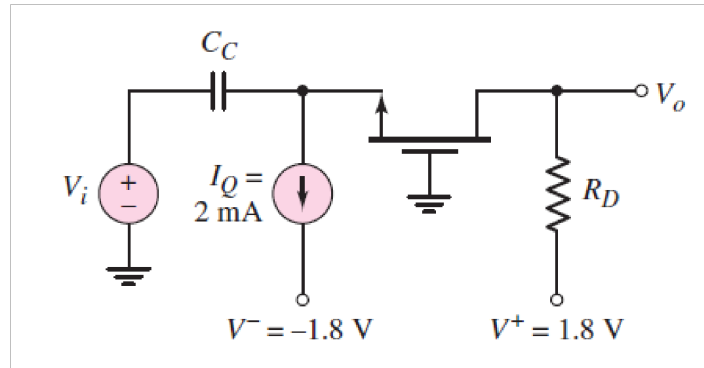


ECE322L -Homework 3 (100 points)
Assigned on Thursday, 02/13/2020-11 am
Due on Thursday, 02/20/2020-11 am

The transistor parameters of the NMOS in the figure below are $V_{TN} = 0.4 \text{ V}$, $K_n = 100 \mu\text{A/V}^2$, and $I = 0$.

- Determine R_D such that $V_{DSQ} = V_{DS(\text{sat})} + 0.25 \text{ V}$.
- Determine the transistor W/L ratio such that the total small-signal voltage gain is $A_v = 6$.
- What is the value of V_{GSQ} ?
- What are the input and the output resistance of the amplifier?
- Please, comment on the performance of the circuit below as a voltage amplifier.



$$(a) \quad V_{DSQ} = V_{out} + V_{GS} \rightarrow V_{out} = V_{DSQ} - V_{GS} \rightarrow V_{out} = \cancel{V_{GS}} - V_{TN} + 0.25 - \cancel{V_{GS}}$$

$$V_{out} = -0.4\text{V} + 0.25\text{V} = -0.15\text{V}$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{1.8\text{V} - (-0.15\text{V})}{2\text{mA}} = 975\Omega$$

$$(b) \quad A_v = g_m R_D = 6V \rightarrow g_m = \frac{6V}{975\Omega} = 6.1538 \frac{\text{mA}}{\text{V}}$$

$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{\frac{k'_n}{2} \left(\frac{W}{L}\right) I_D} \rightarrow \left(\frac{W}{L}\right) = \frac{\left(\frac{g_m}{2}\right)^2}{\frac{k'_n}{2} I_D} = 94.6745$$

$$(c) \quad I_{DQ} = K_n (V_{GS} - V_{TN})^2 \rightarrow V_{GS} = \sqrt{\frac{I_{DQ}}{K_n}} + V_{TN}$$

$$= \sqrt{\frac{2\text{mA}}{\frac{100\mu\text{A}}{\text{V}^2} \times 94.6745}} + 0.4\text{V} = 1.05\text{V}$$

David Kirby

$$(d) \ R_{in} = \frac{1}{g_m} = \frac{1}{6.1538 \frac{mA}{V}} = 162.5 \Omega$$

$$R_{out} = R_D = 975 \Omega$$

- (e) As a voltage amplifier, this circuit would not be very practical. While the gain is positive and large (good qualities), the input resistance is very low which makes for a great current buffer, but is not ideal for a voltage amplifier.