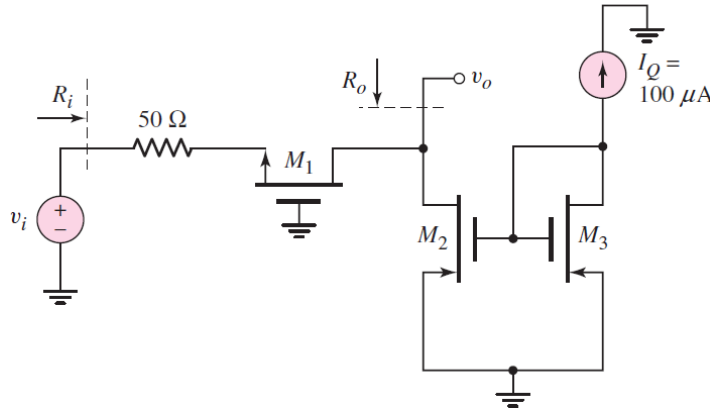


**ECE322L -Homework 4 (100 points)**  
**Assigned on Thursday, 02/20/2020-11 am**  
**Due on Thursday, 02/27/2020-11 am**

The ac equivalent circuit of a CMOS amplifier is shown below. (a) Identify the type of configuration. (b) Determine the small-signal voltage gain, the input resistance, and the output resistance.



The transistor parameters for  $M_1$  are  $V_{TN}=0.5$  V,  $k_n'=85$   $\mu\text{A}/\text{V}^2$ ,  $(W/L)_1=50$ ,  $\lambda = 0.05$   $\text{V}^{-1}$ , and for  $M_2$  and  $M_3$  are  $V_{TP}=-0.5$  V,  $k_p'=40$   $\text{mA}/\text{V}^2$ ,  $(W/L)_{2,3}=50$  and  $\lambda = 0.075$   $\text{V}^{-1}$ .

(a) Common gate

$$(b) r_{01} = \frac{1}{\lambda_1 I_D} = \frac{1}{(0.05 \text{V}^{-1})(100 \mu\text{A})} = 200 \text{k}\Omega$$

$$r_{02} = \frac{1}{\lambda_2 I_D} = \frac{1}{(0.075 \text{V}^{-1})(100 \mu\text{A})} = 133.333 \text{k}\Omega$$

$$g_{m1} = 2\sqrt{K_n I_D} = 2\sqrt{\frac{k'_n}{2} \left(\frac{W}{L}\right)_1 I_D} = 2\sqrt{\frac{85 \frac{\mu\text{A}}{\text{V}^2}}{2} (50) 100 \mu\text{A}} = 921.95 \frac{\mu\text{A}}{\text{V}}$$

$$R_{in1} = \frac{1}{g_{m1}} = \frac{1}{921.95 \frac{\mu\text{A}}{\text{V}}} = 1.0847 \text{k}\Omega$$

$$V_{GS1} = - \left( \frac{R_{in1}}{R_{in1} + R_{sig}} \right) V_{in} \rightarrow \frac{V_{GS1}}{V_{in}} = - \left( \frac{R_{in1}}{R_{in1} + R_{sig}} \right)$$

$$\frac{V_{GS1}}{V_{in}} = - \frac{1.0847 \text{k}\Omega}{1.0847 \text{k}\Omega + 50 \Omega} = - 955.94 \text{mV}$$

David Kirby

$$A_v = -g_{m1} (r_{01} \parallel r_{02}) \frac{V_{GS1}}{V_{in}} = - \left( 921.95 \frac{\mu A}{V} \right) (200k\Omega \parallel 133.33k\Omega) (-955.94mV)$$

$$A_v = 70.506 \left( \frac{V}{V} \right)$$

$$R_{in} = \frac{1}{g_m} + R_{sig} = \frac{1}{921.95 \frac{\mu A}{V}} + 50\Omega = 1.1347k\Omega$$

$$R_{out} = r_{01} \parallel r_{02} = 200k\Omega \parallel 133.33k\Omega = 80k\Omega$$