

# Memory Structures

Ramon Canal  
NCD - Master MIRI


Slides based on: Introduction to CMOS VLSI Design. D. Harris



# Outline


- Memory Arrays
- SRAM Architecture
  - SRAM Cell
  - Decoders
  - Column Circuitry
  - Multiple Ports
- Serial Access Memories

# Memory Arrays

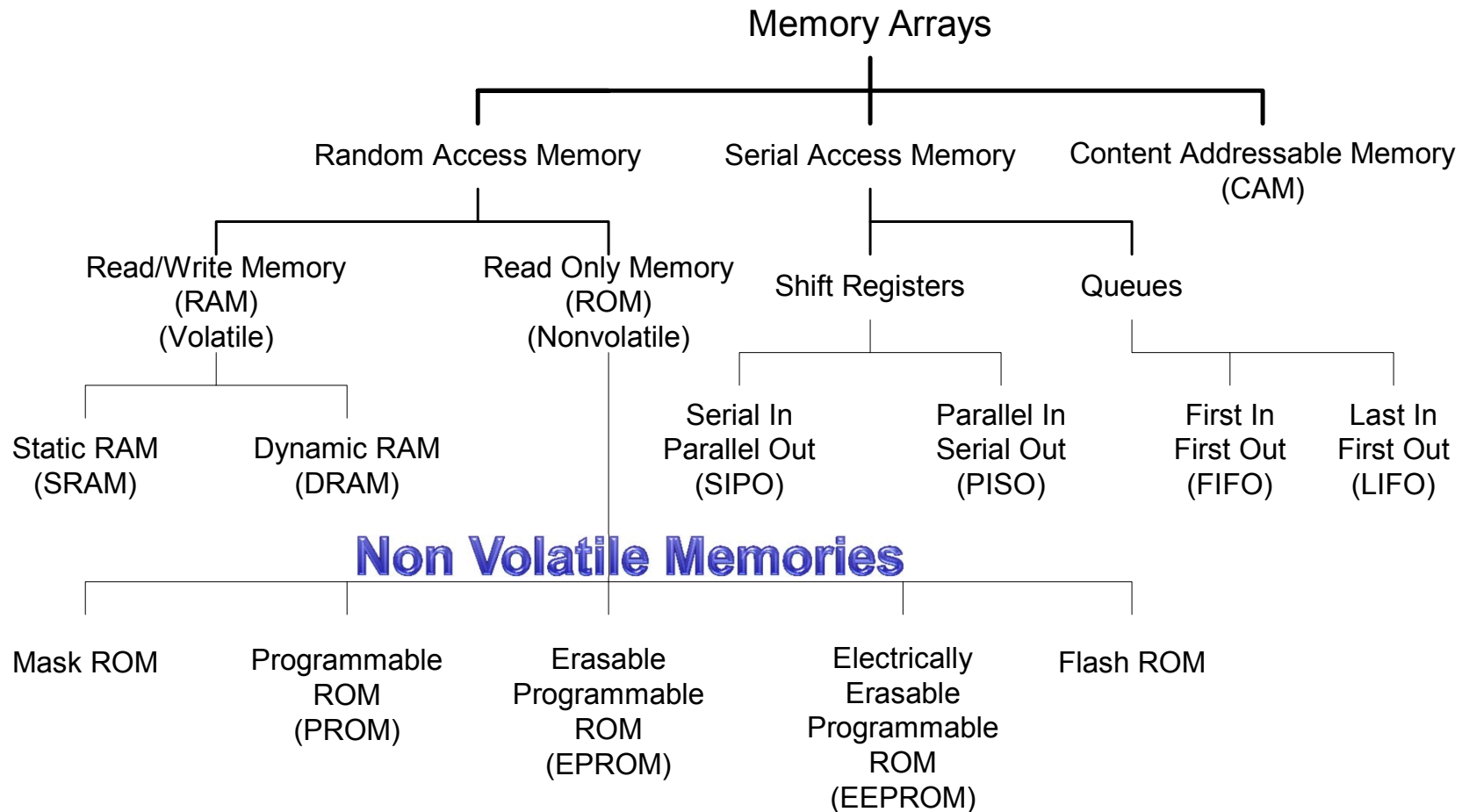
 
# Array Architecture



- $2^n$  words of  $2^m$  bits each
- If  $n \gg m$ , fold by  $2^k$  into fewer rows of more columns



- Good regularity – easy to design
- Very high density if good cells are used

  
# 12T SRAM Cell

- Basic building block: SRAM Cell
  - Holds one bit of information, like a latch
  - Must be read and written
- 12-transistor (12T) SRAM cell
  - Use a simple latch connected to bitline
  - 46 x 75  $\lambda$  unit cell




 
# 6T SRAM Cell

- Cell size accounts for most of array size
  - Reduce cell size at expense of complexity
- 6T SRAM Cell
  - Used in most commercial chips
  - Data stored in cross-coupled inverters
- Read:
  - Precharge bit, bit\_b
  - Raise wordline
- Write:
  - Drive data onto bit, bit\_b
  - Raise wordline



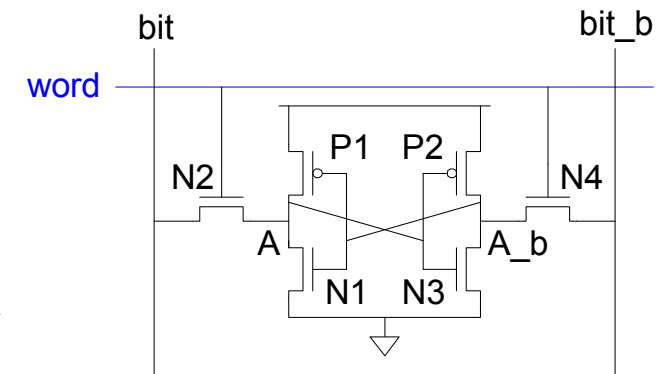
 
# SRAM Read

- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Ex:  $A = 0$ ,  $A\_b = 1$ 
  - bit discharges, bit\_b stays high
  - But A bumps up slightly
- *Read stability*
  - A must not flip


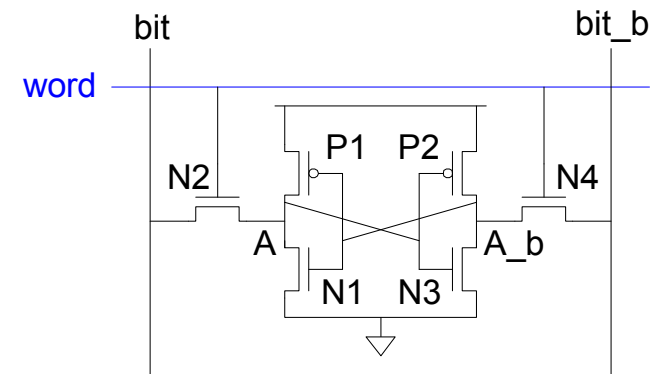 
# SRAM Read



- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Ex:  $A = 0, A_b = 1$ 
  - bit discharges, bit\_b stays high
  - But A bumps up slightly
- *Read stability*
  - A must not flip
  - $N1 \gg N2$





 
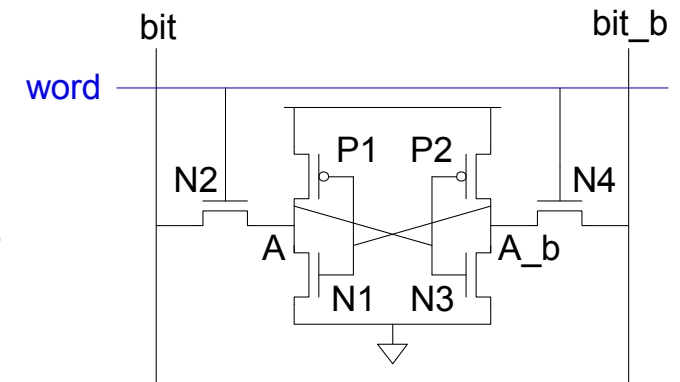
# SRAM Write

- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex:  $A = 0$ ,  $A\_b = 1$ ,  $\text{bit} = 1$ ,  $\text{bit\_b} = 0$ 
  - Force  $A\_b$  low, then  $A$  rises high
- *Writability*
  - Must overpower feedback inverter



 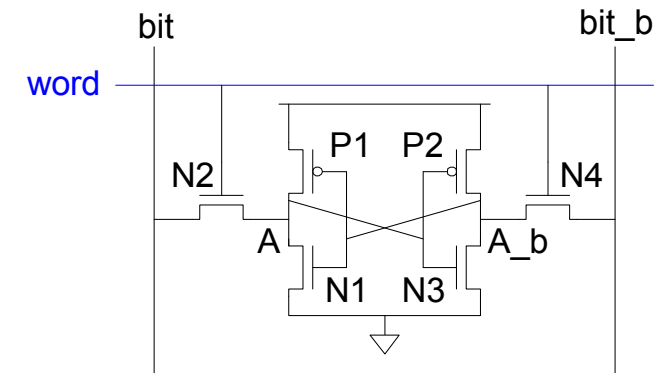
# SRAM Write

- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex:  $A = 0$ ,  $A\_b = 1$ ,  $\text{bit} = 1$ ,  $\text{bit\_b} = 0$ 
  - Force  $A\_b$  low, then  $A$  rises high
- *Writability*
  - Must overpower feedback inverter
  - $N2 \gg P1$



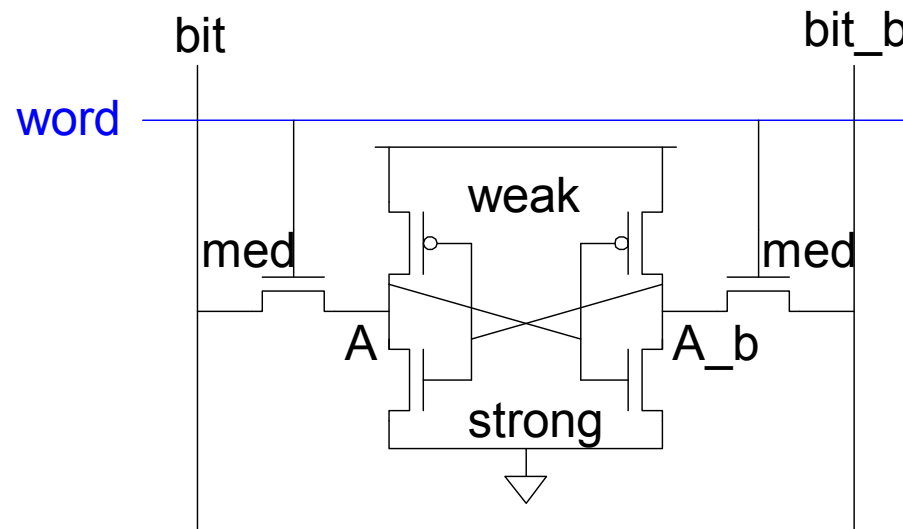
# SRAM Sizing

- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell




# SRAM Column Example

## Read



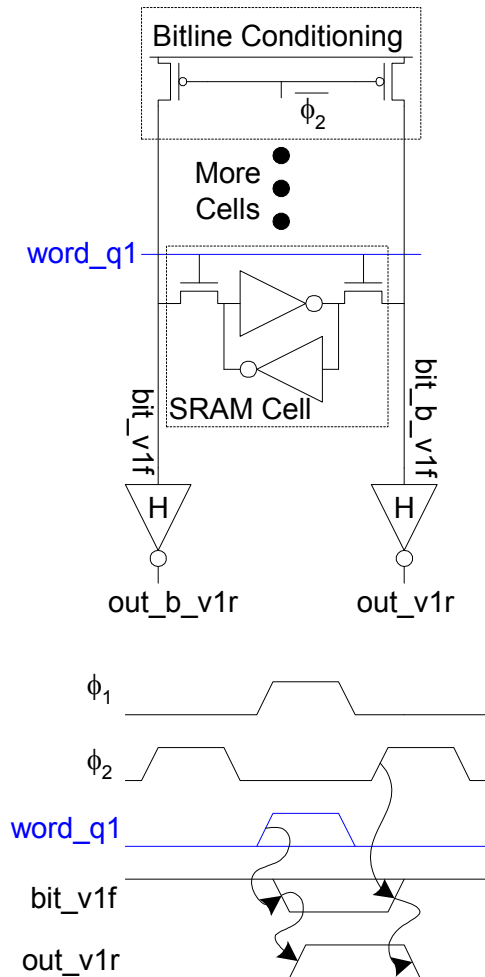


## Write

 
   
# SRAM Layout

- Cell size is critical:  $26 \times 45 \lambda$  (even smaller in industry)
- Tile cells sharing  $V_{DD}$ , GND, bitline contacts




# Periphery

- ❑ **Decoders**
- ❑ **Sense Amplifiers**
- ❑ **Input/Output Buffers**
- ❑ **Control / Timing Circuitry**


# Decoders

- $n:2^n$  decoder consists of  $2^n$   $n$ -input AND gates
  - One needed for each row of memory
  - Build AND from NAND or NOR gates

## Static CMOS

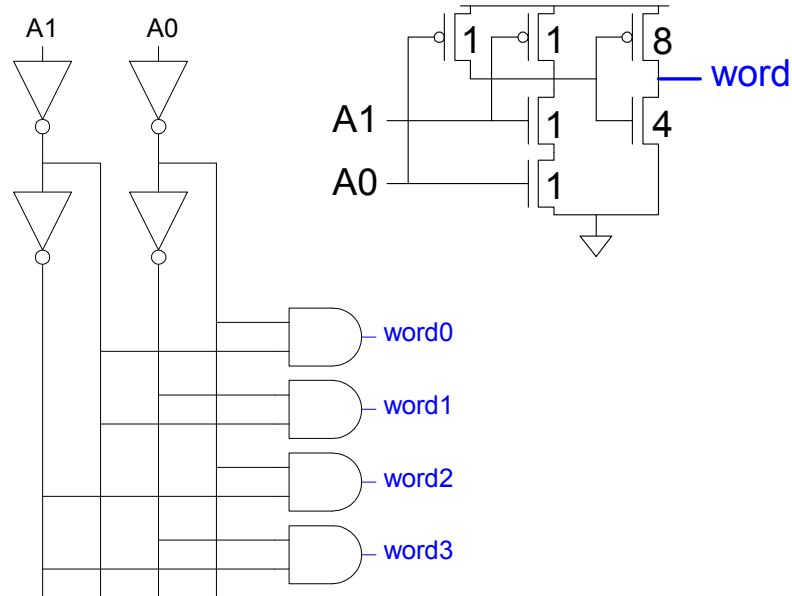


## Pseudo-nMOS

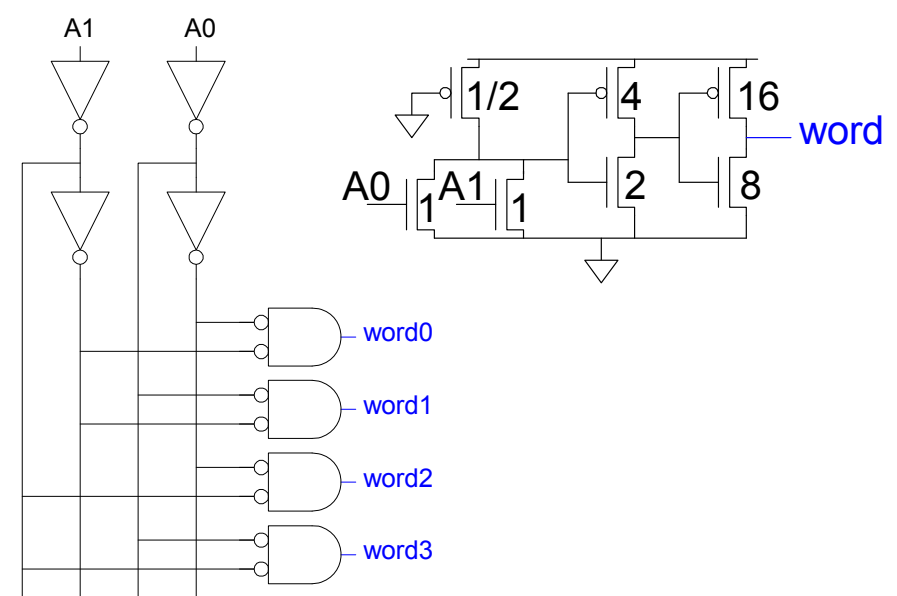
 
# Decoder Layout


- Decoders must be pitch-matched to SRAM cell
  - Requires very skinny gates





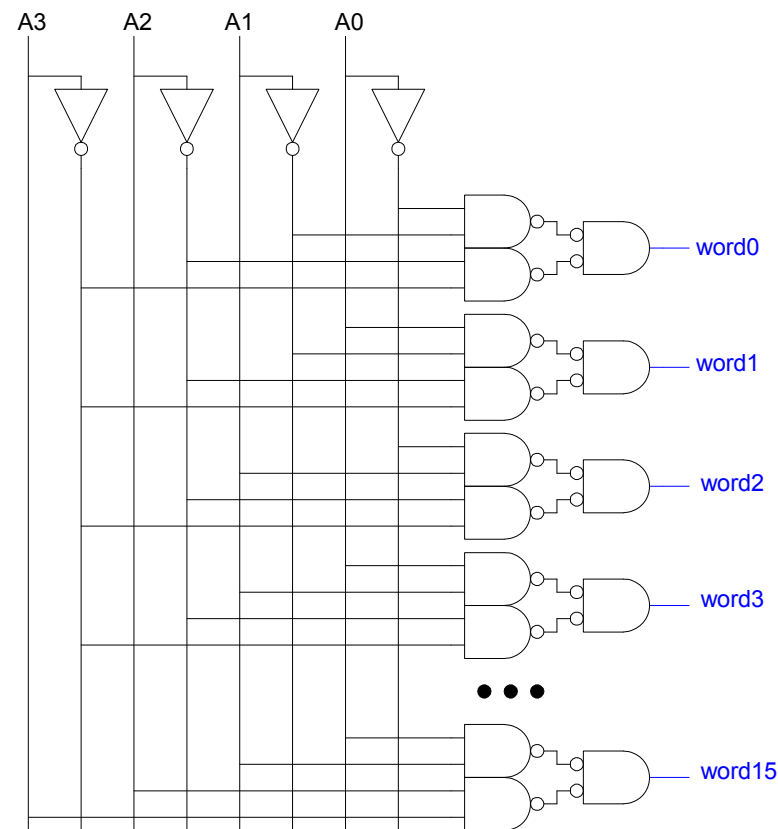
# Large Decoders

- For  $n > 4$ , NAND gates become slow
  - Break large gates into multiple smaller gates


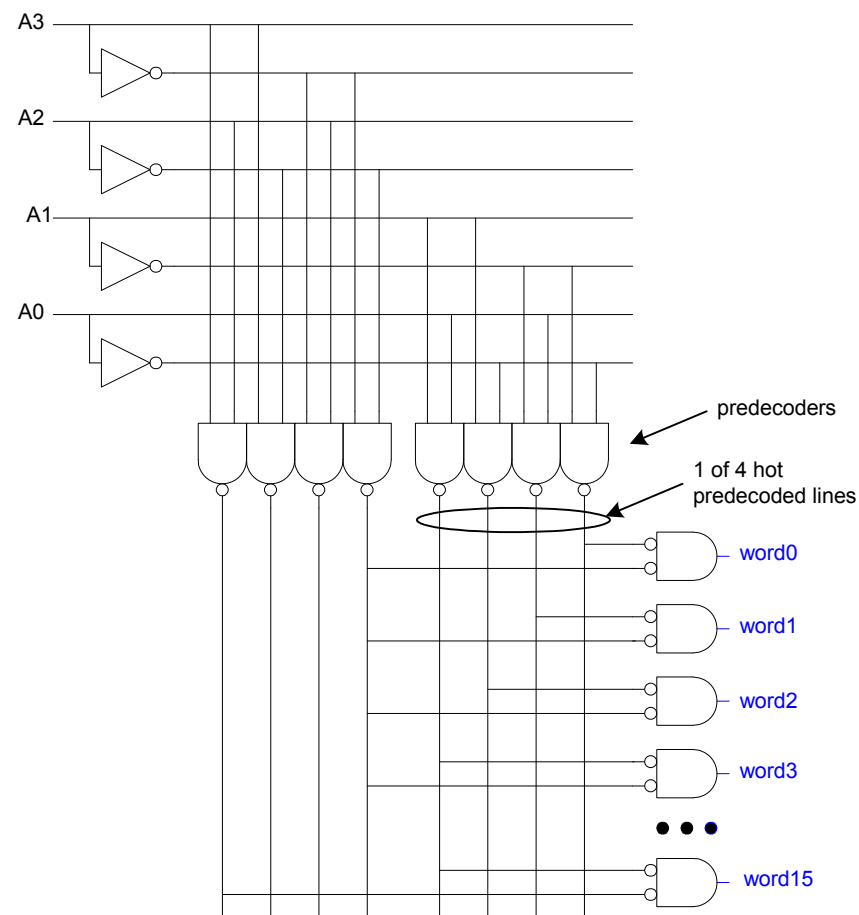
# Predecoding

- Many of these gates are redundant
  - Factor out common gates into predecoder
  - Saves area
  - Same path effort



# Periphery

- ❑ Decoders
- ❑ **Sense Amplifiers**
- ❑ Input/Output Buffers
- ❑ Control / Timing Circuitry

# Sense Amplifiers


$$t_p = \frac{C \cdot \Delta V}{I_{av}}$$

make  $\Delta V$  as small as possible

large

small

**Idea: Use Sense Amplifier**

 


# Sense Amplifiers

- Bitlines have many cells attached
  - Ex: 32-kbit SRAM has 256 rows x 128 cols
  - 128 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$ 
  - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
  - Discharged slowly through small transistors (small I)
- *Sense amplifiers* are triggered on small voltage swing (reduce  $\Delta V$ )

 
# Differential Pair Amp

- Differential pair requires no clock
- But always dissipates static power


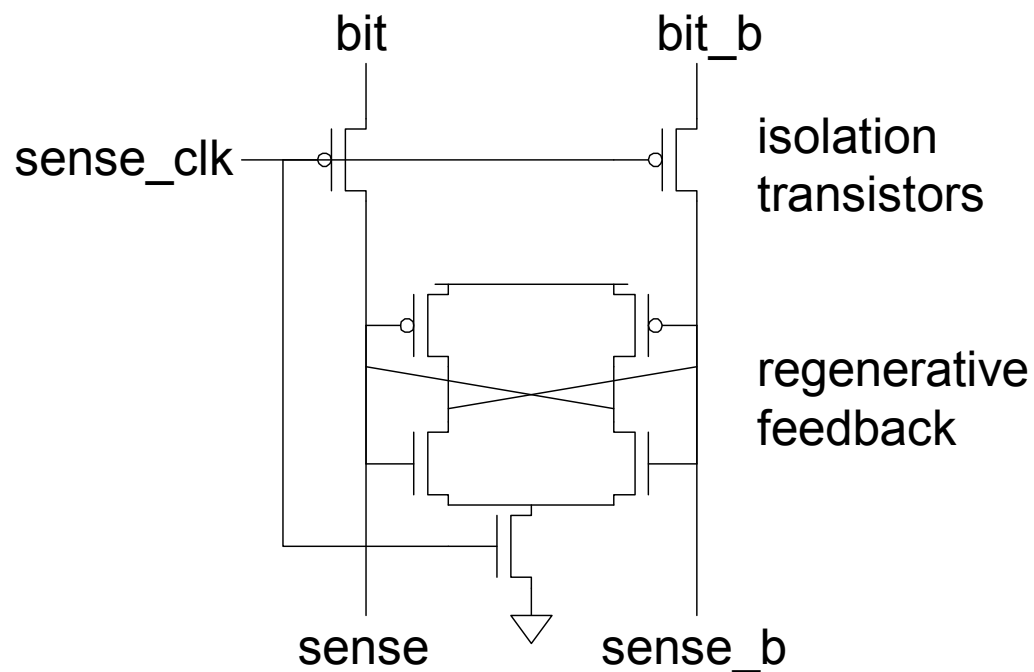
# Clocked Sense Amp

- Clocked sense amp saves power
- Requires sense\_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance



# Periphery

- ❑ Decoders
- ❑ Sense Amplifiers
- ❑ Input/Output Buffers
- ❑ **Control / Timing Circuitry**




# Column Circuitry


- Some circuitry is required for each column
  - Bitline conditioning
  - Column multiplexing

# Bitline Conditioning

- Precharge bitlines high before reads

 


 - Equalize bitlines to minimize voltage difference when using sense amplifiers


 
# Twisted Bitlines

- Sense amplifiers also amplify noise
  - Coupling noise is severe in modern processes
  - Try to couple equally onto bit and bit\_b
  - Done by *twisting* bitlines




# Column Multiplexing

- Recall that array may be folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
  - Must select 16 output bits from the 128 columns
  - Requires 16 8:1 column multiplexers

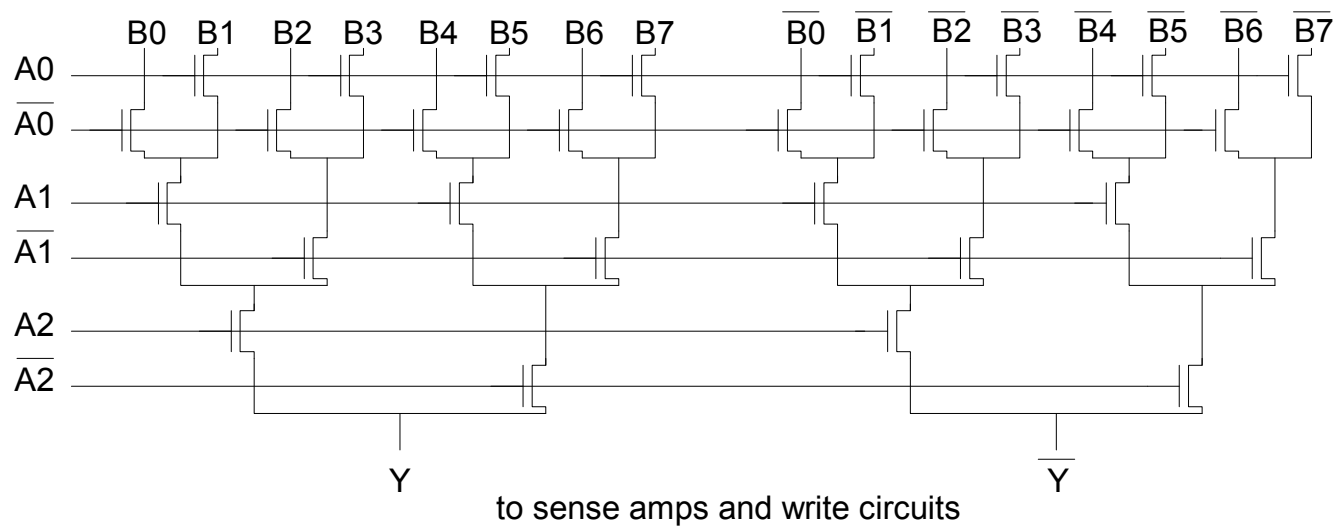
# Tree Decoder Mux

- Column mux can use pass transistors
  - Use nMOS only, precharge outputs
- One design is to use k series transistors for  $2^k:1$  mux
  - No external decoder logic needed



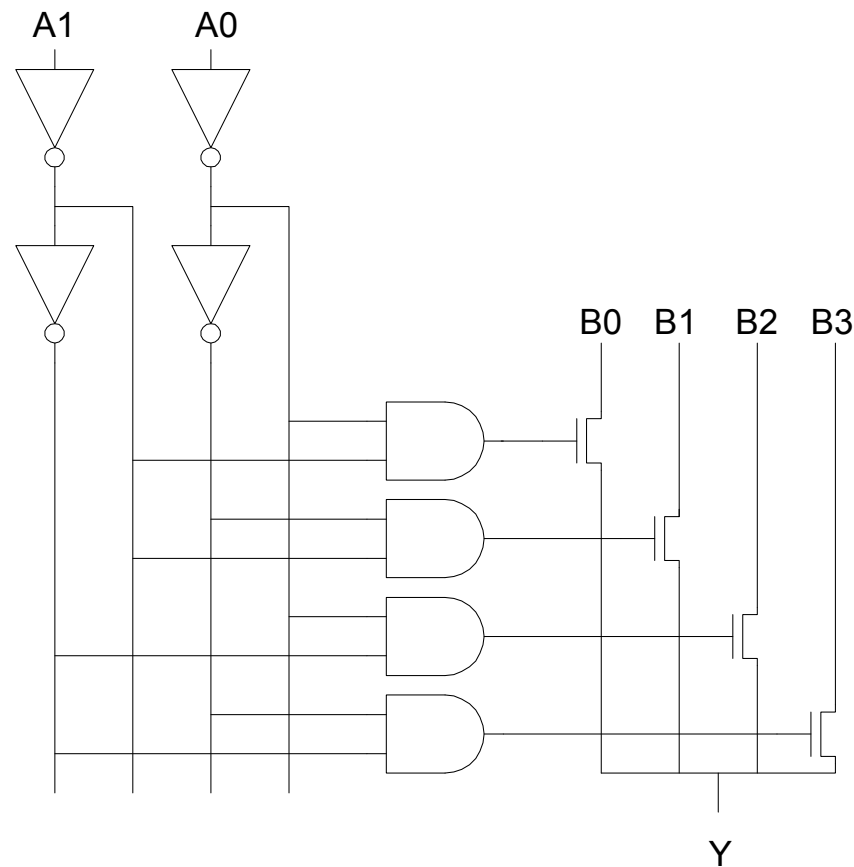
# Single Pass-Gate Mux

- Or eliminate series transistors with separate decoder



# Ex: 2-way Muxed SRAM

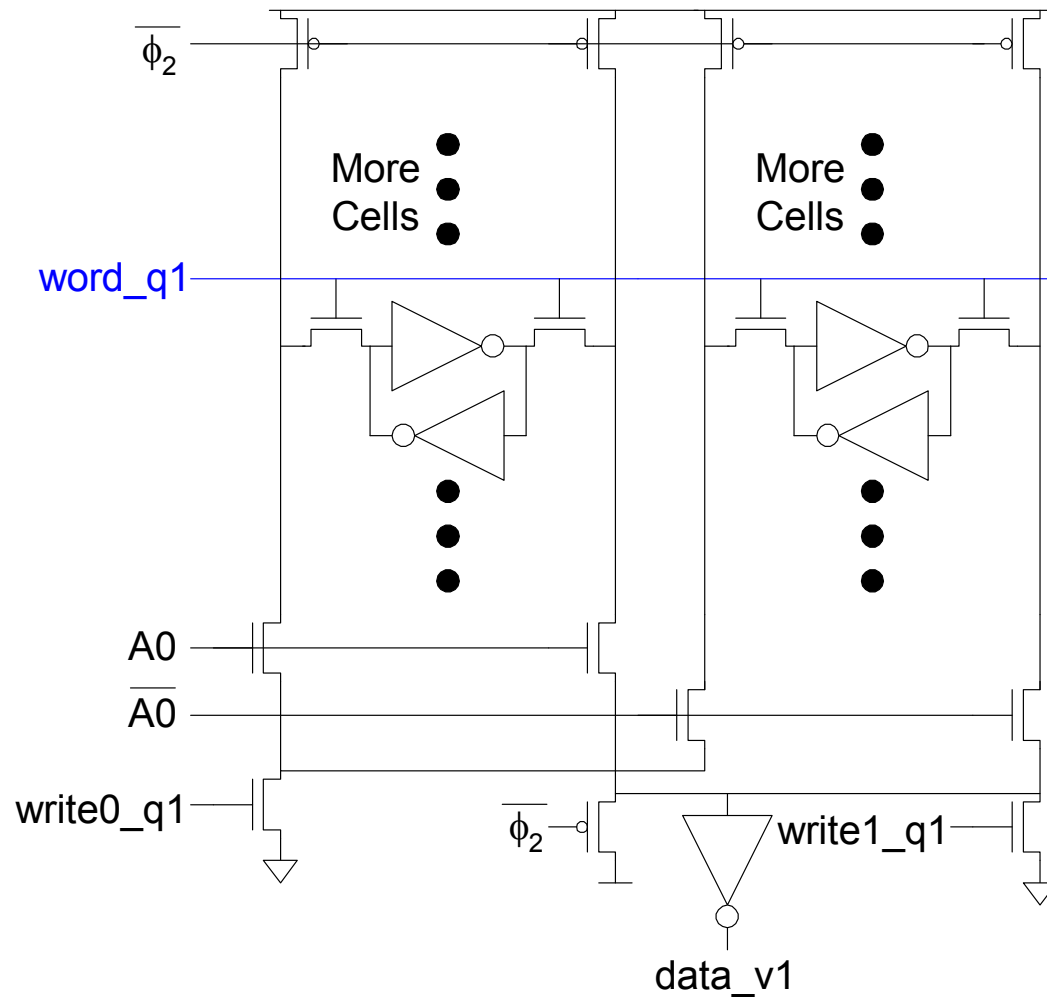

# Memory configuratons

- ❑ **Multiported memories**
- ❑ CAM Memories
- ❑ Serial Access, Queues




# Multiple Ports

- We have considered single-ported SRAM
  - One read or one write on each cycle
- *Multiported* SRAM are needed for register files
- Examples:
  - Multicycle processor must read two sources or write a result on some cycles
  - Pipelined processor must read two sources and write a third result each cycle
  - Superscalar processor must read and write many sources and results each cycle
 
# Dual-Ported SRAM


- Simple dual-ported SRAM
  - Two independent single-ended reads
  - Or one differential write



- Do two reads and one write by time multiplexing
  - Read during ph1, write during ph2
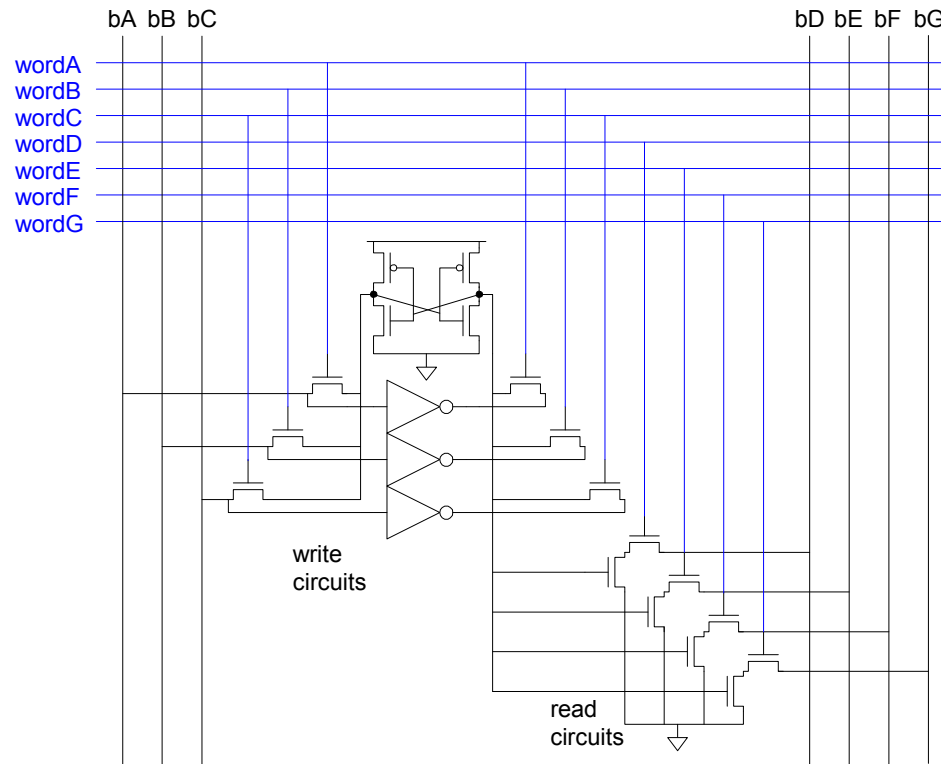
# Multi-Ported SRAM


- Adding more access transistors hurts read stability
- Multiported SRAM isolates reads from state node
- Single-ended design minimizes number of bitlines



# Memory configuratons

- ❑ Multiported memories
- ❑ **CAM Memories**
- ❑ Serial Access, Queues

# Contents-Addressable Memory

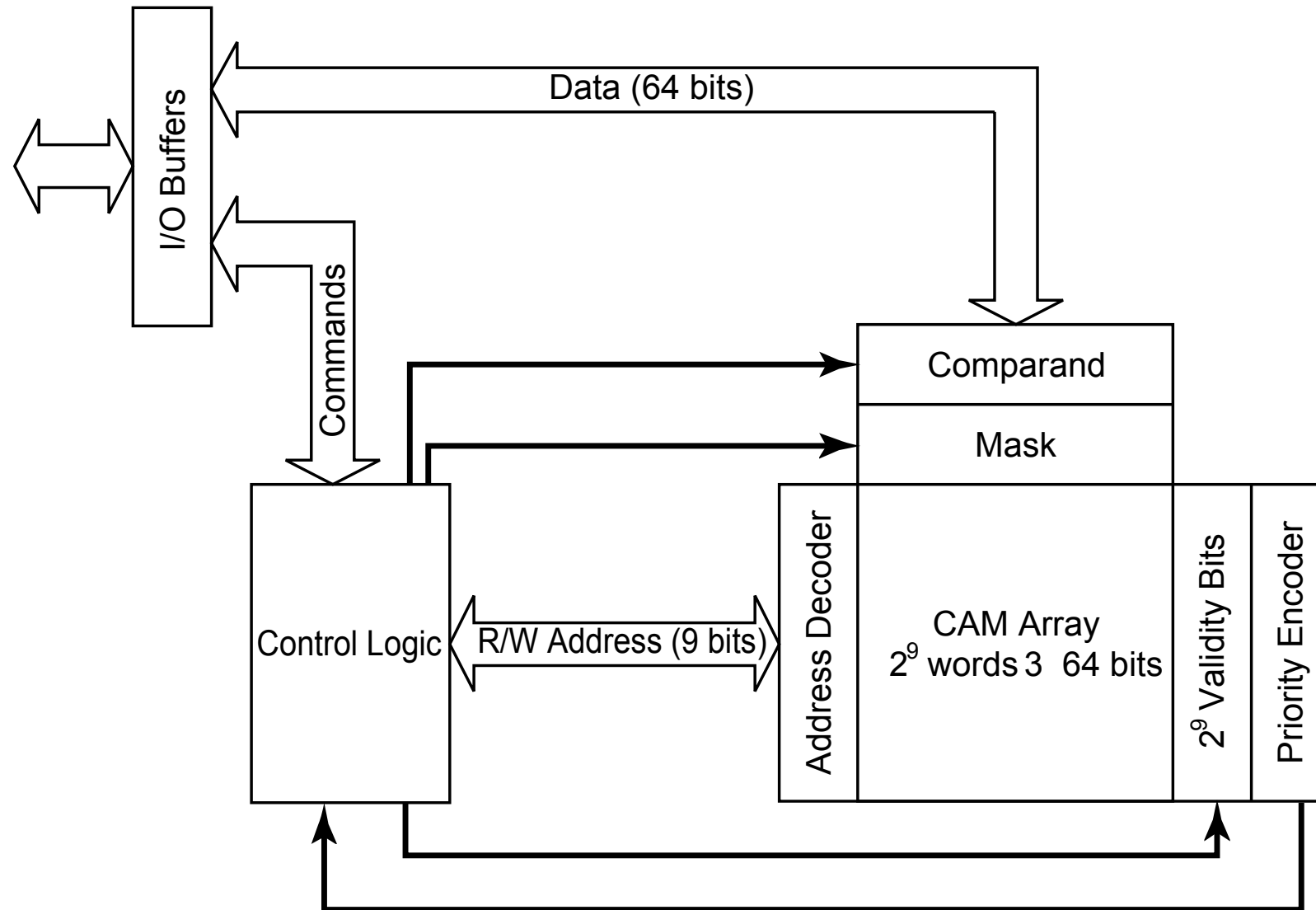

# Memory configuratons


- ❑ Multiported memories
- ❑ CAM Memories
- ❑ **Serial Access, Queues**

# Serial Access Memories

- Serial access memories do not use an address
  - Shift Registers
  - Tapped Delay Lines
  - Serial In Parallel Out (SIPO)
  - Parallel In Serial Out (PISO)
  - Queues (FIFO, LIFO)
 
# Shift Register


- *Shift registers* store and delay data
- Simple design: cascade of registers
  - Watch your hold times!





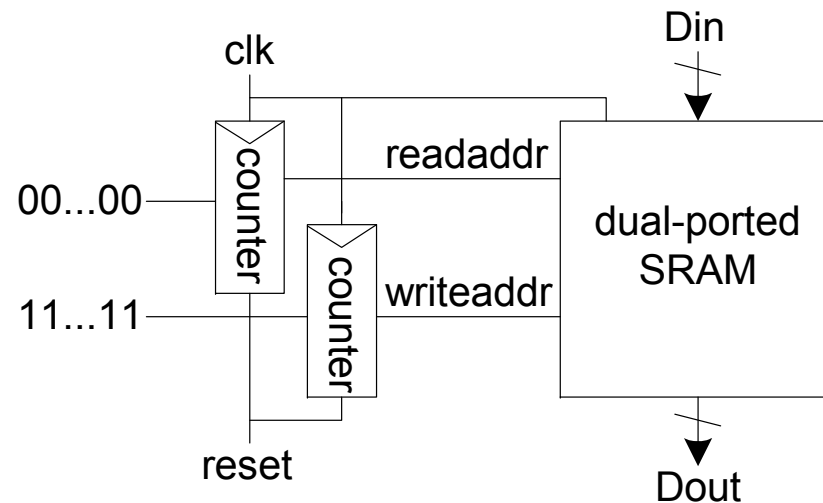
# Denser Shift Registers

- Flip-flops aren't very area-efficient
- For large shift registers, keep data in SRAM instead
- Move read/write pointers to RAM rather than data
  - Initialize read address to first entry, write to last
  - Increment address on each cycle



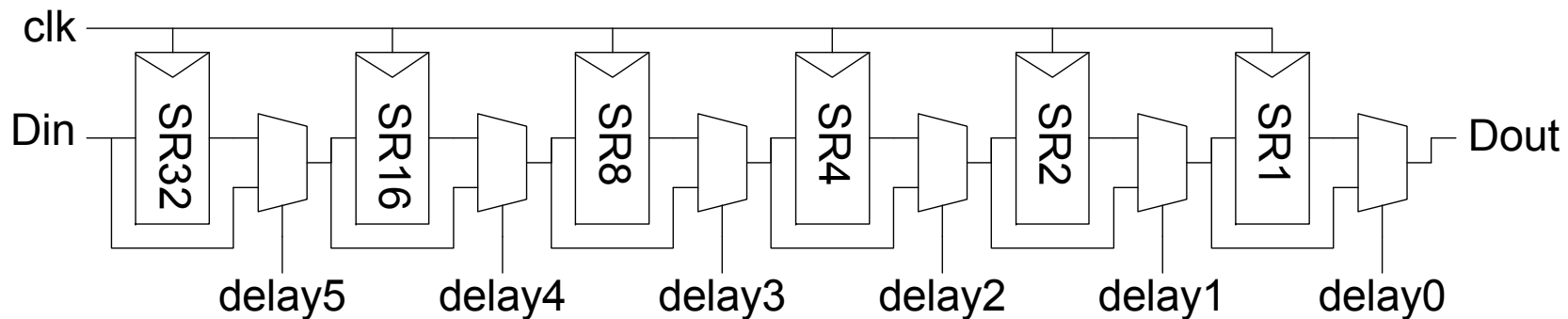
# Tapped Delay Line

- A *tapped delay line* is a shift register with a programmable number of stages
- Set number of stages with delay controls to mux
  - Ex: 0 – 63 stages of delay



 
# Serial In Parallel Out

- 1-bit shift register reads in serial data
  - After N steps, presents N-bit parallel output



 
# Parallel In Serial Out

- Load all N bits in parallel when shift = 0
  - Then shift one bit out per cycle


 
# Queues

- *Queues* allow data to be read and written at different rates.
- Read and write each use their own clock, data
- Queue indicates whether it is full or empty
- Build with SRAM and read/write counters (pointers)





# FIFO, LIFO Queues

- *First In First Out* (FIFO)
  - Initialize read and write pointers to first element
  - Queue is EMPTY
  - On write, increment write pointer
  - If write almost catches read, Queue is FULL
  - On read, increment read pointer
- *Last In First Out* (LIFO)
  - Also called a *stack*
  - Use a single *stack pointer* for read and write

# Other considerations

- ☐ Leakage control
- ☐ Redundancy
- ☐ Flash Memories

# Suppressing Leakage in SRAM

 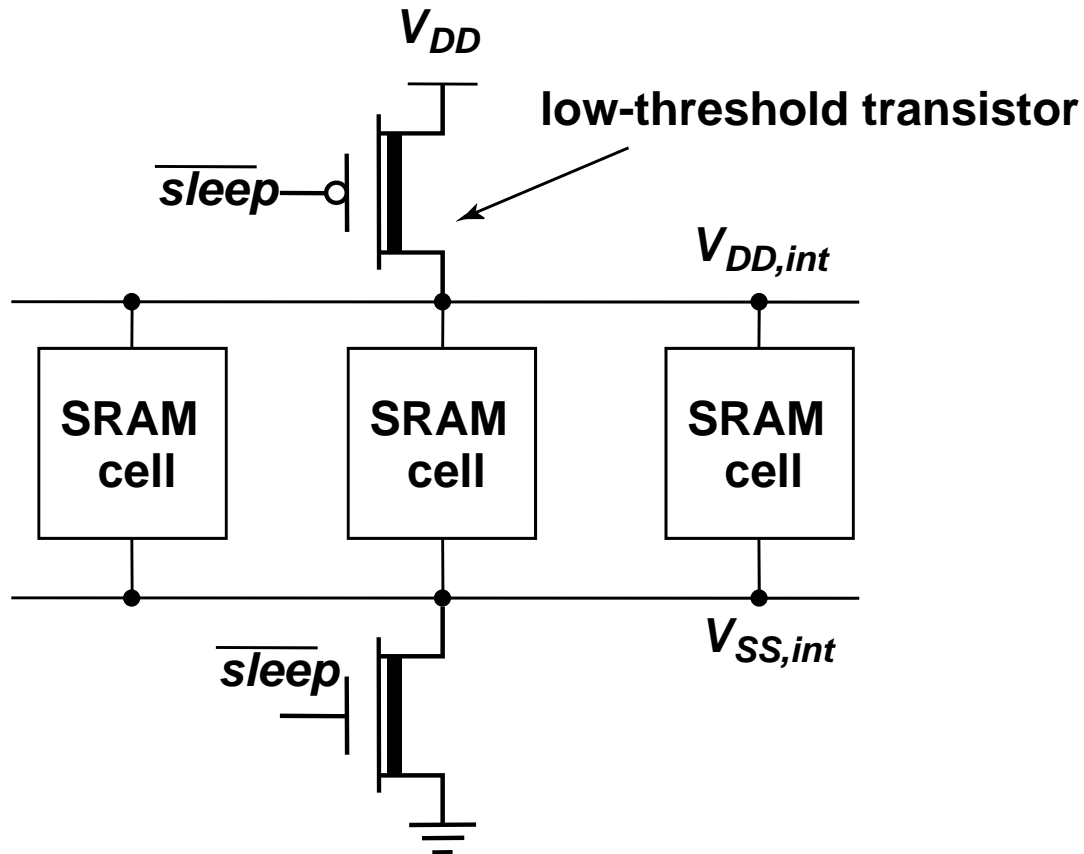

*Inserting Extra Resistance*


*Reducing the supply voltage*



# Other considerations

- ☐ Leakage control
- ☐ **Redundancy**
- ☐ Flash Memories

# Redundancy

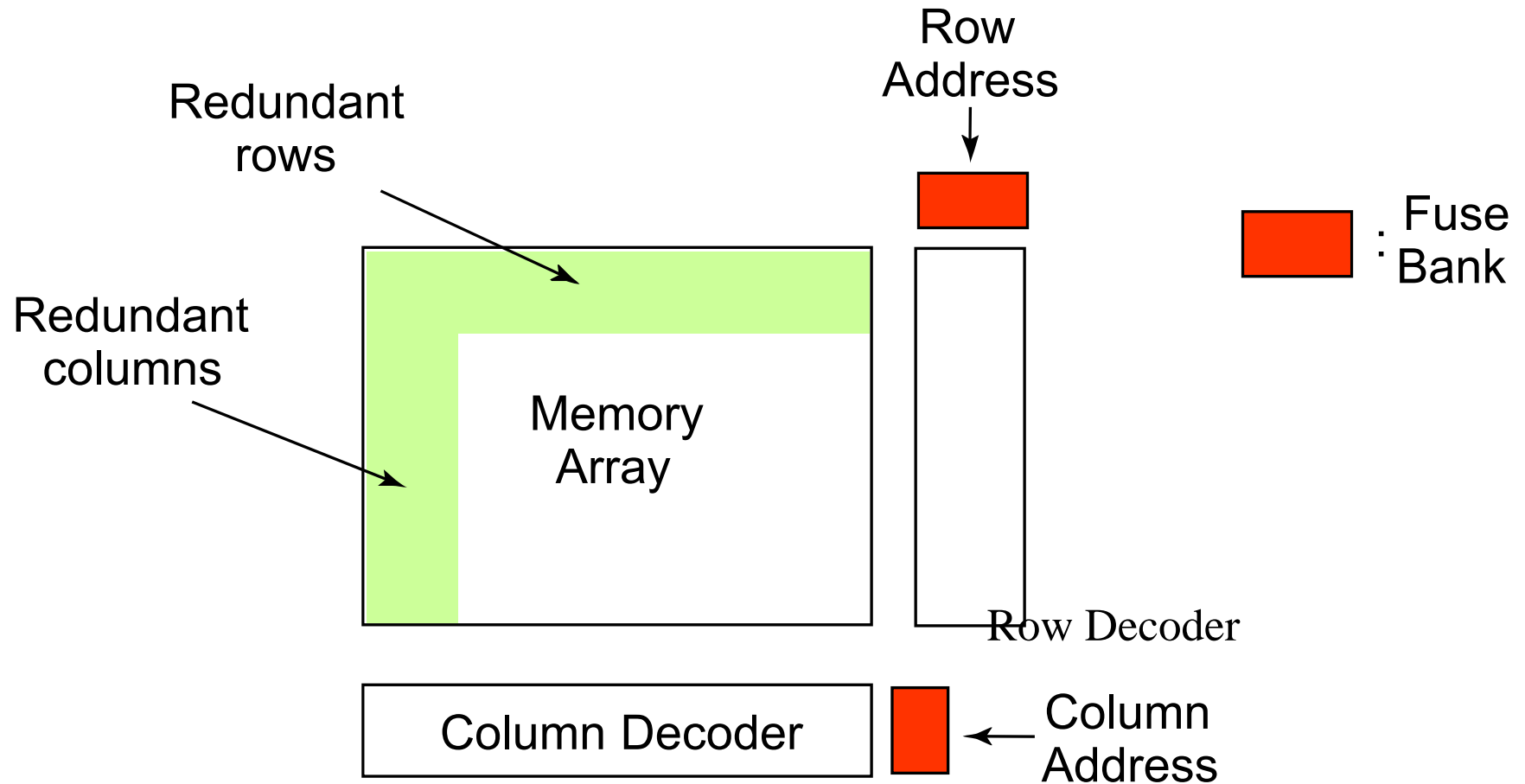

# Error-Correcting Codes

## Example: Hamming Codes

$P_1 P_2 B_3 P_4 B_5 B_6 B_7$

*e.g. B3 Wrong*

*with*

$$P_1 \oplus B_3 \oplus B_5 \oplus B_7 = 0$$

1

$$P_2 \oplus B_3 \oplus B_6 \oplus B_7 = 0$$


1

= 3

$$P_4 \oplus B_5 \oplus B_6 \oplus B_7 = 0$$

0


# Redundancy and Error Correction

 

# Other considerations

- ☐ Leakage control
- ☐ Redundancy
- ☐ **Flash Memories**


# Flash EEPROM

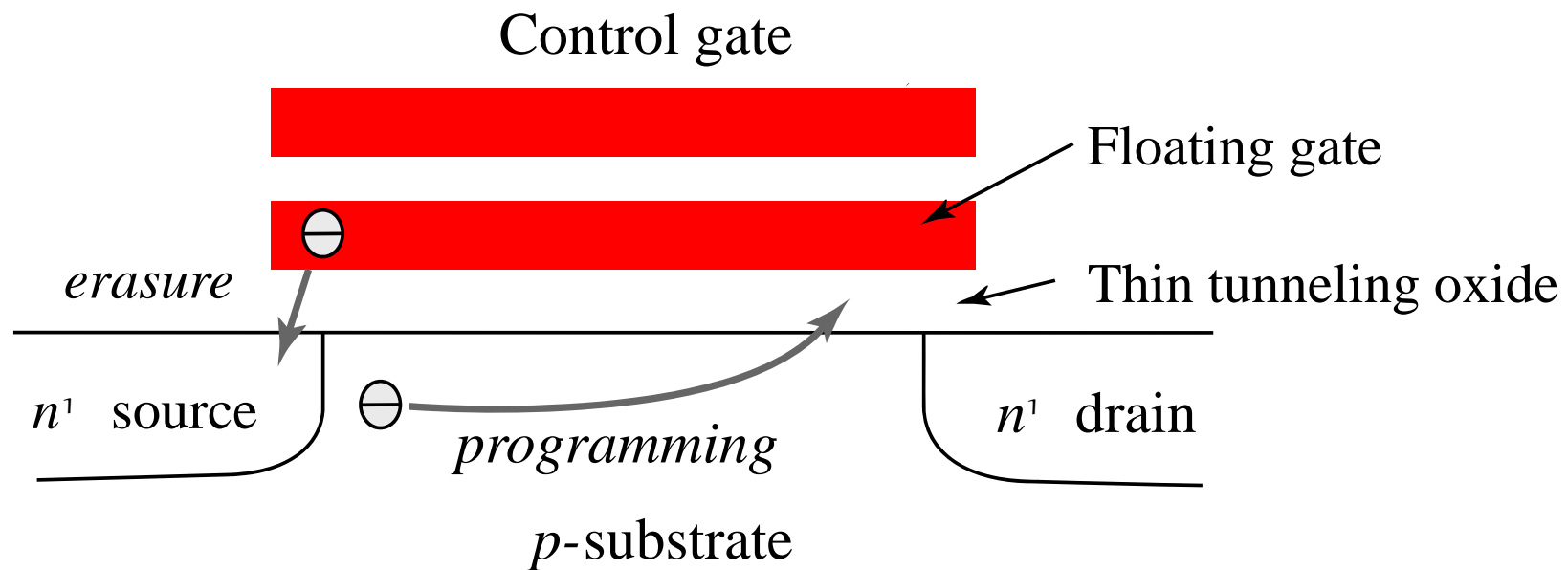

**Many other options ...**



# Cross-sections of NVM cells

 

**Flash**

**EPROM**





Departament d'Arquitectura  
de Computadors

UNIVERSITAT POLITÈCNICA DE CATALUNYA



NCD - Master MIRI  
*Courtesy Intel*
  
# Basic Operations in a NOR Flash Memory— Erase






  
# Basic Operations in a NOR Flash Memory— Write



# Basic Operations in a NOR Flash Memory—

## Read

  

# Conclusions

## Memory Structure:

