
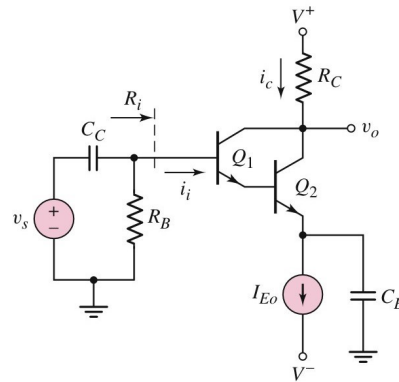


ECE322L -Homework 8 (100 points)
Assigned on Thursday, 03/26/2020-11 am
Due on Thursday, 04/09/2020-11 am

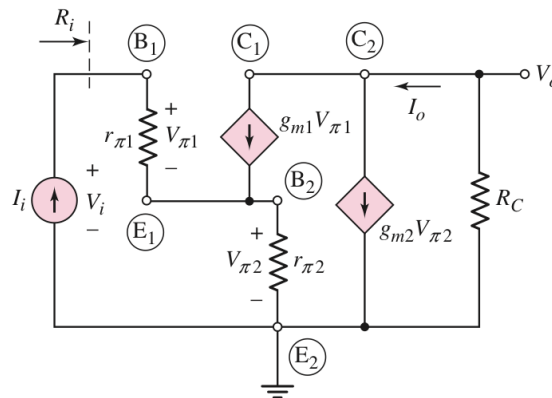Calculate the output resistance of the amplifier below. Note that V_A is infinite for Q_1 and Q_2 . What application would be most advantageous to use the amplifier below for? Justify your answer.



This is a Darlington pair configuration that provides larger current gain which are typically used in switches and delays.



From the small-signal equivalent circuit, we see that $g_{m1} V_{\pi1} = g_{m1} r_{\pi1} I_{in} = \beta_1 I_{in}$ and the output current is

$I_{out} = g_{m1} V_{\pi1} + g_{m2} V_{\pi2}$. This gives us an overall current gain of $A_i = \frac{I_{out}}{I_{in}} \approx \beta_1 \beta_2$ and means our output

resistance is simply $R_{out} = R_C$.