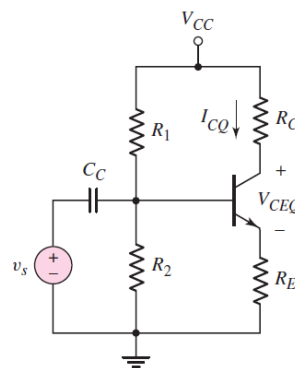


**ECE322L -Homework 7 (100 points)**  
**Assigned on Thursday, 03/12/2020-11 am**  
**Due on Thursday, 03/26/2020-11 am**

The figure below shows a common emitter amplifier configuration.

- (a) Provide an expression for the maximum  $v_{ce}-v_{be}$  gain of the amplifier with the BJT still remaining in the forward active region.
- (b) Discuss the possible trade-off strategies to select the Thevenin equivalent voltage seen looking from the base of the transistor into the  $R_1$ ,  $R_2$  voltage divider.
- (c) Specify the role of the capacitor  $C_C$ .
- (d) Discuss the possible trade-off strategies to select the resistor  $R_E$ .



- (a) Assuming the BJT remains in forward-active region, therefore  $I_E = (1 + \beta) I_B$

$$A_V = \frac{V_{out}}{V_s} = \frac{-(\beta I_b)R_C}{V_s} = -\beta R_C \left( \frac{V_{in}}{R_{ib}} \right) \times \left( \frac{1}{V_s} \right)$$

- (b) The trade-offs of using  $V_{TH}$  are that these assumptions must be true:

$$R_{TH} \ll (1 + \beta)R_E, \beta \gg 1, \text{ and } \frac{\beta}{(1 + \beta)} \cong 1.$$

$$\text{These assumptions allow us to say } V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC}.$$

- (c) The coupling capacitor  $C_C$  acts as an open circuit to dc, isolating the signal source from the dc base current. The dc transistor biasing is then established by  $R_1$  and  $R_2$ , and is not disturbed when the source signal is coupled.
- (d) Including an emitter resistor provides stability in the Q-point, but reduces the small-signal voltage gain significantly.