

# Lecture 20 Problem - Maximum undistorted power.

①

$$\overline{P}_{RL} = V_{rms} I_{rms} = \frac{1}{\sqrt{2}} V_p \cdot \frac{1}{\sqrt{2}} I_p = \frac{1}{2} \cdot \frac{V_p^2}{R_L} \quad V_p: \text{Peak value of the ac signal}$$

The maximum undistorted power transferred to a load is the average power transferred to a load when the signal across the load is undistorted.


The maximum undistorted signal can be calculated using the cut-off and the saturation limit and selecting the minimum value between the 2.

$$V_p = \frac{V_{PP}}{2} = 2 I_{CQ} r_c \quad (\text{cut-off limit})$$

$$V_p = \frac{V_{PP}}{2} = 2 V_{CEQ} \quad (\text{saturation limit})$$

In order to determine  $V_p$  we need to calculate

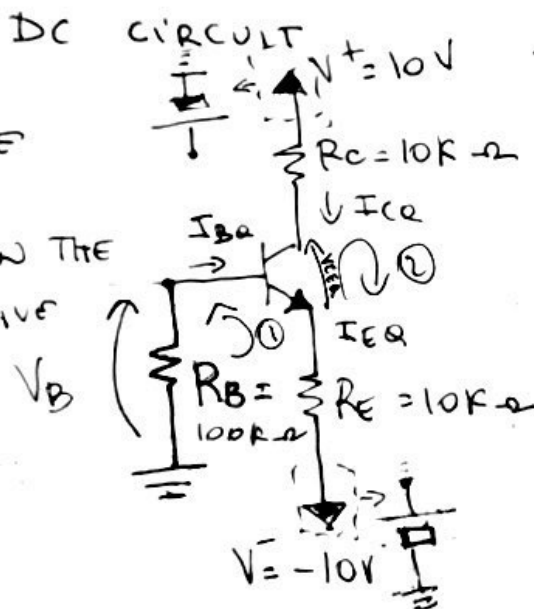$I_{CQ}$ ,  $V_{CEQ}$ , and  $r_c$  (the inverse of the slope of the ac load line).



$$KVL @ \textcircled{1} \quad -R_B I_{BQ} - V_{BE(on)} - R_E I_{EQ} - V^- = 0$$

$$I_{BQ} = - \frac{V^- + V_{BE(on)}}{R_B + (\beta + 1) R_E} =$$

$$= \frac{-V^- - V_{BE(on)}}{R_B + \beta + 1 R_E} =$$

$$= \frac{10 - 0.7}{100 + 101 \cdot 10} = 0.00838 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 0.838 \text{ mA} \quad I_{EQ} = 0.846 \text{ mA}$$


$$KVL @ \textcircled{2} \quad V^- + R_E I_{EQ} + V_{CEQ} + R_C I_{CQ} - V^+ = 0$$

$$-20 + 10 \cdot 0.864 + V_{CEQ} + 10 \cdot 0.838 = 0$$

$$V_{CEQ} = 3.16 \text{ V} > V_{CE,sat} = 0.2 \text{ V}$$


The assumption of the BJT being in F.A region is verified

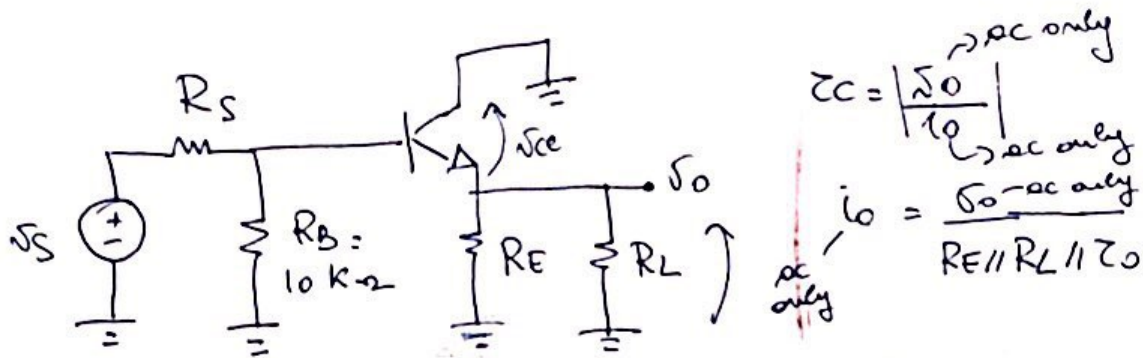Next step is to determine  $r_c$ . In order to do that, we need to sketch the AC circuit. (2)



$$Z_c = \frac{v_o}{i_o} \quad \text{ac only}$$
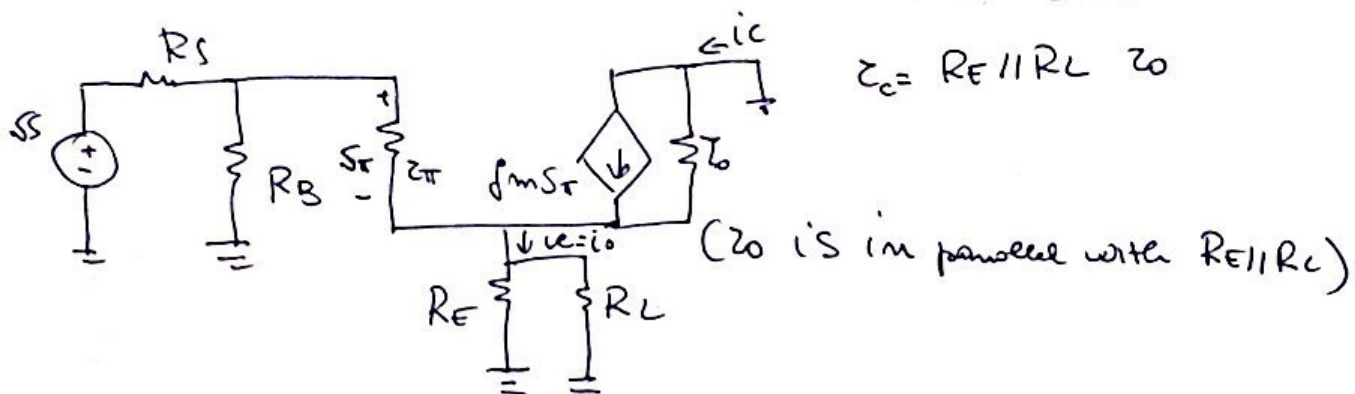
$$i_o = \frac{v_o - v_{ce}}{R_E \parallel R_L \parallel Z_o} \quad \text{ac only}$$




$$Z_c = R_E \parallel R_L \parallel Z_o$$

( $Z_o$  is in parallel with  $R_E \parallel R_L$ )

$$Z_o = \frac{100}{0.838} = 11.9\text{ k}\Omega$$

$$Z_{c1\text{ k}\Omega} = 0.502\text{ k}\Omega$$
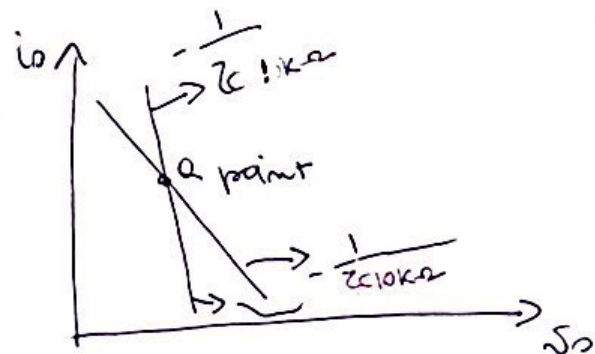
$$Z_{c10\text{ k}\Omega} = 4.8\text{ k}\Omega$$



$$V_p = \frac{V_{ce}}{2} = \frac{2 \cdot 3.16}{2} = 3.16\text{ V (saturation limit)}$$

$$V_p = \frac{V_{ce}}{2} = \frac{2 \cdot 3.16}{2} = 3.16\text{ V (saturation limit)}$$

$$\overline{P}_{RL=1\text{ k}\Omega} = \frac{1}{2} \frac{(0.756)^2}{1\text{ k}\Omega} = 0.286\text{ mW}$$

$$R_L = 10 \text{ k}\Omega$$

(3)

$$V_p = \frac{V_{pp}}{2} = 4.8 \text{ k} \cdot 0.838 \text{ m} = 4.02 \text{ V (Sat. limit)}$$

$$V_p = \frac{V_{pp}}{2} = 3.16 \text{ V (Cut-off limit)} \leftarrow$$

$$\overline{P_{RL}} = \frac{1}{2} \frac{(3.16)^2}{10 \text{ k}} = 0.499 \text{ mW}$$

$$\overline{P_{RL=1 \text{ k}\Omega}} = 0.286 \text{ mW} ; \overline{P_{RL=10 \text{ k}\Omega}} = 0.499 \text{ mW}$$

None understood power can be transferred to a higher load.  
 This could be immediately understood by looking at the ac load lines in the two cases. For the higher load, the ac load line has a lower slope which yields a larger voltage swing.