

# PROBLEM 1

$$S_{out-oe} = G_V \cdot S_{in-oe}$$

(1)

$$S_{out-ole} = S_{out-oe} + V_c$$

↳ COLLECTOR VOLTAGE OR VOLTAGE BETWEEN THE COLLECTOR AND GROUND.

$$G_V = ?$$

In order to calculate  $G_V$  we need to determine the small-signal parameters  $\tau_{\pi}$ ,  $\tau_{\mu}$ , and  $\mu_{tr}$ .

$$\tau_{\pi} = \frac{\beta}{\mu_{tr}} \quad \mu_{tr} = \frac{I_e}{V_t}$$




$$V_t = 0.025 V (300 K)$$

$$\tau_o = \frac{V_A + V_{EC}}{I_e}$$

Therefore, we need to determine the Q point of the transistor.
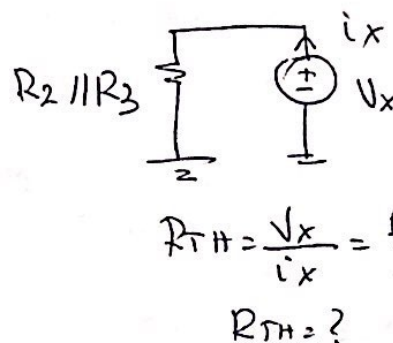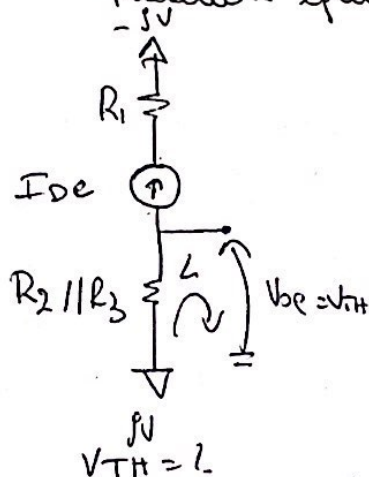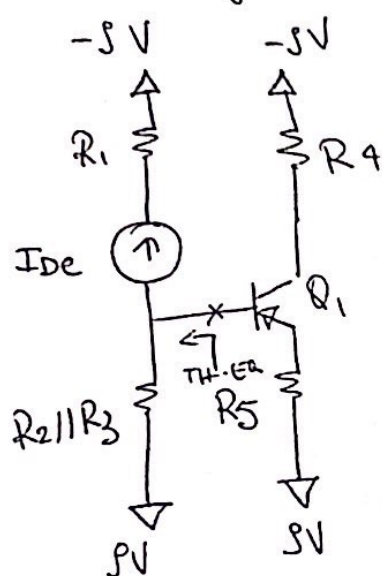
## DC analysis

It is convenient to reduce the linear circuit seen from the base of  $Q_1$  to its Thevenin equivalent circuit.




$$R_{TH} = \frac{V_x}{i_x} = R_2 || R_3$$

$$R_{TH} = ?$$

KVL @ L:

$$V_{TH} + (R_2 || R_3) I_{De} - 5 = 0$$

$$V_{TH} = 7 V$$

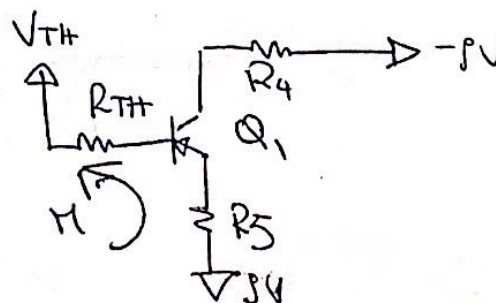

KVL @ H:

$$7V + I_B \cdot 10K + 0.64 + I_E \cdot 1.5K - 9 = 0$$

(2)

Assuming operation in the active region, we can write

$$I_E = (\beta + 1) I_B ; I_C = \beta I_B ; I_C = \frac{\beta}{\beta + 1} I_E$$

Then the KVL @ H can be written in terms of  $I_B$  only:

$$I_B = [10K + (201) 1.5K] = 2 - 0.64$$

$$I_B = 4.36 \mu A ; I_C \approx I_E = 873 \mu A.$$

In order to verify the assumption of active mode operation, we need to calculate the voltages on the base, on the emitter and on the collector. Indeed, a BJT transistor is in active mode if the E-B junction is forward biased (FB) and the B-C junction is reverse biased (RB).

For that to happen

$$V_{EB} \geq V_{EB(ON)} = 0.64$$

$$V_{CB} < V_{CB(ON)} \approx 0.4 - 0.5 V \text{ (Typical values)}$$

$$V_E = -9 + 10K I_E = -0.27 V$$

$$V_B = 7V + I_B \cdot 10K = 7.044V$$

$$V_C = 9V - I_E \cdot 1.5K = 7.68V$$


All these equations are obtained using KVL analysis.

$$V_{CB} = -7.314V \text{ CB Junction is reverse biased}$$

$$V_{EB} = 0.64V \text{ E-B Junction is forward biased}$$

THE ASSUMPTION OF ACTIVE MODE CONDITION IS VERIFIED.

AC (Small-signal analysis)

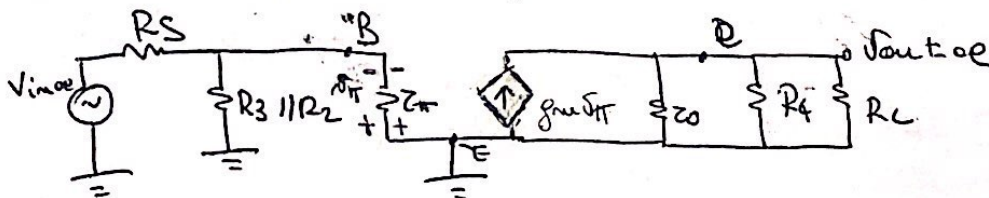

$$g_m = \frac{I_E}{V_T} = \frac{873 \mu A}{0.025V} = 0.03375 \frac{A}{V}$$

$$r_o = \frac{V_A}{I_E} = \frac{200}{0.00337} = 5.5K\Omega$$

$$Z_o = \frac{V_A + V_{EE}}{V_T} = \frac{100 + 7.55}{0.025} = 123K\Omega$$




$$GV = \frac{V_{out-ac}}{V_{in-ac}} = \frac{V_{out-ac}}{V_{\pi}} \cdot \frac{V_{\pi}}{V_{in}}$$

(3)

$$V_{\pi} = V_{in} \left( \frac{Z_{\pi} // R_2 // R_3}{R_s + Z_{\pi} // R_2 // R_3} \right)$$

$$V_{out-ac} = z-fm V_{\pi} (Z_o // R_4 // R_L)$$

$$GV = -5.57 \text{ V/V}$$

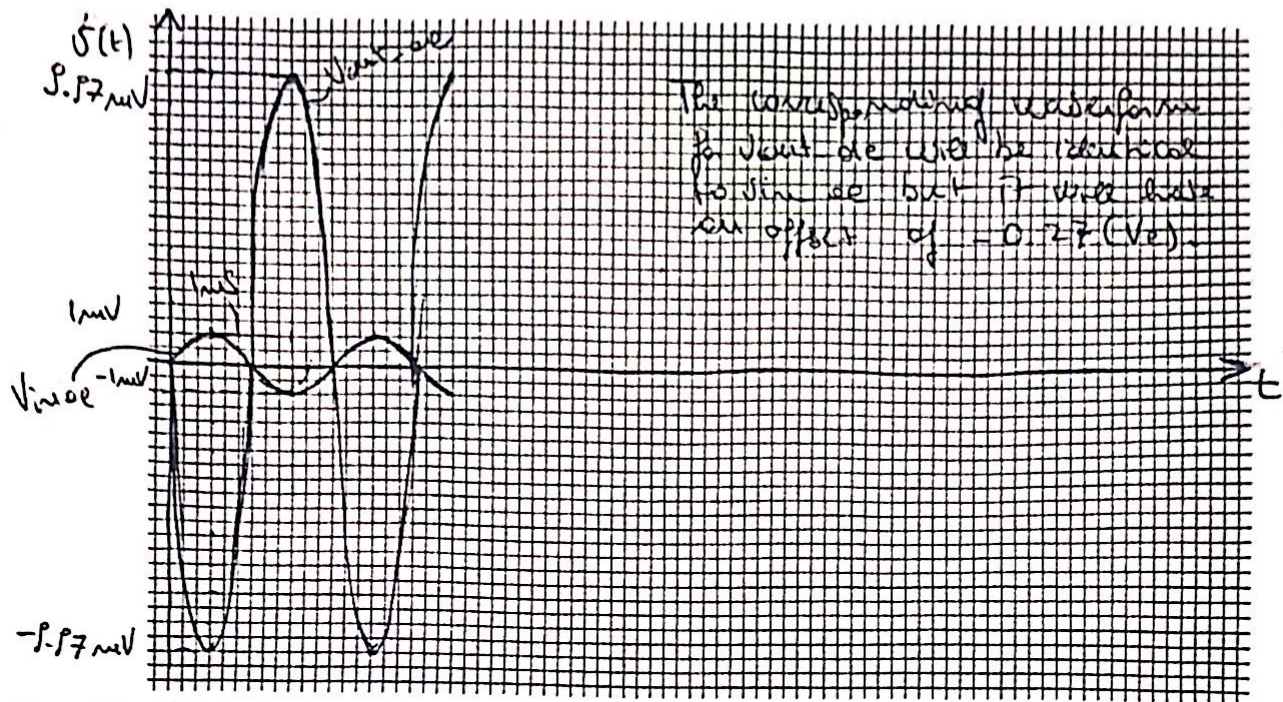

The corresponding waveform for  $V_{out-ac}$  will be identical to  $V_{in-ac}$  but it will have an offset of  $-0.27 (V_e)$  with respect to  $N(t) \Rightarrow$  axis.

PROBLEM 2


(a) Stage 1: CS ; Stage 2: CD

(b) In order to calculate the small-signal voltage gain we'll have to determine the position of the Q point. The reason for this is that the small-signal parameters ( $g_m, r_o$ ) are related to the coordinates of the Q point (e.g.,  $I_{DQ}$  and  $V_{DSQ}$ ).



Q POINT - DC analysis

$H_1$  and  $H_2$  are decoupled in DC due to  $C_2$ .

Stage 1 - DC analysis

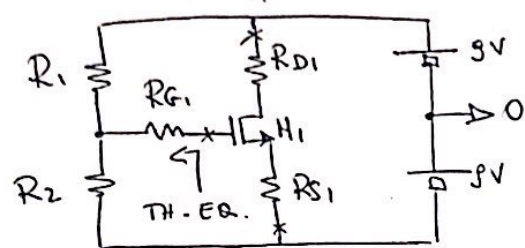


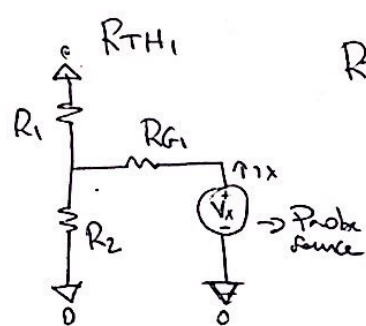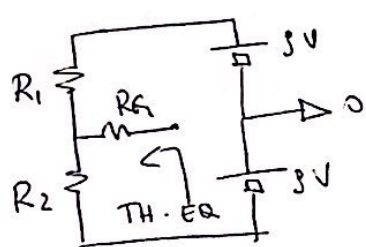It is convenient to reduce the circuit seen from the base to its Thevenin equivalent circuit.



$$R_{TH1} = \frac{V_x}{i_x} = R_{G1} + R_1 // R_2$$

$$R_{TH1} = 128.8 \text{ k}\Omega$$

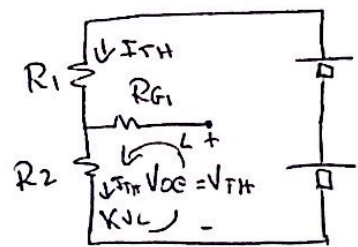


$$\text{KVL @ L: } V_{TH1} = -9 + R_2 I_{TH1}$$

$$I_{TH1} = \frac{18}{400\text{k} + 180\text{k}} = 30.51 \mu\text{A}$$
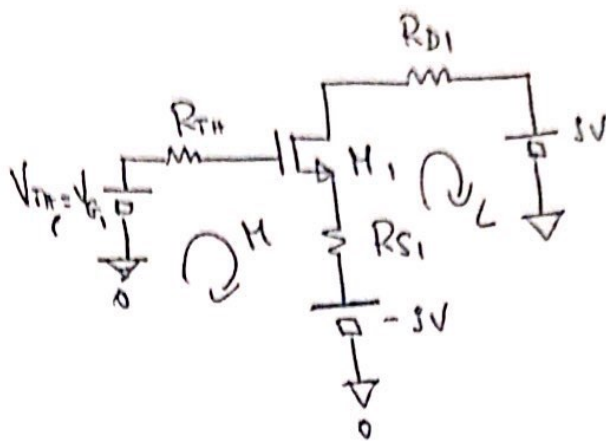
$$V_{TH1} = -9 + (30.51 \mu\text{A}) \cdot 180\text{k} = -3.2 \text{ V}$$





KVL @ L:

$$-I + I_{D1} R_{S1} + V_{DS1} + I_{D1} R_{D1} - I = 0$$

$$V_{DS1} = 18 - I_{D1} \cdot 13K$$

KVL @ H:

$$-I + I_{D1} R_{S1} + V_{GS1} - V_{TH1} = 0$$

$$-I + I_{D1} 5K + V_{GS1} + 3.2 = 0$$

$$5.8 = I_{D1} R_{S1} + V_{GS1} \Rightarrow V_{GS1} = 5.8 - I_{D1} 5K$$

Assuming that  $M_1$  operates in saturation,

$$I_{D1} = \frac{1}{2} \left( k_n' \frac{W}{L} \right) (V_{GS1} - V_T)^2 (1 + \lambda_1 V_{DS1})$$

$$I_{D1} = \frac{1}{2} (0.0027) (5.8 - I_{D1} 5K - 0.5)^2 (1 + 0.1 (18 - I_{D1} 13K))$$

↓  
ALGEBRA BOX

$$45.14 \mu A I_{D1}^3 - 308.47 K I_{D1}^2 + 516.74 I_{D1} - 0.1308 = 0$$

↓  
ALGEBRA BOX

$$I_{D1} = 930 \mu A$$


$$I_{D1} = 930 \mu A \Rightarrow V_{DS1} = 18 - 930 \mu \cdot 13K = 5.31 V$$

$$V_{GS1} = 5.8 - 930 \mu \cdot 5K = 1.15 V$$

$$V_{DS1} \geq V_{GS1} - V_T = 1.15 - 0.5 V$$



The saturation assumption is verified for  $M_1$ .

Stage 2 - DC analysis

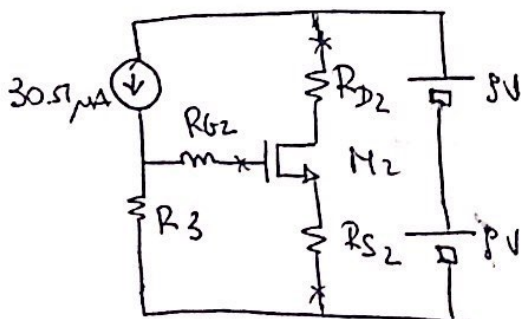

It is again convenient to use a Thevenin equivalent circuit of the network seen from the gate of  $M_2$ .


⑥

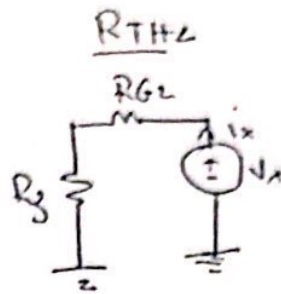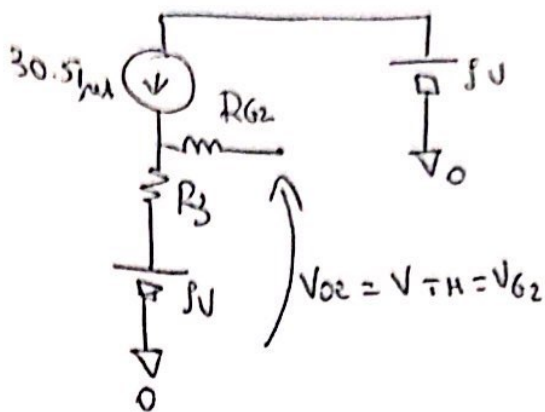

$$V_{TH} = V_{G2} = 30.5 \mu A (150 k\Omega) - 8 = -3.2 V$$

$$R_{TH2} = R_{G2} + R_3$$
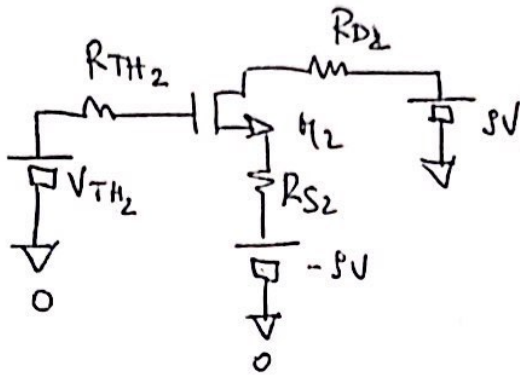
$$R_{TH2} = 75 + 150 k\Omega = 150.075 k\Omega \approx 150 k\Omega$$




Now, as  $V_{TH2} = V_{TH1}$   
 $R_{S2} = R_{S1}$ ,  $R_{D2} = R_{D1}$   
 $R_{TH2} \neq R_{TH1}$  but no current flows in it  
 The current flowing in  $R_3$  is the same value of the current flowing in  $R_1$  and  $R_2$ .

As a result the circuits determined for stage ① and ② provide identical values of  $V_{DS}$ ,  $V_{GS}$ , and  $I_D$ .

$$V_{GS2} = V_{GS1}, V_{DS2} = V_{DS1}, I_{D2} = I_{D1}$$

### AC (SMALL-SIGNAL) ANALYSIS

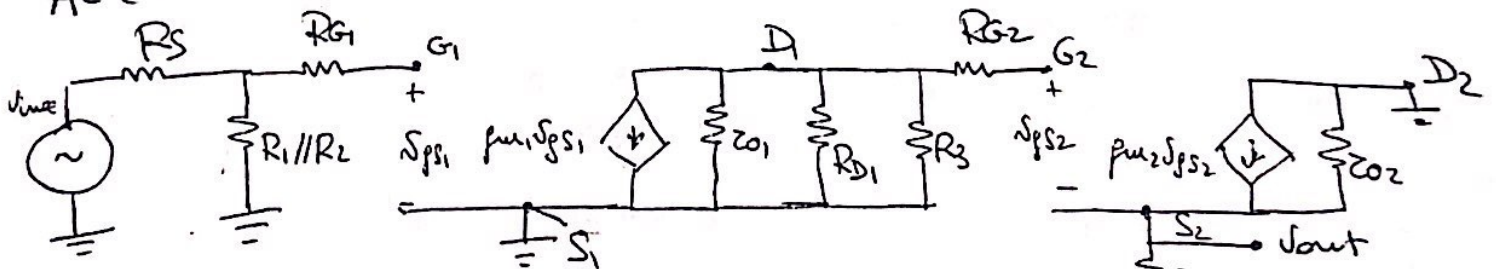

$$r_{o1} = r_{o2} = r_o = \frac{1}{\lambda + V_{DS1,2}} = \frac{10 + 5.91}{930 \mu} = 17.1 k\Omega$$

$$g_{m1} = g_{m2} = g_m = \frac{I_{D1,2}}{\left(\frac{V_{GS1} - V_T}{2}\right)} = \frac{930 \mu}{\frac{1.3 - 0.5}{2}} = 2.32 \text{ mA/V}$$

$$G_V = \frac{v_{out}}{v_{in,ac}} = \frac{v_{out}}{v_{ps2}} \cdot \frac{v_{ps2}}{v_{ps1}} \cdot \frac{v_{ps1}}{v_{in,ac}} = \frac{v_{out}}{v_{ps2}} \cdot \frac{v_{ps2}}{v_{g2}} \cdot \frac{v_{g2}}{v_{ps1}} \cdot \frac{v_{ps1}}{v_{in,ac}} \quad (7)$$

$$v_{ps1} = v_{in,ac} \cdot \frac{R_1 // R_2}{R_1 // R_2 + R_S} \Rightarrow \frac{v_{ps1}}{v_{in,ac}} = \frac{R_1 // R_2}{R_1 // R_2 + R_S} = \frac{128.8k}{128.8k + 75} \approx 1 \text{ V/V}$$

$$v_{g2} = v_{ps2} + v_{out}; \quad v_{out} = g_{m2} v_{ps2} (R_{S2} // R_{O2})$$

$$v_{g2} = v_{ps2} (1 + g_{m2} (R_{S2} // R_{O2})) \Rightarrow \frac{v_{ps2}}{v_{g2}} = \frac{1}{1 + g_{m2} (R_{S2} // R_{O2})}$$

$$\frac{v_{ps2}}{v_{g2}} = \frac{1}{1 + 2.32m(5k // 17.1k)} = \frac{1}{1 + 8.97} = 0.1 \text{ V/V}$$

$$v_{g2} = -g_{m1} (R_{D1} // R_3 // R_{O1}) v_{ps1} \Rightarrow \frac{v_{g2}}{v_{ps1}} = -g_{m1} (R_{D1} // R_3 // R_{O1})$$

$$\frac{v_{g2}}{v_{ps1}} = -2.32m(8k // 180k // 17.1k) = -2.32m \cdot 5.3k \approx -12.3 \text{ V/V}$$

$$v_{out} = g_{m2} v_{ps2} (R_{S2} // R_{O2}) \Rightarrow \frac{v_{out}}{v_{ps2}} = g_{m2} (R_{S2} // R_{O2})$$

$$\frac{v_{out}}{v_{ps2}} = 2.32m(5k // 17.1) = 8.97 \text{ V/V}$$


$$G_V = 8.97 \cdot 0.1 \cdot (-12.3)(1) \approx -11.1 \text{ V/V}$$



Problem 13  
 $V_{out} = 6V$  Sec

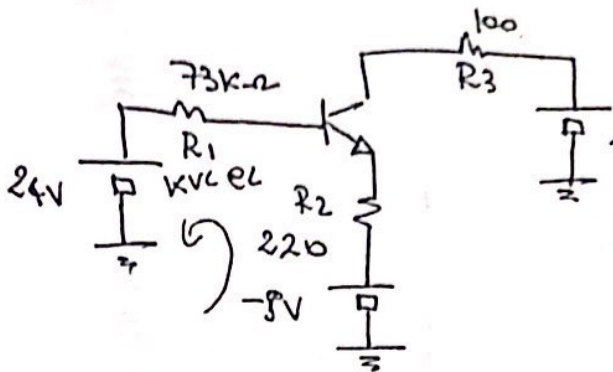(18)

In order to calculate the gain we need to determine the small signal parameters, which in turn depend on the coordinates of the Q point. Hence, the first thing to do is the DC analysis of the circuit.



KVL @  $L_1$

$$-5 + I_E R_2 + 0.7 + I_B R_1 = 24$$

$$I_E = (\beta + 1) I_B \quad \text{Assuming that the BJT is in active mode.}$$

$$I_B = \frac{24 + 5 - 0.7}{(\beta + 1) R_2 + R_1} = 335 \mu A$$

$$I_C = \beta I_B = 100 \cdot 335 \mu A = 33.5 \mu A$$

$$I_E = (\beta + 1) I_B = 101 \cdot 335 \mu A = 34.3 \mu A$$

Now we need to verify the assumption of active mode operation for the BJT.

$$V_{BE} > V_{BE(on)} = 0.7 V \quad (\text{B-E junction FB})$$

$$V_{CB} < V_{CB(on)} = 0.7 V \quad (\text{B-C junction FB})$$

$$V_E = 24 - R_3 I_E = 20.6 V$$

$$V_B = 24 - R_1 I_B = -0.76 V$$

$$V_E = -5 V + I_E R_2 = -1.46 V$$

$$\begin{cases} V_C > V_B \\ V_B > V_E \end{cases} \rightarrow \text{Active mode assumption is verified.}$$

$$g_m = \frac{I_C}{V_T} = \frac{33.5 \mu A}{0.025 V} = 1.3057 \frac{A}{V}$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{15 + 22.06}{33.5 \mu A} = 1.052 k\Omega$$


$$Z_{\pi} = \frac{\beta}{g_m} = \frac{100}{1.3057} = 76.35 \Omega$$





Small-signal equivalent circuit.

9

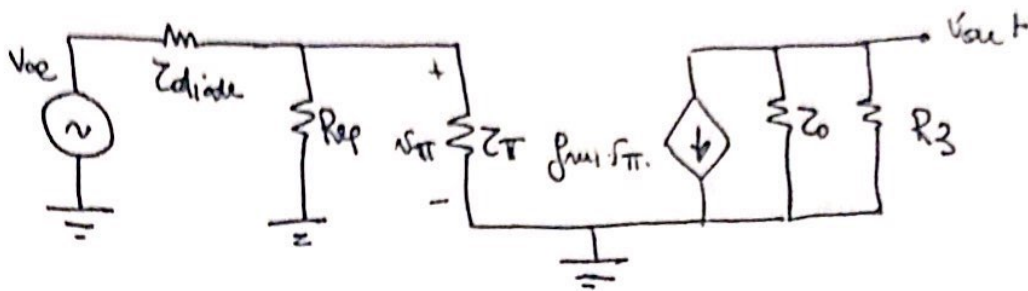

$$R_{eq} = R_1 // (R_4 + R_5)$$


$$G_V = \frac{v_{out}}{v_{ac}} = \frac{v_{out}}{v_{\pi}} \times \frac{v_{\pi}}{v_{ac}}$$

$$v_{out} = -g_m v_{\pi} (Z_o // R_3)$$

$$v_{\pi} = v_{ac} \frac{R_{eq} // Z_{\pi}}{R_{eq} // Z_{\pi} + Z_{diode}}$$

$$G_V = -g_m (Z_o // R_3) \left[ \frac{R_{eq} // Z_{\pi}}{R_{eq} // Z_{\pi} + Z_{diode}} \right]$$
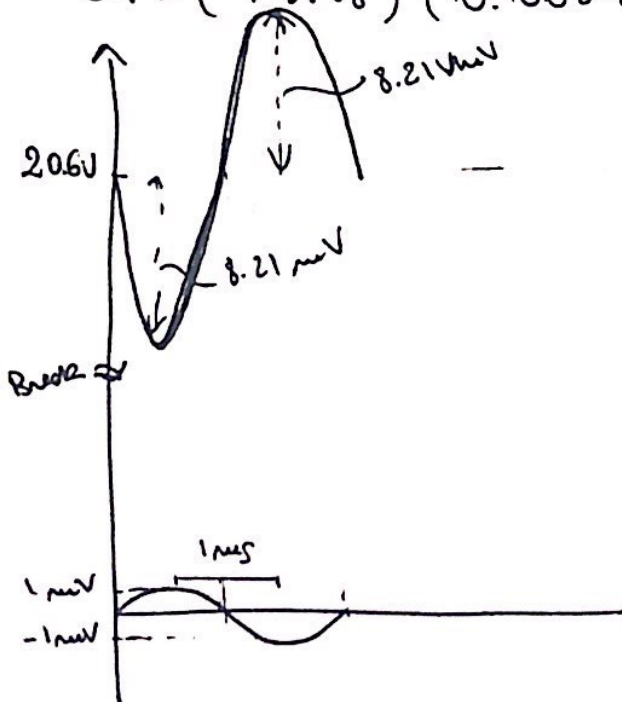
$$G_V = (-119.98) (0.0684) \text{ V/V} = -8.21 \text{ V/V}$$



NOT TO SCALE

Problem 4  
(e) Stage 1: CS - Stage 2: CD

(10)

(b)  $G_V = \frac{v_{out}}{v_{in}}$


$G_V$  will depend on the parameters of the small-signal circuit

$$g_m = 2\sqrt{k_n I_{DQ}} \quad \omega_o \approx \frac{1}{\lambda I_{DQ}}$$

One needs to perform the DC analysis of the circuit to be able to calculate  $g_m$  and  $\omega_o$ .

The 2 stages are coupled in DC.

DC CIRCUIT


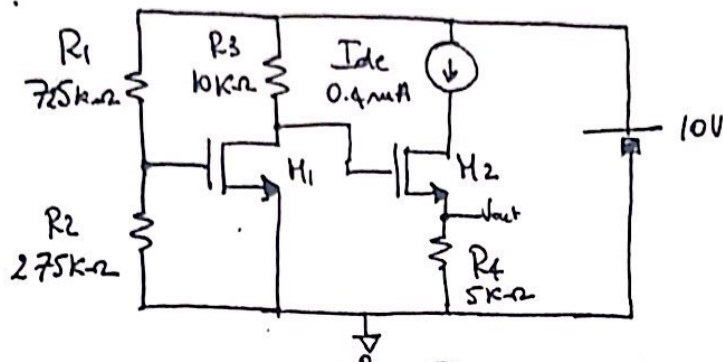



DC analysis for stage ①

Using the Thevenin equivalent of the circuit seen from the gate of  $M_1$ , I obtain

$$V_{TH} = \frac{10 \cdot 275}{275 + 725} \approx 2.75V$$

$$R_{TH} = 275k // 725k = 185.4k\Omega$$

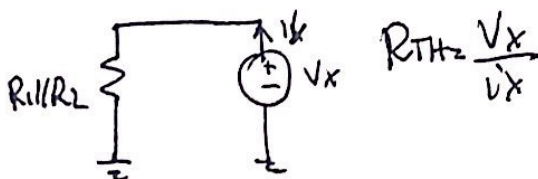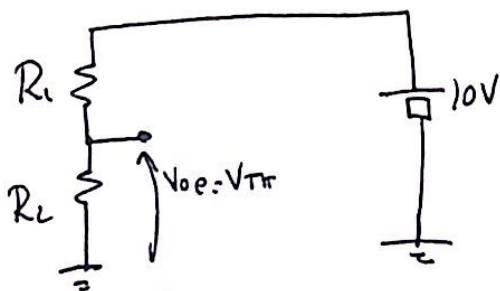

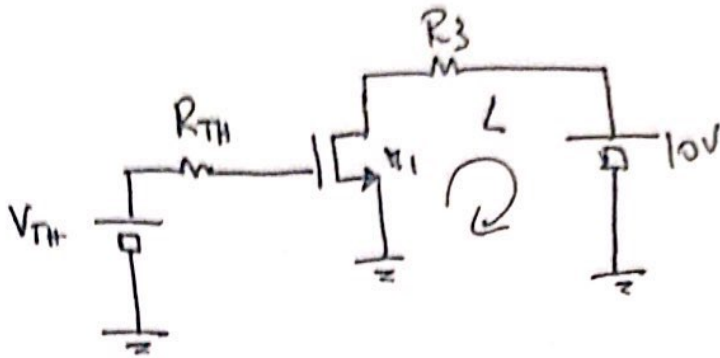

Since the source is grounded  $V_{GS1} = V_{G1} = V_{TH} = 2.75$

$$V_{DS1} = 10 - I_{D1} R_3 \quad (\text{From a KVL @ L})$$

Assuming that  $M_1$  is in saturation

$$I_{D1} = K_n (V_{GS1} - V_{TN})^2 (1 + \lambda V_{DS1})$$

$$I_{D1} = 125 \mu (2.75 - 1)^2 (1 + 0.1 [10 - I_{D1} \cdot 10K])$$

$$I_{D1} = (0.0003828) [2 - I_{D1} \cdot 1K] \Rightarrow I_{D1} = 0.000766 - 0.3828 I_{D1}$$

$$I_{D1} = \frac{0.000766}{1 + 0.3828} = 554 \mu A$$

Now let's verify that the assumption of saturation for  $M_1$  is correct.

$$V_{DS1} > V_{GS1} - V_{TN} \quad (\text{Condition for saturation})$$

$$V_{DS1} = 10 - [(554 \mu) \cdot 10K] = 4.46V$$

$$V_{GS1} = 2.75V \Rightarrow V_{GS1} - V_{TN} = 1.75V$$

$$V_{TN} = 1V$$

$$V_{DS1} = 4.46V > V_{GS1} - V_{TN}$$

The saturation assumption is verified for  $M_1$


DC analysis for stage ②

Since the DC current source forces a constant current through the drain and source,  $M_2$  should be in saturation.





(12)

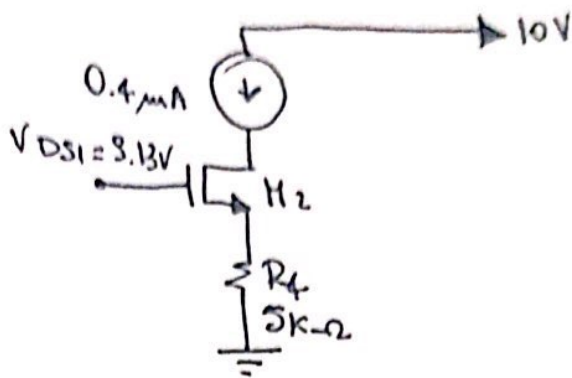

$$V_{S2} = 0.4 \text{ mA} \cdot 5 \text{ k}\Omega = 2 \text{ V}$$

$$V_{GS2} = V_{G2} - V_{S2} = V_{DS1} - V_{S2} = 4.46 \text{ V} - 2 \text{ V} = 2.46 \text{ V}$$

$$I_{D2} = K_M (V_{GS2} - V_{TN})^2 (1 + \lambda V_{DS2})$$

$$I_{D2} = 0.4 \text{ mA}$$

$$0.4 \text{ mA} = 1.25 \mu\text{A} (2.46 - 1)^2 (1 + 0.1 V_{DS2}) \Rightarrow 0.4 \text{ mA} = 0.00026 (1 + 0.1 V_{DS2})$$

$$\frac{0.4 \text{ mA}}{0.00026} = 1 + 0.1 V_{DS2} \Rightarrow 0.501 = 0.1 V_{DS2} \Rightarrow V_{DS2} = 5.01 \text{ V}$$

$$V_{DS2} = 5.01 > V_{GS2} - V_{TN} \quad (V_{GS2} - V_{TN} = 1.46 \text{ V})$$


$$g_{m1} = \frac{I_{D1}}{\frac{V_{GS1} - V_T}{2}} = 633 \mu\text{A/V}$$

$$g_{m2} = \frac{I_{D2}}{\frac{V_{GS2} - V_T}{2}} = 548 \mu\text{A/V}$$

$$Z_{O1} = \frac{1}{\lambda K_M (V_{GS1} - V_T)^2} = 26.1 \text{ k}\Omega \quad Z_{O2} = 37.53 \text{ k}\Omega$$

We can now calculate the small-signal voltage gain  $G_v$ .

Small-signal equivalent circuit.

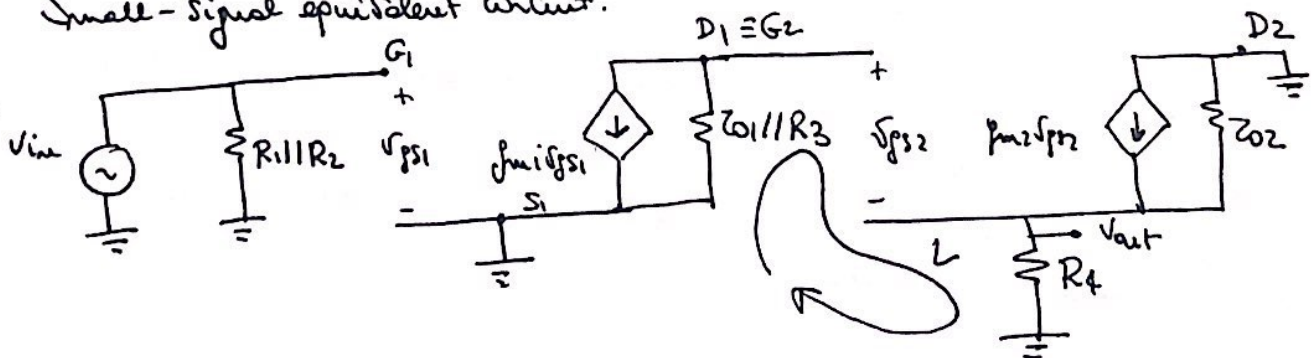

(13)

$$G_V = \frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_{gs2}} \cdot \frac{v_{gs2}}{v_{gs1}} \cdot \frac{v_{gs1}}{v_{in}}$$

$$v_{out} = g_{m2} v_{gs2} (R_4 // Z_{o2})$$

$$\text{KVL @ L: } (-g_{m1} v_{gs1})(Z_{o1} // R_3) = g_{m2} v_{gs2} (R_4 // Z_{o2}) + v_{gs2}$$

$$v_{in} = v_{gs1}$$

$$\frac{v_{gs2}}{v_{gs1}} = \frac{-g_{m1} (Z_{o1} // R_3)}{1 + g_{m2} (R_4 // Z_{o2})}$$

$$\frac{v_{out}}{v_{gs2}} = g_{m2} (R_4 // Z_{o2})$$

$$G_V = g_{m1} (R_3 // Z_{o1}) \left[ \frac{-g_{m2} (R_4 // Z_{o2})}{1 + g_{m2} (R_4 // Z_{o2})} \right] (1) =$$

$$= \underbrace{-g_{m1} (R_3 // Z_{o1})}_{\text{CS gain}} \underbrace{\left[ \frac{g_{m2} (R_4 // Z_{o2})}{1 + g_{m2} (R_4 // Z_{o2})} \right]}_{\text{CD gain}}$$

$$G_V = - (0.000633)(7230) \left[ \frac{0.000548 \cdot 4412}{1 + 0.000548 \cdot 4412} \right] =$$

$$= -4.577 \cdot 0.707 = -3.24 \text{ V/V}$$