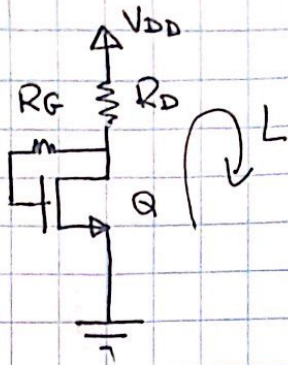


## ECE 322L - SPRING 2020

## LECTURE 4 - PROBLEM 1



$$I_D = 0.5 \mu\text{A} \quad V_{DD} = 5\text{V} \quad R_G = 1\text{M}\Omega$$

$$K_n' \frac{W}{L} = 1 \text{ mA/V}^2 \quad V_{TN} = 1\text{V} \quad \lambda = 0$$

$$R_D = ? ; I_{D, \text{ACT}} = ? ; V_{D, \text{ACT}} = ?$$

$V_G = V_D \Rightarrow V_{GS} = V_{DS} \Rightarrow V_{DS} > V_{GS} - V_T$ . Thus Q is in saturation.

KVL @ loop L:

$$V_{DD} - R_D I_D - V_{DS} = 0$$

$$R_D = \frac{V_{DD} - V_{DS}}{I_D}$$

$$R_D = \frac{V_{DD} - V_{GS}}{I_D}$$

$$I_D = \frac{1}{2} K_n' \frac{W}{L} (V_{GS} - V_{TN})^2 \Rightarrow (V_{GS} - V_{TN})^2 = \frac{0.5 \mu\text{A}}{1 \text{ mA/V}^2} = 1\text{V}$$

$$(V_{GS} - V_{TN}) = \pm 1 \Rightarrow V_{GS} \begin{cases} 0\text{V} \\ 2\text{V} \end{cases}$$

$V_{GS} = 0$  will be discarded as it is lower than the threshold

voltage.  $I_D = 0.5 \mu\text{A}$  hence, the transistor cannot be in cut-off.  
We select

$$V_{GS} = 2\text{V}$$

$$R_D = \frac{V_{DD} - V_{GS}}{I_D} = \frac{5 - 2}{0.5 \mu\text{A}} = 6 \text{ k}\Omega$$

We select  $R_D = 6.2 \text{ k}\Omega$  among the list of 5% resistor values.

Now, let's calculate  $I_{D,ACT}$  and  $V_{D,ACT}$ .

$$I_D = \frac{1}{2} \cdot 1m (V_{GS} - 1)^2 \quad V_{GS} = V_{DD} - R_D I_D$$

$$I_D = \frac{1}{2} m (V_{DD} - R_D I_D - 1)^2$$

$$I_D = \frac{1}{2} m (4 - 6.2k I_D)^2$$

$$38.44 I_D^2 - 51.6 I_D + 16 = 0 \rightarrow I_D \begin{cases} 0.49mA \\ 0.86mA \end{cases}$$

• For  $I_D = 0.86mA$ ,  $V_{GS} = V_{DD} - R_D I_D \Rightarrow V_{GS} = 5 - 6.2k \cdot 0.86mA$

$$V_{GS} = 5 - 5.33 = -0.33V$$

$V_{GS} < V_T$  Q is in cut-off for  $V_{GS} = -0.33V$ . As the required  $I_D = 0.5mA$ , Q can't be in saturation.

• For  $I_D = 0.49mA$ ,  $V_{GS} = 5 - 6.2k \cdot 0.49mA = 1.96V$

$$V_{GS} > V_{TN}$$

$$I_{D,ACT} = 0.49mA$$

$$V_{D,ACT} = 1.96V$$



## LECTURE 4 - PROBLEM 2

$$\frac{L_2}{L_1} = 1 \quad \frac{W_2}{W_1} = 5 \quad I = I_{D2} = 0.5 \text{ mA} \quad V_{DD} = -V_{SS} = 5 \text{ V}$$

$$K_n' \left( \frac{W}{L} \right)_1 = 0.8 \text{ mA/V}^2 \quad V_{TN} = 1 \text{ V} \quad \lambda = 0 \quad R = ?$$

$$V_{G_{1,2}} = ?$$

$$I = I_{REF} \frac{(W/L)_2}{(W/L)_1} = I_{REF} \cdot \frac{W_2}{W_1} \Rightarrow I_{REF} = I \cdot \frac{W_1}{W_2} = \frac{0.5 \text{ mA}}{5} = 0.1 \text{ mA}$$

$$I_{REF} = \frac{V_{DD} - V_G}{R} \Rightarrow R = \frac{V_{DD} - V_G}{I_{REF}}$$

$$V_{GS_1} = V_{DS_1} \Rightarrow Q_1 \text{ is in saturation. Thus}$$

$$I_{D1} = I_{REF}$$

$$I_{REF} = \frac{K_n'}{2} \left( \frac{W}{L} \right)_1 (V_{GS_1} - V_{TN})^2 \Rightarrow (V_{GS_1} - V_{TN})^2 = \frac{0.1 \cdot 2}{0.8}$$

$$V_{GS_1} - V_{TN} = \pm 0.5 \Rightarrow V_{GS_1} = \begin{cases} 1.5 \text{ V} & \text{(Select as it is larger than } V_{TN}) \\ 0.5 \text{ V} & \text{(Discard as it is lower than } V_{TN}) \end{cases}$$

$$V_G = V_{SS} + V_{GS_1} \Rightarrow V_G = V_{SS} + V_{GS_1} = -5 \text{ V} + 1.5 = -3.5 \text{ V}$$

$$R = \frac{5 - (-3.5)}{0.1 \text{ mA}} = 85 \text{ k}\Omega$$

$$V_{D_{2 \text{ min, SAT}}} = V_{SS} + V_{DS_{1 \text{ SAT}}} ; V_{DS_{1 \text{ SAT}}} = V_{GS_2} - V_{TN}$$

$$V_{GS_2} = V_{GS_1} = 1.5 \text{ V} \Rightarrow V_{DS_{2 \text{ SAT}}} = 1.5 - 1 = 0.5 \text{ V}$$

$$V_{D_{2 \text{ min, SAT}}} = -5 + 0.5 = -4.5 \text{ V}$$