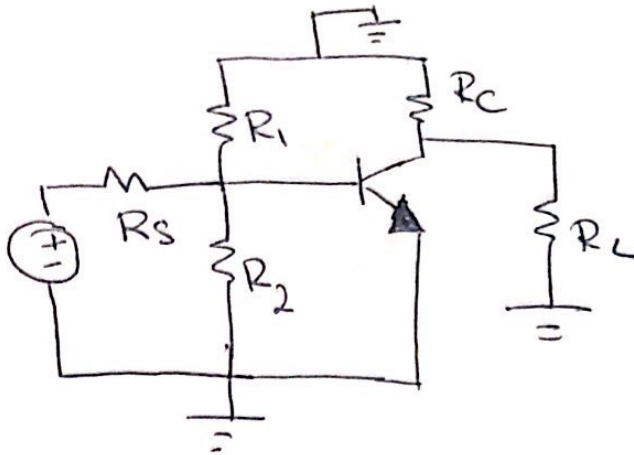



# In class problem - Lecture 18

(1)


Determine the upper cut-off frequencies of the given circuit.



AC CIRCUIT AT HIGH FREQUENCY

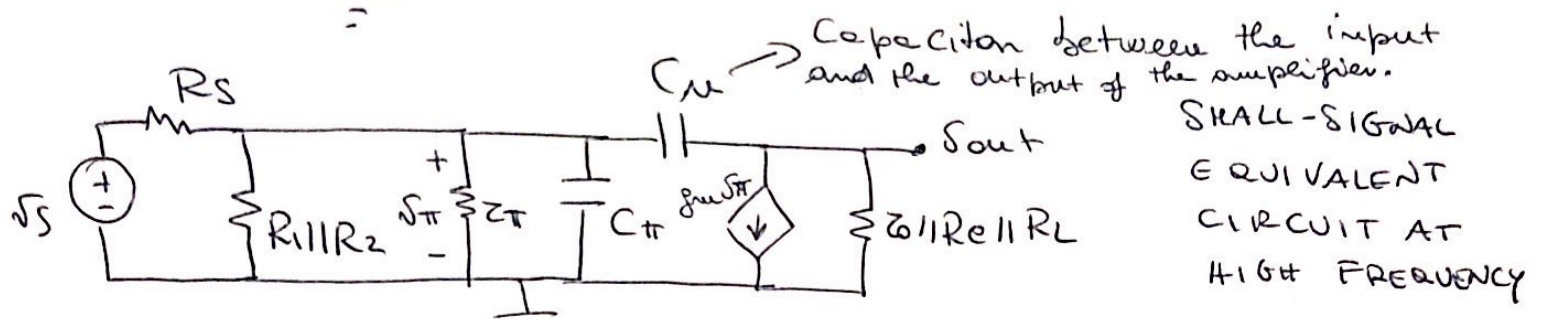

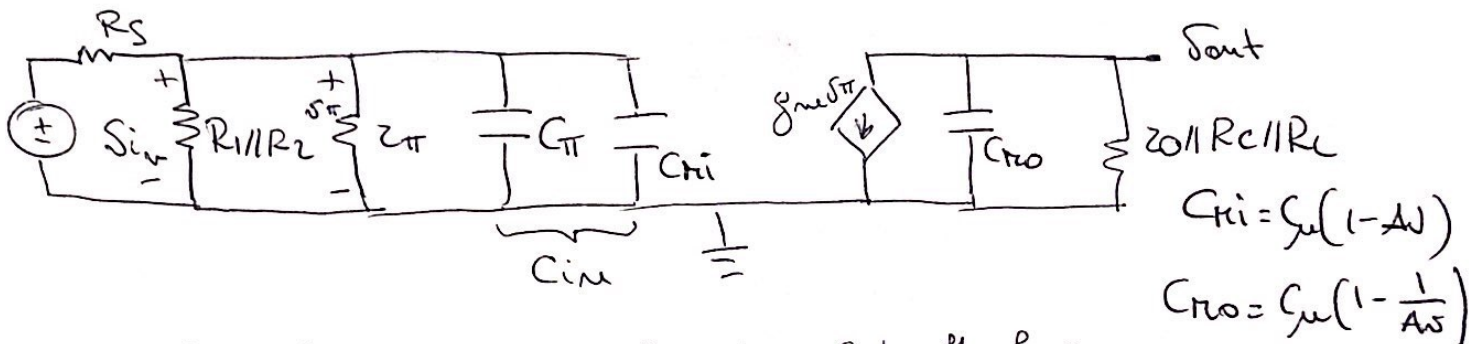Using the Miller theorem we can reduce the circuit to



$C_{in} = C_{\pi} + C_{mi}$  will yield one upper cut-off frequency


$$f_{H_{in}} = \frac{1}{2\pi R_{eq_{in}} C_{in}}$$

$C_{out} = C_{\mu} + C_{mo}$  will yield one upper cut-off frequency

$$f_{H_{out}} = \frac{1}{2\pi R_{eq_{out}} C_{out}}$$

$A_v$  is the amplifier midband gain:  $A_v = V_{out} / V_{in}$

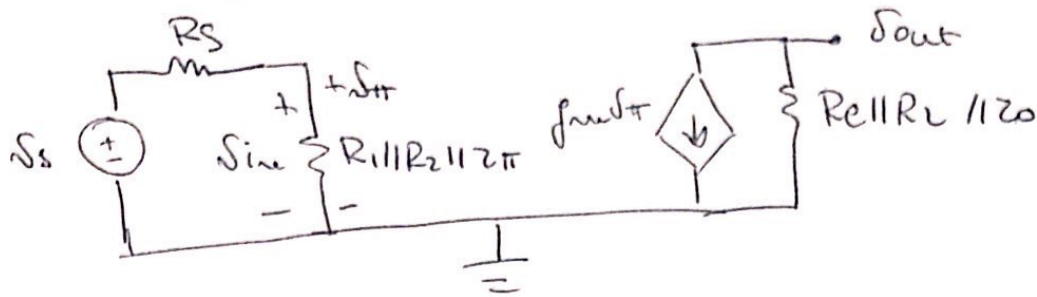As we need the midband gain to determine the 2 Miller Capacitances, we need to sketch the midband circuit



$$A_V = \frac{S_{out}}{v_{in}}$$

$$S_{out} = -g_m v_{\pi} (R_D \parallel R_L \parallel Z_o)$$

$$v_{\pi} = S_{in}$$


$$A_V = -g_m (R_D \parallel R_L \parallel Z_o) = -73.35 \text{ V/V}$$

Thus

$$C_{Mi} = C_{\mu} (1 - A_V) = (2.4 \text{ pF}) (74.35) = 178.44 \text{ pF}$$

$$C_{Mo} = C_{\mu} \left( 1 - \frac{1}{A_V} \right) \approx 2.4 \text{ pF} \cdot 1 = 2.4 \text{ pF}$$

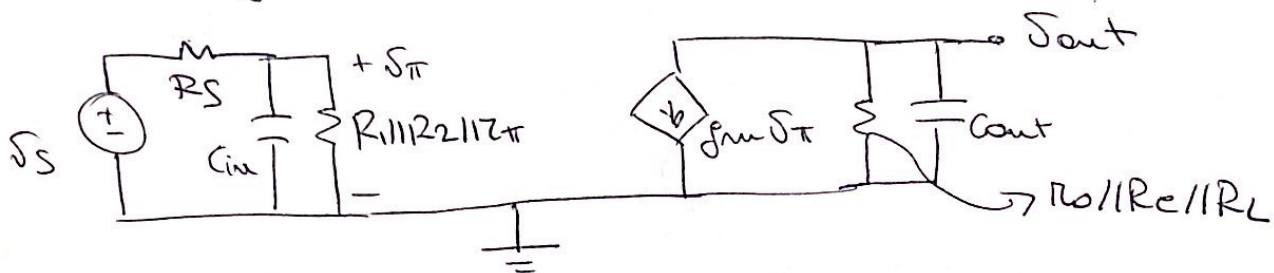Now, going back to the high frequency circuit



$$C_{in} = C_{\pi} + C_{Mi} = 20 \text{ pF} + 178.44 \text{ pF} = 198.44 \text{ pF}$$

$$C_{out} = C_{Mo} = 2.4 \text{ pF}$$

To determine the upper cut-off frequencies established by  $C_{in}$  and  $C_{out}$  we need to determine the equivalent resistance seen by the 2 capacitors, namely  $R_{eqin}$  and  $R_{eqout}$ .


Repin

(3)

$$sS=0$$

$$\frac{1}{j\omega C_{in}} = \infty$$

$C_{in}$  replaced by a probe source

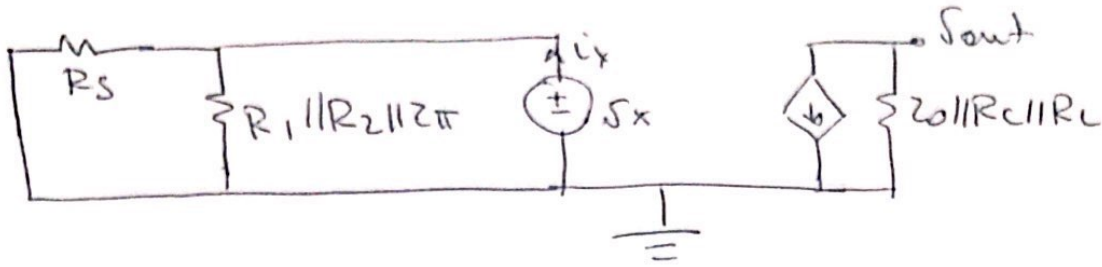

$$R_{pin} = \frac{S_x}{i_x} = R_S \parallel R_1 \parallel R_2 \parallel \frac{1}{j\omega\pi} = 389.47 \Omega$$


$$f_{H_{in}} = \frac{1}{2\pi R_{pin} C_{in}} = \frac{1}{2\pi \cdot 389.47 \cdot 198.46 \text{ pF}} \approx 2 \text{ kHz}$$

Report

$$sS=0$$

$$\frac{1}{j\omega C_{in}} = \infty$$


$C_{in}$  replaced by a probe source.

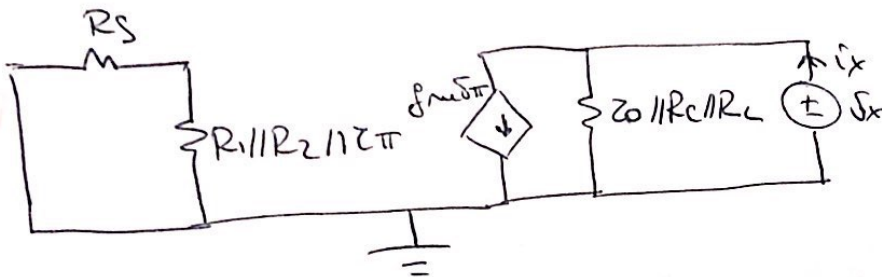

$$R_{out} = \frac{S_x}{i_x}$$

$$s\pi=0 \Rightarrow \text{for } s\pi=\infty$$

Thus the circuit reduces to

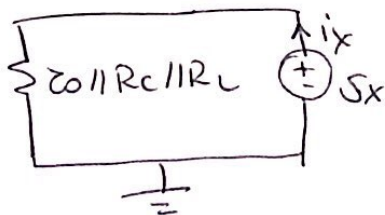

$$R_{out} = \frac{S_x}{i_x} = Z_0 \parallel R_C \parallel R_L = 1.08 \text{ k}\Omega$$

$$f_{H_0} = \frac{1}{2\pi R_{out} C_{out}} \approx 61.4 \text{ kHz}$$

The two upper corner frequencies of the circuit are (4)

$$f_{H1} \approx 2 \text{ MHz} \quad \text{and} \quad f_{H2} \approx 61.4 \text{ kHz}$$

The dominant upper cut-off frequency is the lowest of the two

$$f_H = f_{H1} \approx 2 \text{ MHz}$$