


Assigned on April 6<sup>th</sup> 2020 at 10:30 am-Due on April 7<sup>th</sup> 2020 at 12:30 pm

NAME: David Kirby MAXIMUM POINTS: 100+15 Extra-credit

ECE 322L: Electronics-II (Spring 2020, University of New Mexico)  
MID TERM EXAMINATION-II

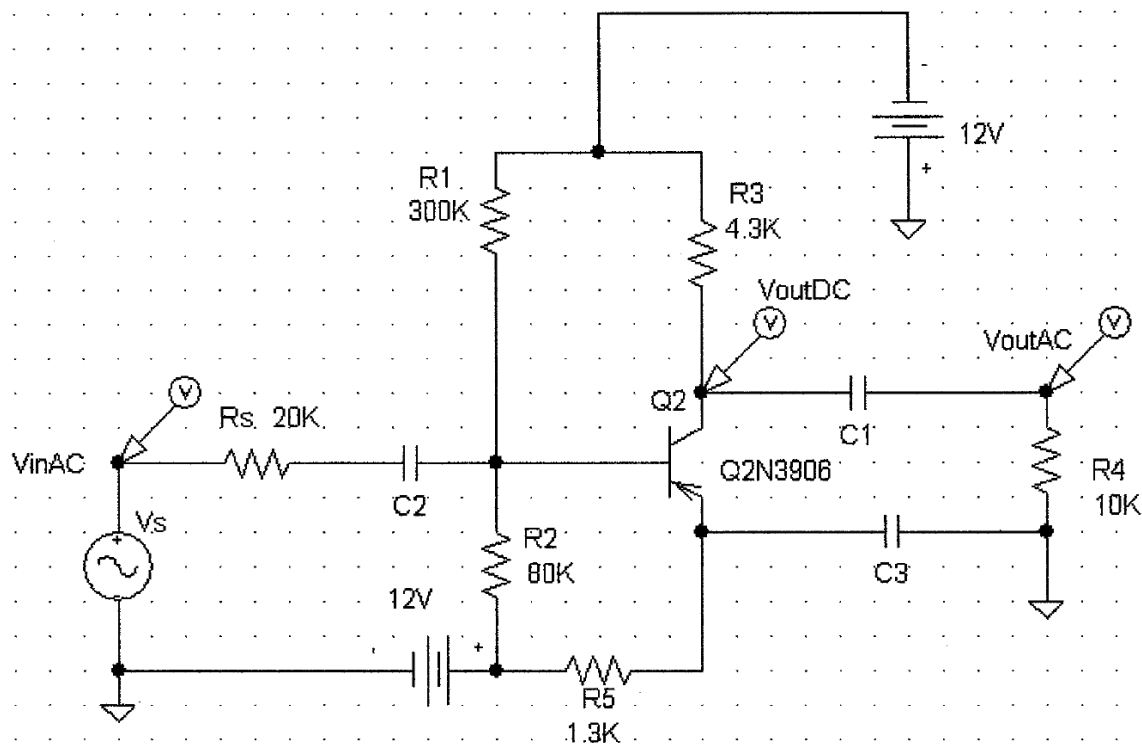**Problem 1 (100 pts.)**

For the circuit below:  $V_{EB(on)}=0.7$  V,  $\beta=180.7$ ,  $V_A=100$  V,  $V_{inAC} = 1$  mV amplitude (i.e., 2m V peak to





peak sinusoidal signal) at 1 KHz.

Given the above input voltage,  $V_{inAC}$ , sketch (or plot) and accurately label a plot the TWO output waveforms  $V_{outAC}$  and  $V_{outDC}$  on the graph paper provided on the next page. Assume the turn on voltages for all forward biased junctions are 0.7 V. You may assume all capacitors are AC shorts. For full credit, be sure to check your assumptions on the mode of operation of the transistor and to clearly label the axes of your plot.

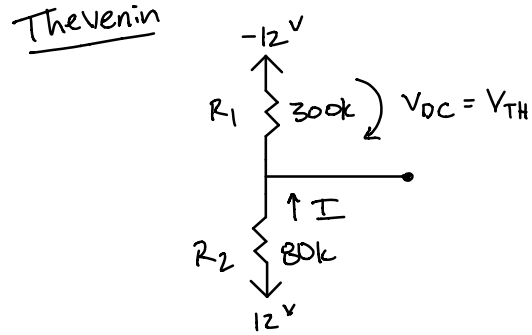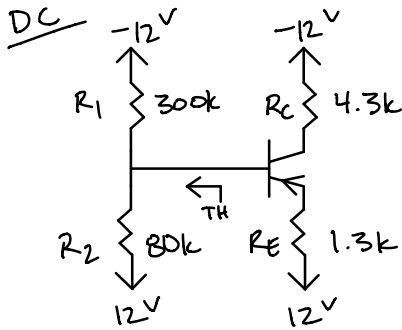**Extra-credit question (15 pts.)**

Identify the corresponding different operation regions of a pnp BJT in each quadrant of the  $V_{EB}$ - $V_{CB}$  parameter space.



$$V_{TH} = -12V + I R_1$$

$$I = \frac{12 - (-12)}{R_1 + R_2} = \frac{24V}{380k\Omega} = 63.158\mu A$$

$$= -12V + (63.158\mu A)(300k)$$

$$= 6.9474V$$

$$R_{TH} = R_1 \parallel R_2 = 300k \parallel 80k = 63.158k\Omega$$

KVL

$$V^+ = (1 + \beta) I_{BQ} R_E + V_{EB(on)} + I_{BQ} R_{TH} + V_{TH}$$

$$12V = (181.7) I_{BQ} (1.3k\Omega) + 0.7V + I_{BQ} (63.158k\Omega) + 6.9474V$$

$$I_{BQ} = 14.539\mu A$$

$$I_{CQ} = \beta I_{BQ} = (80.7)(14.539\mu A) = 2.6273mA$$

$$I_{EQ} = \frac{I_C (1 + \beta)}{\beta} = 14.620\mu A$$

check Assumptions

$$V_{EB} \geq V_{EB(on)} = 0.7V$$

$$V_{CB} < V_{CB(on)} \approx 0.4V - 0.5V \text{ (typical values)}$$

$$V_C = V^- + I_C R_C = -12 + (2.6273mA)(4.3k) = \boxed{-0.7027V} \quad V_{out DC}$$

$$V_B = V_{TH} + I_B R_B = 6.9474V + (14.539\mu A)(63.158k\Omega) = 7.866V$$

$$V_E = V^+ - I_E R_E = 12V - (14.620\mu A)(1.3k\Omega) = 11.981V$$

$$V_{CB} = V_C - V_B = -0.7027V - 7.866V = -8.5684V$$

$$V_{EB} = V_E - V_B = 4.1153 \text{ V}$$

$$V_{EB} \geq V_{EB(on)} = 0.7 \text{ V}$$

$$4.1153 \geq 0.7 \quad \checkmark$$

$$V_{CB} < V_{CB(on)} \approx 0.4 \text{ V} - 0.5 \text{ V}$$

$$-0.5684 < 0.4 \quad \checkmark$$

The assumption of  
for active mode  
is verified.


$$V_{EC} = V_E - V_C = 11.981 \text{ V} - (-0.727 \text{ V}) = 12.684 \text{ V}$$

AC

$$g_m = \frac{I_C}{V_T} = \frac{2.6273 \text{ mA}}{0.0259 \text{ V}} = 0.10144 \frac{\text{A}}{\text{V}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{180.7}{0.10144} = 1.7814 \text{ k}\Omega$$

$$r_o = \frac{|V_A|}{I_C} = \frac{100 \text{ V}}{2.6273 \text{ mA}} = 38.062 \text{ k}\Omega$$

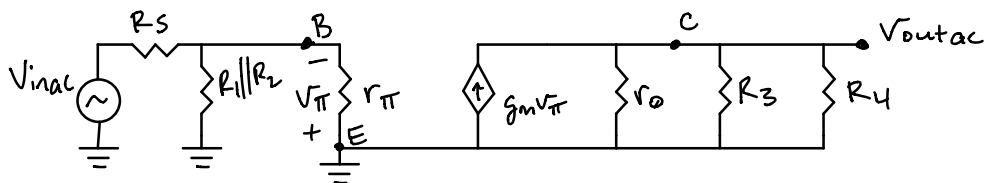


$$G_V = \frac{V_{out ac}}{V_{in ac}} = \frac{V_{out ac}}{V_{\pi}} \cdot \frac{V_{\pi}}{V_{in}}$$

$$\begin{aligned} V_{\pi} &= V_{in} \left( \frac{r_{\pi} || R_1 || R_2}{R_S + r_{\pi} || R_1 || R_2} \right) \\ &= (1 \text{ mV}) \left( \frac{1.7814 \text{ k}\Omega || 80 \text{ k}\Omega || 300 \text{ k}\Omega}{20 \text{ k}\Omega + 1.7814 \text{ k}\Omega || 80 \text{ k}\Omega || 300 \text{ k}\Omega} \right) \end{aligned}$$


$$= (1 \text{ mV}) \frac{1.7325 \text{ k}\Omega}{21.733 \text{ k}\Omega} = 79.719 \text{ mV}$$

$$\begin{aligned} V_{out ac} &= -g_m V_{\pi} (r_o || R_3 || R_4) \\ &= (-0.10144)(79.719 \text{ mV})(2.7868 \text{ k}\Omega) \\ &= -22.536 \end{aligned}$$

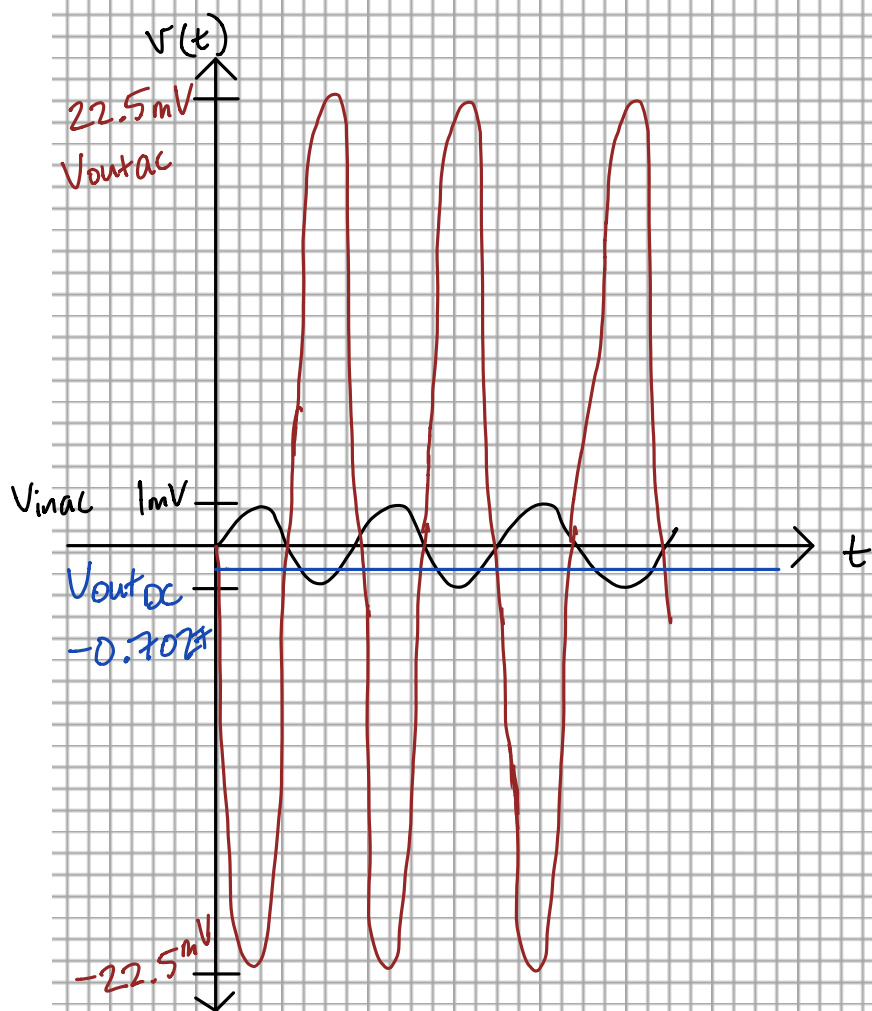
$$G_V = \frac{V_{out ac}}{V_{in ac}} = -22.536$$



## Extra credit

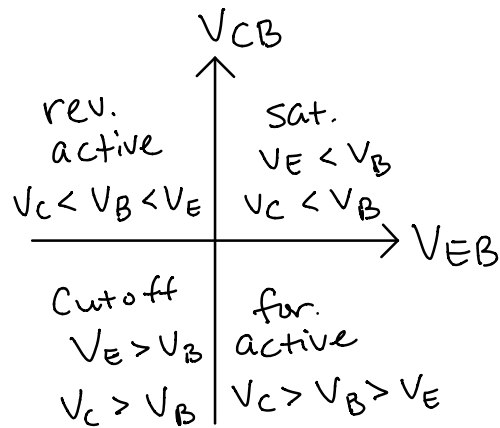

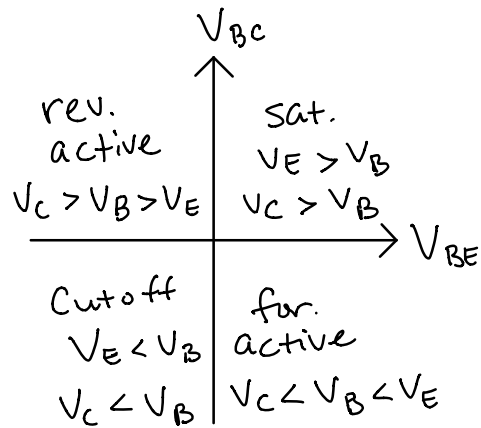For pnp we use the graph from class, but replace  $V_{BC}$  with  $V_{CB}$  and replace  $V_{BE}$  with  $V_{EB}$ .



Alternatively, we could flip all of the signs.