

ECE 438: Computer Design
Electrical and Computer Engineering
University of New Mexico

Instructor: Andrew Targhetta

Lab 2

The Instruction and ALU Decoders

Due: March 12th, 2020

Introduction

The objective of the second laboratory exercise is to describe the decode logic using an HDL. As with the previous lab, this lab is VHDL centric, but you are welcome to use Verilog.

Background

The decode logic within our processor takes as input the *Opcode* and *Function* fields from the MIPS instruction and outputs a number of control signals that orchestrate the flow of data through the datapath. To simplify the decode logic and remain consistent with lecture material, we will create two components for decoding, namely the **Instruction Decode Unit** and the **ALU Decode Unit**. Figure 1 depicts the single cycle microarchitecture with both decode logic components and their associated output control signals. For now, we will support the following instructions:

- Arithmetic — ADDU, ADDIU, SUBU
- Logical — AND, ANDI, NOR, OR, ORI, XOR, XORI
- Shift — SLL, SRL, SRA

- Comparison — SLTU, SLTIU
- Loads and stores — LW and SW
- Branch Equal and Jump — BEQ and J
- Load Upper Immediate — LUI

 


Figure 1: Single-cycle MIPS Block Diagram

Procedure

1. Describe the ALU decode unit in VHDL. The **ALU Decode Unit** allows further decoding of an R-type instruction with the *Function* field from the MIPS instruction. The process of decoding an instruction into a control code that the ALU can understand (Table 1) is split up into two blocks. The first block is contained within the instruction decode unit and will be addressed shortly. The second block is the ALU decode unit shown in Figure 1, which takes in an ALU op code from the main decode unit and the function field from the instruction. The ALU control logic should asynchronously function as follows:

Operation	ALU Control Line
AND	0000
OR	0001
SLL	0011
SRL	0100
ADDU	1000
SUBU	1001
XOR	1010
SLTU	1011
NOR	1100
SRA	1101
LUI	1110

Table 1: Arithmetic Logic functions and associated control codes

- When *AluOp* is not equal to “1111,” *AluCtrl* should be set to *AluOp*.
- When *AluOp* is equal to “1111,” the function field should be used to determine *AluCtrl*.

For R-type instructions, the instruction decode unit simply sets the *AluOp* to “1111” and the ALU decode unit will interpret the arithmetic or logic function needed to carry out the instruction and pass this information on to the ALU. However, when an instruction other than an R-type instruction is decoded, the instruction decode unit must specify the correct ALU control code on *AluOp*.

Helpful Hints:

- Describe the ALU decode logic in VHDL using the following entity:

```

1 entity AluDecode is
2     port( AluOp: in std_logic_vector(3 downto 0);
3           Funct: in std_logic_vector(5 downto 0);
4           AluCtrl: out std_logic_vector(3 downto 0)
5 );
6     end AluDecode;
```

- CASE statements can be nested within IF ELSE statements within PROCESS blocks.
2. Describe the Instruction Decode Unit in VHDL. The **Instruction Decode Unit** essentially takes as input the *Opcod*e field from the MIPS instruction and decodes it into various control signals that will orchestrate the flow of data. Use the skeleton code below to guide you through the process:

```

-----
2  -- This component describes the instruction decode unit
  -- in our MIPS processor.
4  -----

6  library ieee;
   use ieee.std_logic_1164.all;
8  -----

10
   entity InstrDecode is
12
   port ( --6-bit op field of instruction
14         Opcode: in std_logic_vector(5 downto 0);
          --6-bit funct field of instruction
16         Funct: in std_logic_vector(5 downto 0);
          -- asserted when shamt field is input to ALU
18         UseShamt: out std_logic;
          -- asserted when the immediate field is input to ALU
20         UseImmed: out std_logic;
          -- asserted when immed needs to be sign extended
22         SignExtend: out std_logic;
          -- asserted when instruction is a jump
24         Jump: out std_logic;
          -- asserted when instruction is a branch
26         Branch: out std_logic;
          -- Determines ALU operation, see ALU decode unit
28         AluOp: out std_logic_vector(3 downto 0);
          -- selects between rt and rd for the register destination
30         RegDst: out std_logic;
          -- asserted when reading from memory (loads!)
32         MemRdEn: out std_logic;
          -- asserted when writing to memory (stores!)
34         MemWrEn: out std_logic;
          -- selects the source for writing into register file
36         RegSrc: out std_logic;
          -- asserted when writing into register file
38         RegWrEn: out std_logic
          -- that's all folks!
40 );
   end InstrDecode;
42
-----

44
   architecture InstrDecode of InstrDecode is
46
   begin
48       --One big ol' case statement makes this description easy!
       process (Opcode, Funct) -- output depends on op field and funct

```

```

50     begin
51         case Opcode is
52             -- R-type instruction
53             -- For our small instruction set, the R-type instruction
54             -- is the only instruction where we have to look at the
55             -- function field...
56             when b"000000" =>
57                 -- SLL, SRL, and SRA use the shamt field
58                 if (Funct=b"000000" or Funct=b"000010" or Funct=b"000011") then
59                     UseShamt <= '1'; -- using shamt
60                 else
61                     UseShamt <= '0'; --not using shamt
62                 end if;
63                 UseImmed <= '0'; -- nor immediate
64                 SignExtend <= '-'; -- doesn't matter
65                 Jump <= '0'; --don't jump!
66                 Branch <= '0'; -- don't branch either
67                 AluOp <= b"1111"; --use function field
68                 RegDst <= '1'; --rd specifies destination
69                 MemRdEn <= '0'; --leave memory alone
70                 MemWrEn <= '0';
71                 RegSrc <= '1'; --use ALU output
72                 RegWrEn <= '1'; --writing into register file
73             -- Fill in the rest of the supported instructions
74             -- to avoid describing latches
75             when others =>
76                 -- don't care because invalid instruction!
77                 UseShamt <= '-';
78                 UseImmed <= '-';
79                 SignExtend <= '-';
80                 Jump <= '0'; --don't jump!
81                 Branch <= '0'; -- don't branch either
82                 AluOp <= (others => '-');
83                 -- fill in the rest here!
84                 MemRdEn <= '0'; --leave memory alone
85                 MemWrEn <= '0';
86                 -- finish this, but don't allow state to change
87                 -- when an invalid instruction is encountered!
88                 -- I'm going to test for this, so get it right...
89             end case;
90     end process;
91     -- was that so hard?!?
92 end InstrDecode;

```

1 Deliverables

1. Email all HDL source files with comments to `adtargh@unm.edu`.

Note: Code submitted without adequate comments will not be graded!

2. Answer the following questions:

- (a) Is the instruction decode unit combinational logic or sequential logic? Describe your reasoning.
- (b) Is the ALU decode unit combinational logic or sequential logic? Describe your reasoning.
- (c) How might you modify the instruction decode HDL to incorporate the functionality of the ALU decode unit?