

# ECE 322L

## Electronics 2

03/05/20- Lecture 13


Biasing the BJT 2

---

# Updates and overview


- There have been issues with UNM Learn reporting incorrect due dates for the assignment. The problem has been rectified.
- Lecture 13- Biasing the BJT 1 (Neamen 5.2 and 5.4, S&S 6.7)

# Biasing configurations

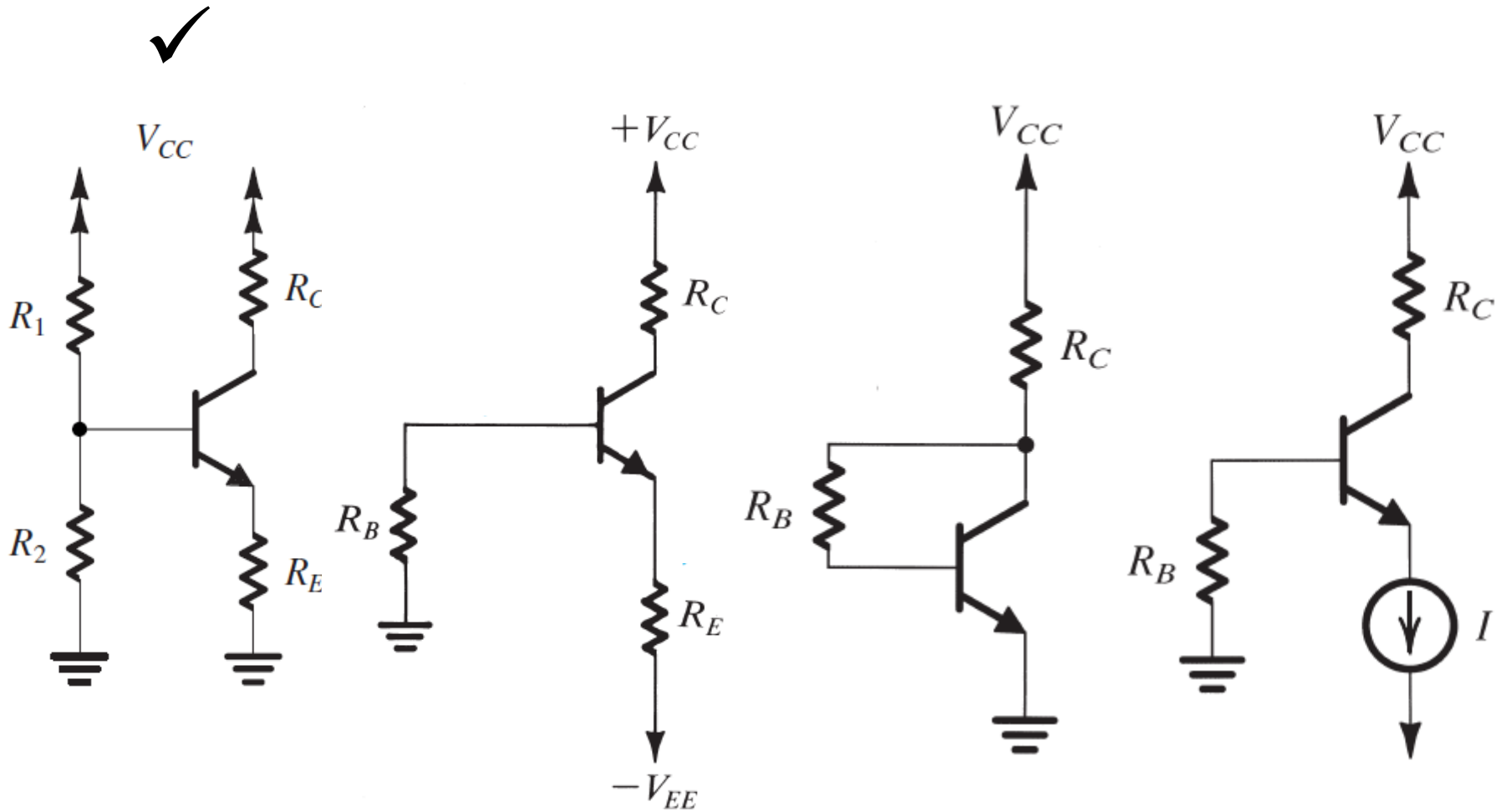

# Biasing configurations (2)

\* See next slide for more details

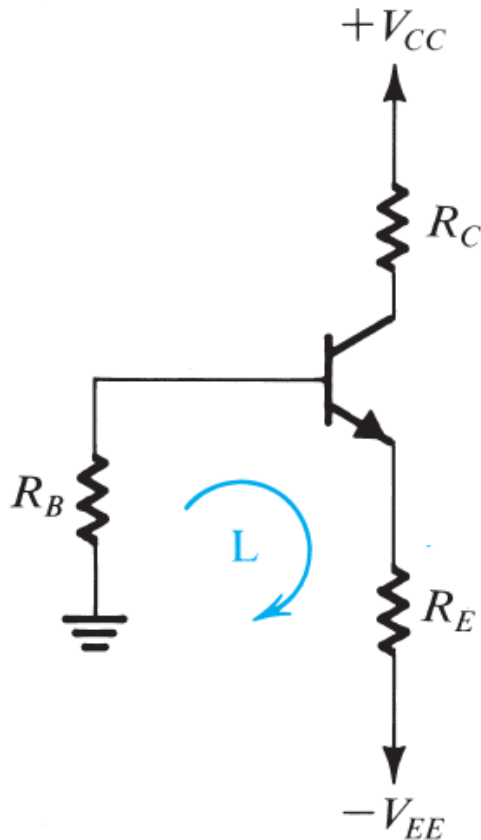

Note: The  $V_{BE}$  on these slide is equivalent to  $V_{BE(on)}$  on the slides of lecture 12 and on the handout

$$\text{KVL on loop L} \quad I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B / (\beta + 1)}$$

$$I_{CQ} = \alpha I_{EQ} = \frac{\beta}{\beta + 1} I_{EQ} \cong \frac{\beta (V_{EE} - V_{BE})}{(\beta + 1) R_E + R_B}$$

$$R_B \ll (\beta + 1) R_E \rightarrow I_{CQ} \cong \frac{\beta (V_{EE} - V_{BE})}{(\beta + 1) R_E}$$

$$\beta \gg 1 \quad \beta / (\beta + 1) \cong 1 \quad I_{CQ} \cong \frac{(V_{EE} - V_{BE})}{R_E}$$

$$V_{EE} \gg V_{BE} \quad I_{CQ} \cong \frac{V_{EE}}{R_E}$$


$$V_{EE} \gg V_{BE} \text{ \& } R_B \ll (\beta + 1) R_E$$

Condition for a bias-stable circuit against variations of temperature and  $\beta$ .

$$V_{EE} \cong \frac{V_{EE} + V_{CC}}{3} \text{ \& } R_B \cong 0.1 (\beta + 1) R_E$$

Rule of thumb

# Biassing configurations (2)

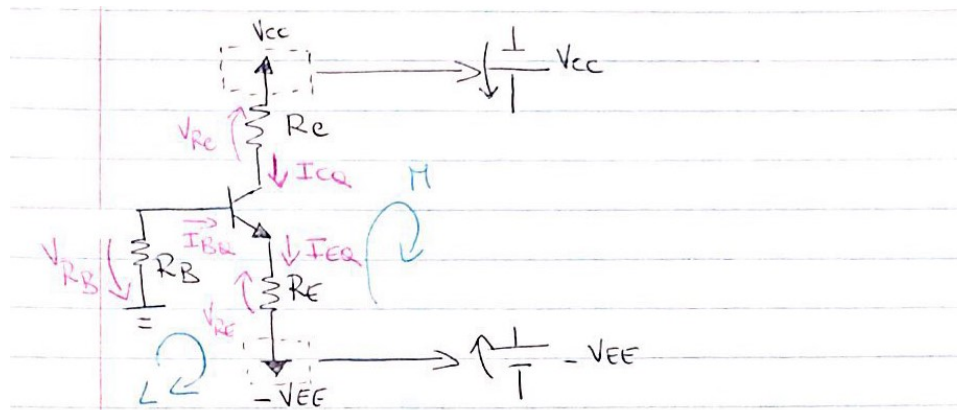

1) KVL on loop  $L$ :

$$-V_{RB} - V_{BE(on)} - V_{RE} - (-V_{EE}) = 0 \quad (1)$$

2) Using Ohm's law

$$-R_B I_{BQ} - V_{BE(on)} - R_E I_{EQ} + V_{EE} = 0 \quad (2)$$

3) Assuming that the BJT is in active mode

$$I_{BQ} = I_{EQ} / (\beta + 1) \quad (3)$$

4) Combining (3) and (2)


$$-R_B \frac{I_{EQ}}{\beta + 1} - V_{BE(on)} - R_E I_{EQ} + V_{EE} = 0 \quad (4)$$

$$I_{EQ} = \frac{V_{EE} - V_{BE(on)}}{R_E + \frac{R_B}{\beta + 1}} \quad (5)$$

$$I_{CQ} = \alpha I_{EQ} = \frac{\beta}{\beta + 1} I_{EQ} = \frac{\beta (V_{EE} - V_{BE(on)})}{R_E (\beta + 1) + R_B} \quad (6)$$
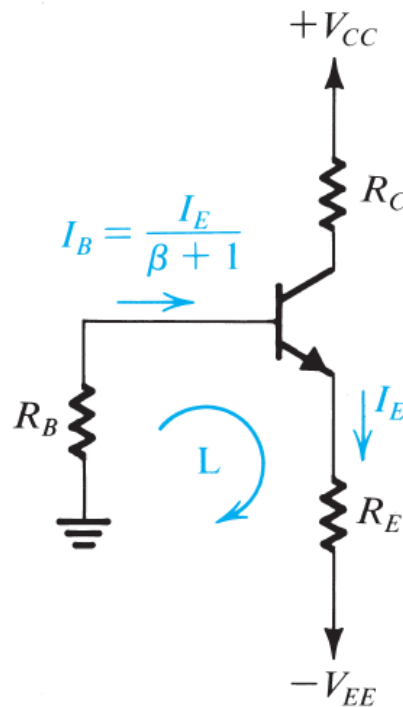
# In-class problem 1


The bias arrangement below is to be used for a common-emitter amplifier. Design the circuit to establish a DC collector current of 1mA and provide the highest possible open-circuit voltage gain while allowing a maximum signal swing of  $\pm 2$  V at the output of the amplifier. Use  $V_{CC}=10$  V and  $V_{EE}=5$  V power supplies. Assume that the peak-to-peak value of the ac signal on the emitter is  $v_{e,pp}=0.04$  V and that  $\beta=200$ . Specify where within the Q point is located (e.g. in the middle of the forward active region, close to the cut-off region or close to the saturation region).



\* See handout for solution

# Biasing configurations (3)

Loop L

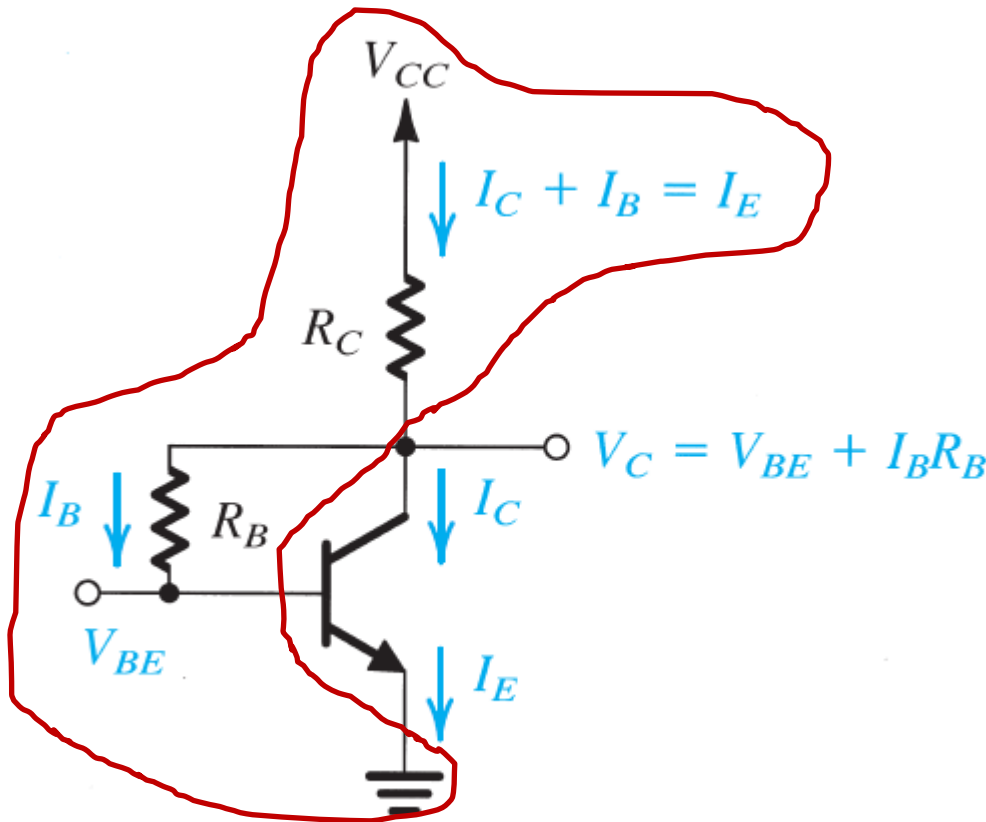

KVL on loop L

$$V_{CC} = I_E R_C + I_B R_B + V_{BE}$$

$$= I_E R_C + \frac{I_E}{\beta + 1} R_B + V_{BE}$$

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + R_B / (\beta + 1)}$$

$$R_B / (\beta + 1) \ll R_C$$

$$V_{CC} - V_{BE}$$


$$V_{CC} \gg V_{BE} \text{ \& } R_B \cong 0.1(\beta + 1) R_C$$

Condition for a bias-stable circuit against variations of temperature and  $\beta$

Note: The  $V_{BE}$  on these slide is equivalent to  $V_{BE(on)}$  on the previous slides

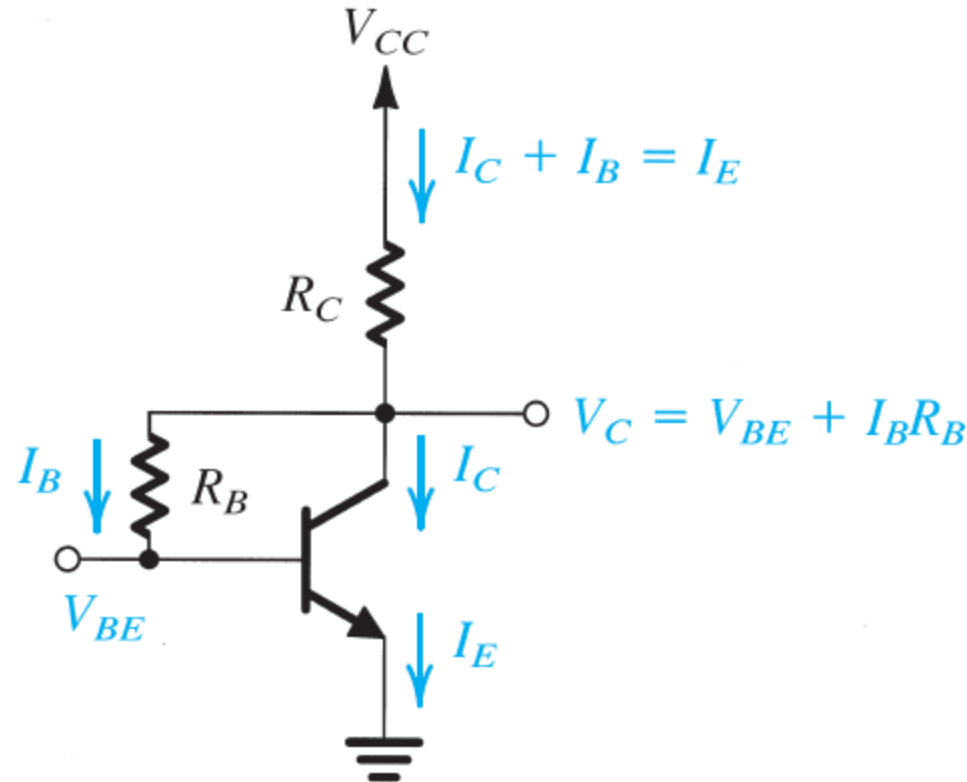
# Take-home problem 1

**D6.49** Design the circuit of Fig. 6.62 to obtain a dc emitter current of 1 mA, maximum gain, and a  $\pm 2$ -V signal swing at the collector; that is, design for  $V_{CE} = +2.3$  V. Let  $V_{CC} = 10$  V and  $\beta = 100$ .





# Take-home problem 1, solution

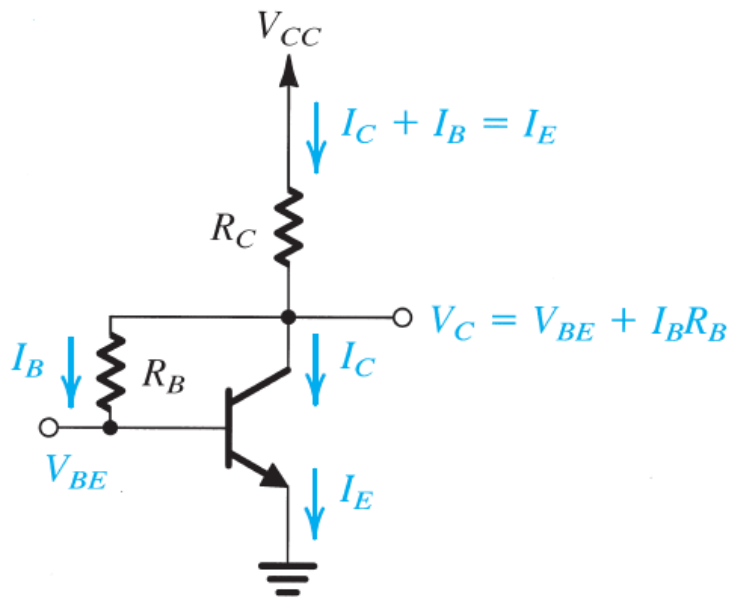

$$I_E = 1 \text{ mA} \quad |A_V| = |A_{V_{\text{max}}}| \quad \beta = 100 \quad V_{CE, \text{SAT}} = 0.3 \text{ V}$$

$$V_{CE} - 2 \text{ V} = V_{CE, \text{SAT}} \Rightarrow V_{CE} = 2.3 \text{ V} \quad I_E \approx I_C$$


$$I_E = \frac{V_{CC} - V_{CE}}{R_E} \Rightarrow R_E = \frac{7.7}{I_E} = 7.7 \text{ k}\Omega$$

$$V_{CB} = V_{CE} - V_{BE} = 2.3 - 0.7 = 1.6 \text{ V}$$

$$I_B R_B = 1.6 \text{ V} \Rightarrow \frac{I_E R_B}{\beta + 1} = 1.6 \text{ V}$$


$$R_B = \frac{101 \cdot 1.6}{1 \text{ mA}} = 160 \text{ k}\Omega$$

# Biasing configurations (4)

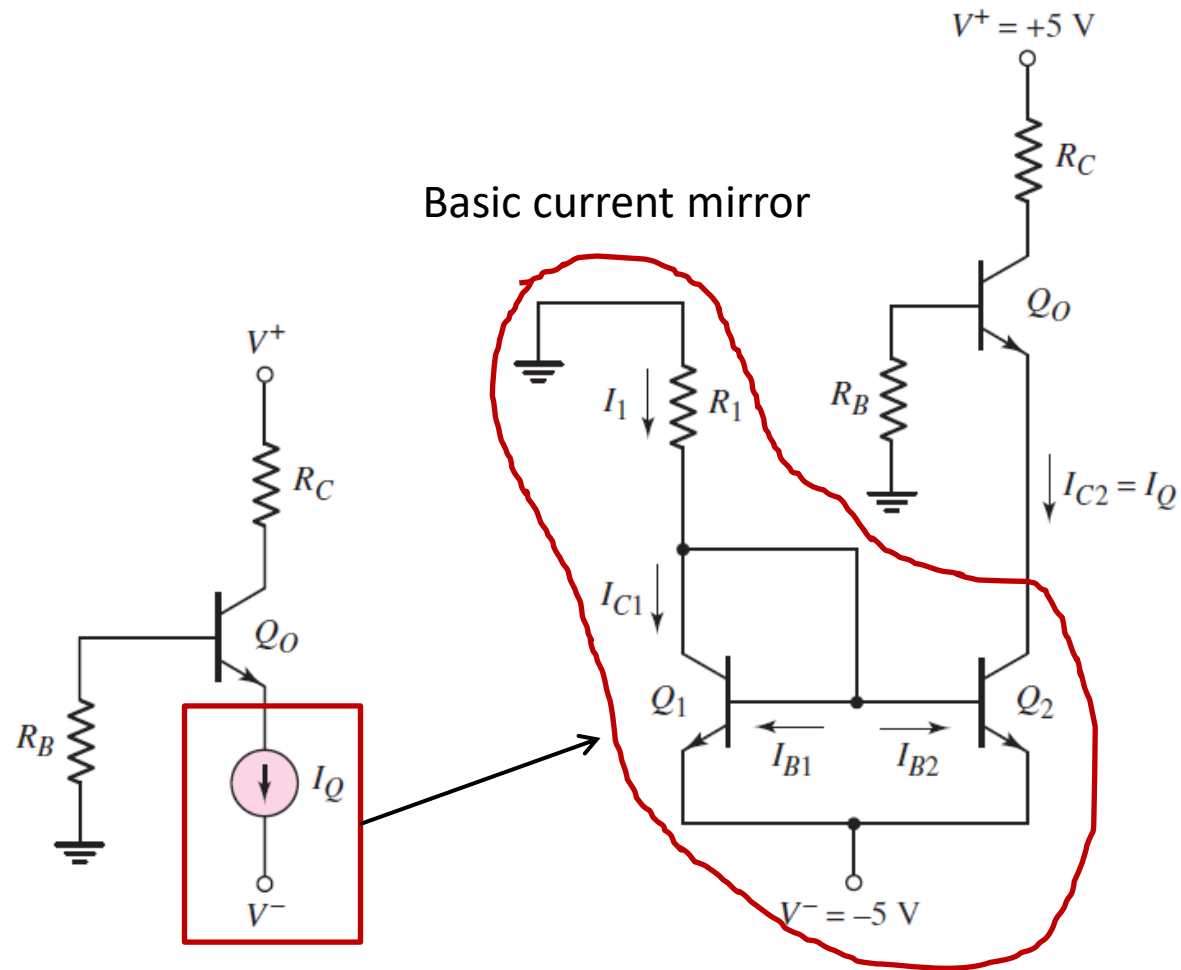

$Q_1$  and  $Q_2$  are two identical transistors held at the same temperature

# Biasing configurations (4)

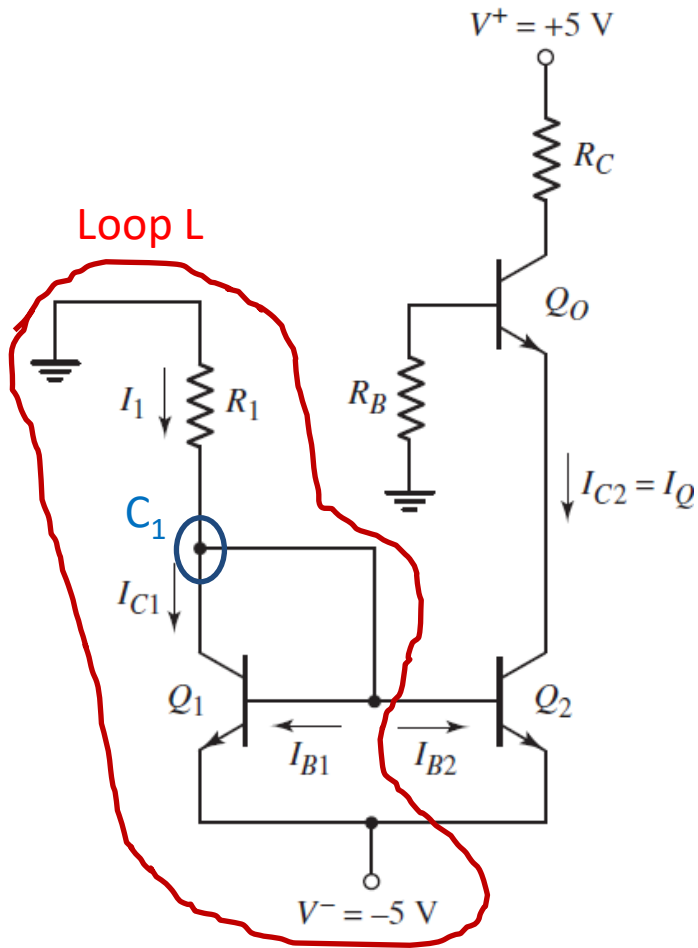

KVL at loop L  $0 = I_1 R_1 + V_{BE} \text{ (on)} + V^-$

$$I_1 = \frac{-(V^- + V_{BE}(\text{on}))}{R_1}$$


KCL at node C1  $I_1 = I_{C1} + I_{B1} + I_{B2}$

$$I_1 = I_{C1} + 2I_{B2} = I_{C2} + \frac{2I_{C2}}{\beta} = I_{C2} \left( 1 + \frac{2}{\beta} \right)$$

$$I_{C2} = I_Q = \frac{I_1}{\left(1 + \frac{2}{\beta}\right)}$$

**$Q_1$  operates in the active region since  $V_{CB}=0$  and  $(V_{CE}=V_{BE(on)}) > V_{CE,SAT}$**

# Biasing configurations (4)

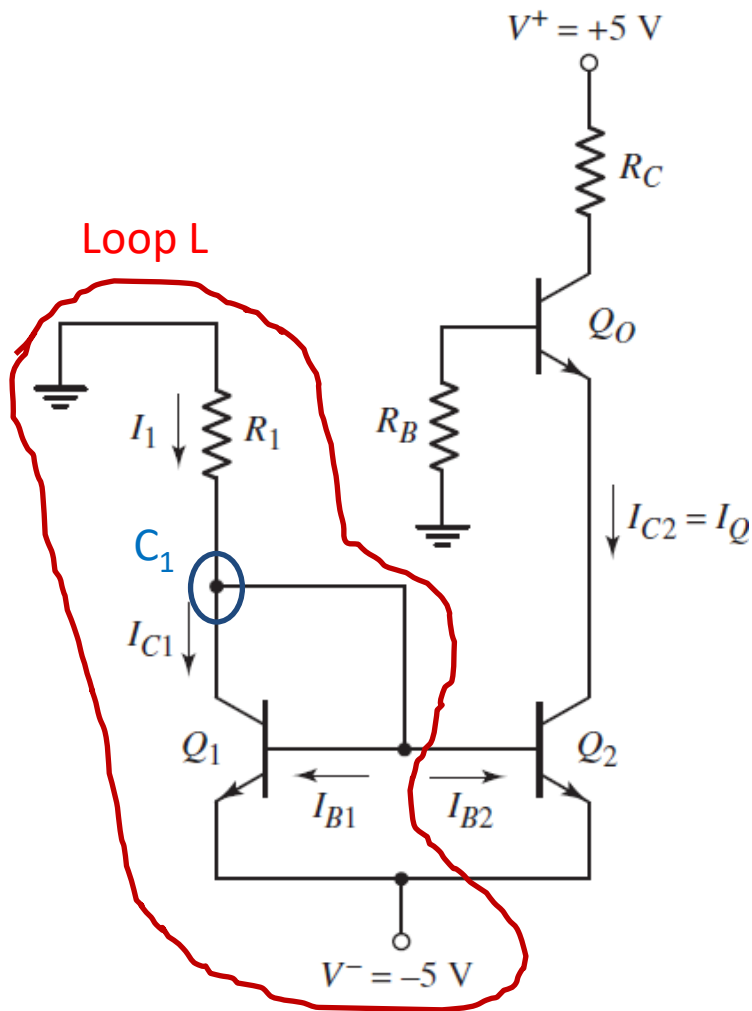


$$I_1 = \frac{-(V^- + V_{BE}(\text{on}))}{R_1}$$

$$I_{C2} = I_Q = \frac{I_1}{\left(1 + \frac{2}{\beta}\right)}$$


- For reasonable values of  $\beta$  the Q point is stable against variations of  $\beta$ .
- The Q point is also independent from  $R_B$ , hence one can select  $R_B$  to optimize the input resistance of a CE voltage amplifier.
- Biasing by a current mirror guarantees stability against variation of temperature if  $V^- \gg V_{BE}(\text{on})$ .
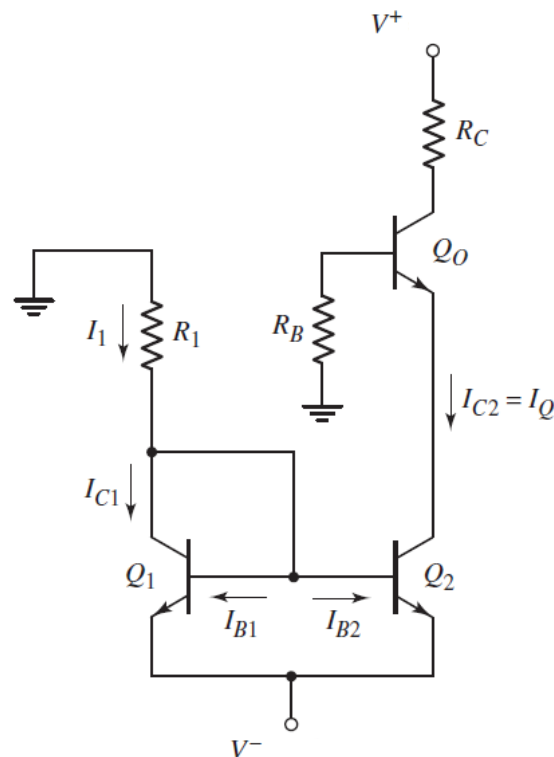
# Take-home problem 2

**Ex 5.18:** In the circuit shown in Figure 5.60, the parameters are  $V^+ = 3.3$  V,  $V^- = -3.3$  V, and  $R_B = 0$ . The transistor parameters are  $\beta = 60$  and  $V_{BE}(\text{on}) = 0.7$  V. Design the circuit such that  $I_{CQ}(Q_O) = 0.12$  mA and  $V_{CEQ}(Q_O) = 1.6$  V. What are the values of  $I_Q$  and  $I_1$ ? (Ans.  $I_Q = 0.122$  mA,  $I_1 = 0.126$  mA,  $R_1 = 20.6$  k $\Omega$ ,  $R_C = 20$  k $\Omega$ )



# Take-home problem 2, solution

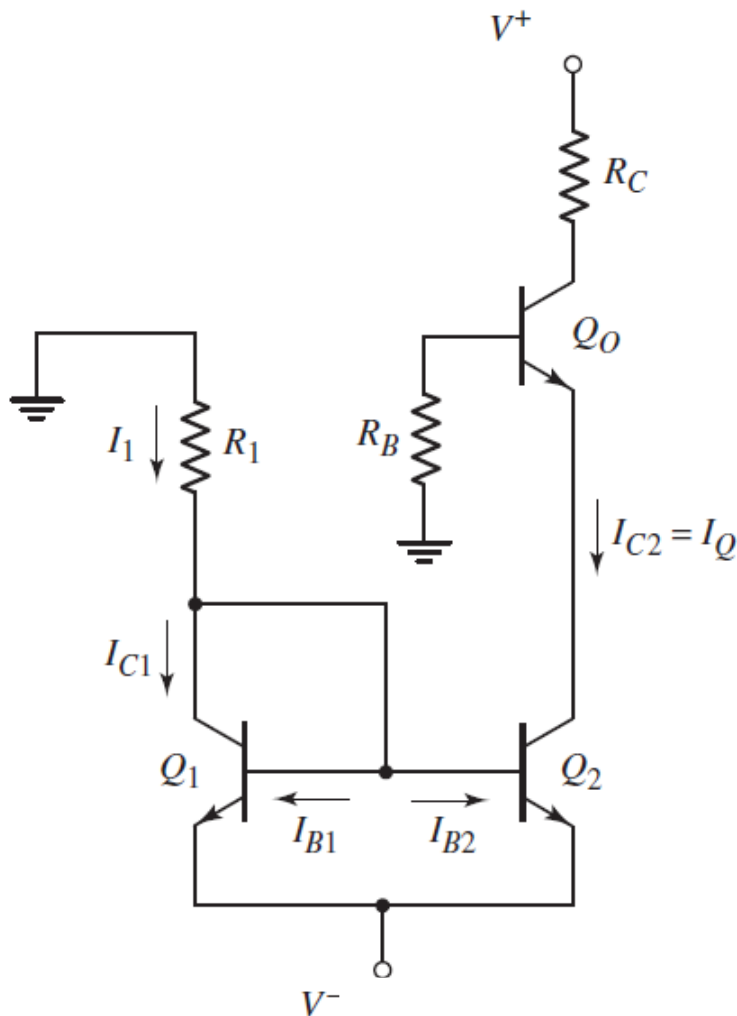

$$V_{EO} = -0.7 \text{ V}, \quad V_{CO} = -0.7 + 1.6 = 0.9 \text{ V}$$

$$R_C = \frac{V^+ - V_{CO}}{I_{CQO}} = \frac{3.3 - 0.9}{0.12} = 20 \text{ k}\Omega$$

$$I_Q = \left( \frac{1 + \beta}{\beta} \right) I_{CQO} = \left( \frac{61}{60} \right) (0.12) = 0.122 \text{ mA}$$

$$I_1 = \left( 1 + \frac{2}{\beta} \right) I_Q = \left( 1 + \frac{2}{60} \right) (0.122) = 0.126 \text{ mA}$$

$$I_1 = 0.126 = \frac{0 - V_{BE(on)} - (-3.3)}{R_1} = \frac{3.3 - 0.7}{R_1} \Rightarrow R_1 = 20.6 \text{ k}\Omega$$

# Overview of lecture 14

## ➤ Signal response of the BJT

BJT small-signal model

(Neamen From 6.2.1 to 6.2.4)

BJT amplifier configurations: overview (Neamen 6.3)

Common emitter configurations (Neamen 6.4)