



UNM LEARN

M David Kirby 5



Course Home Module 2 Take Test: Quiz 2.4



Take Test: Quiz 2.4

Test Information

Description

Instructions

Multiple Attempts This test allows multiple attempts.


Force Completion This test can be saved and resumed later.

QUESTION 1

1 points

Saved

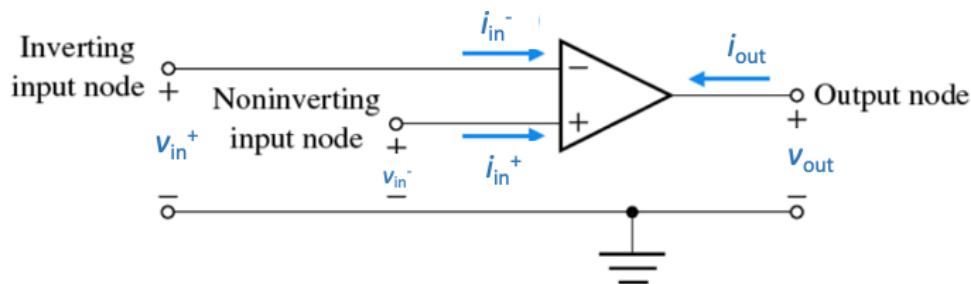Consider the ideal, inverting op-amp. Which of the following statements are correct? (More than one answer may be correct.)



☒ $v_{in}^+ = v_{in}^-$

☒ $i_{in}^+ = 0$ and $i_{in}^- = 0$

☐ $v_{in}^+ = 0$ and $v_{in}^- = 0$

☐ $i_{in}^+ = i_{in}^-$

QUESTION 2**1 points****Saved**

Which of the following describes the current-voltage relationship for a capacitor?

☒ $v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$

☐ $v(t) = C \frac{di(t)}{dt}$

☐ $v(t) = Ci(t)$

QUESTION 3**1 points****Saved**

Which of the following describes the current-voltage relationship for a resistor?

☐ $v(t) = \int_0^t \frac{1}{R} i(\tau) d\tau$

☒ $v(t) = Ri(t)$

☐ $v(t) = R \frac{di(t)}{dt}$

▼ Question Completion Status:

QUESTION 4**1 points****Saved**

Which of the following describes the current-voltage relationship for an inductor?

☐ $v(t) = L \int_0^t i(\tau) d\tau$

☐ $v(t) = Li(t)$

☒ $v(t) = L \frac{di(t)}{dt}$

Click Save and Submit to save and submit. Click Save All Answers to save all answers.

Save All Answers

Save and Submit