

ECE 322L

Electronics 2

04/14/20 - Lecture 21

Intro to power amplifiers


Power transistors

Overview

- Introduction to power amplifiers
 - Power considerations
 - Power transistors-BJT
 - Origin of current, voltage, and power rating for a transistor.
 - Safe operating area (SOA)
 - Heat transfer models from the device to the ambient.
- (Neamen 6.10, 8.1, 8.2.1, 8.2.4-S&S, 6th edition, 11.7)

Power Amplifiers

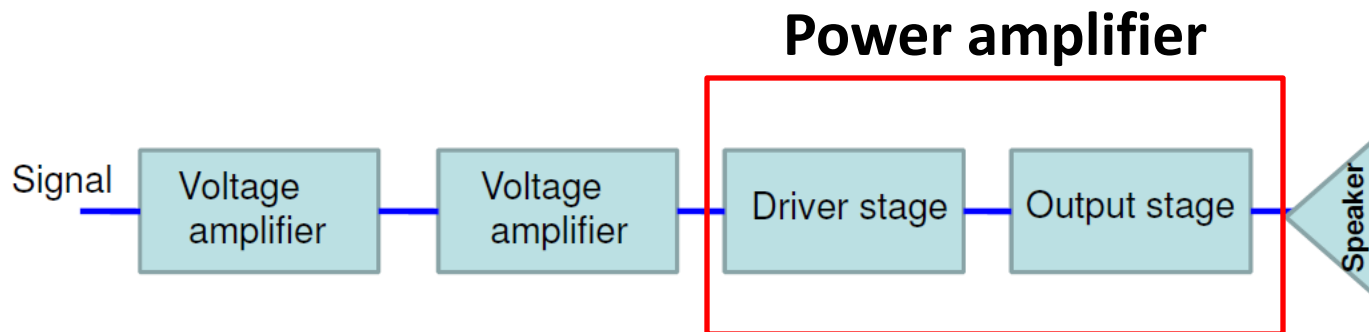- Large-signal amplifiers
- Generally the last stage of a multistage amplifier.
- The function of a practical power amplifier is to deliver high power to an output device, such as a loud speaker.
- Typical output power rating of a power amplifier will be 1W or higher. The schematic diagram of a multi-stage amplifier utilizing a power amplifier is shown below



Desired functionalities of a power amplifier

- Capability to deliver a high level of power to the load without loss of gain and maintaining a linear transfer function.
- Limit power dissipation, i.e., efficiently deliver power to the load.
- Capability to handle large voltage and current.


Power transistor-BJT

Power transistors are used to sustain the high output voltage and current.

Physical structure;

- Large emitter area to handle large current densities
- Narrow emitter width to minimize parasitic base resistance

Cross-sectional view

 

Power transistor-BJT

Large-area devices – the geometry and doping concentration are different from those of small-signal transistors

Examples of BJT rating:

Parameter	Small-signal BJT (2N2222A)	Power BJT (2N3055)	Power BJT (2N6078)
V_{CE} (max) (V)	40	60	250
I_C (max) (A)	0.8	15	7
P_D (max) (W)	1.2	115	45
β	35 – 100	5 – 20	12 – 70
f_T (MHz)	300	0.8	1

Transistor rating

Power transistors need to withstand high levels of voltage, current, and power. Hence, it is important to understand what determines transistors ratings.

A transistor is characterized by three limitations

- Maximum rated current
- Maximum rated voltage
- Maximum rated power.

These three limitations define a safe operating area (SOA) for a transistor



Current rating

The maximum rated collector current, $I_{C(\text{rated})}$ may be related to the following:

- maximum current that the wires connecting the semiconductor to the external terminals can handle
- current which leads to maximum power dissipation when the transistor is in active mode.
- the collector current at which the gain falls below a minimum specified value

Current rating

Current gain vs I_C

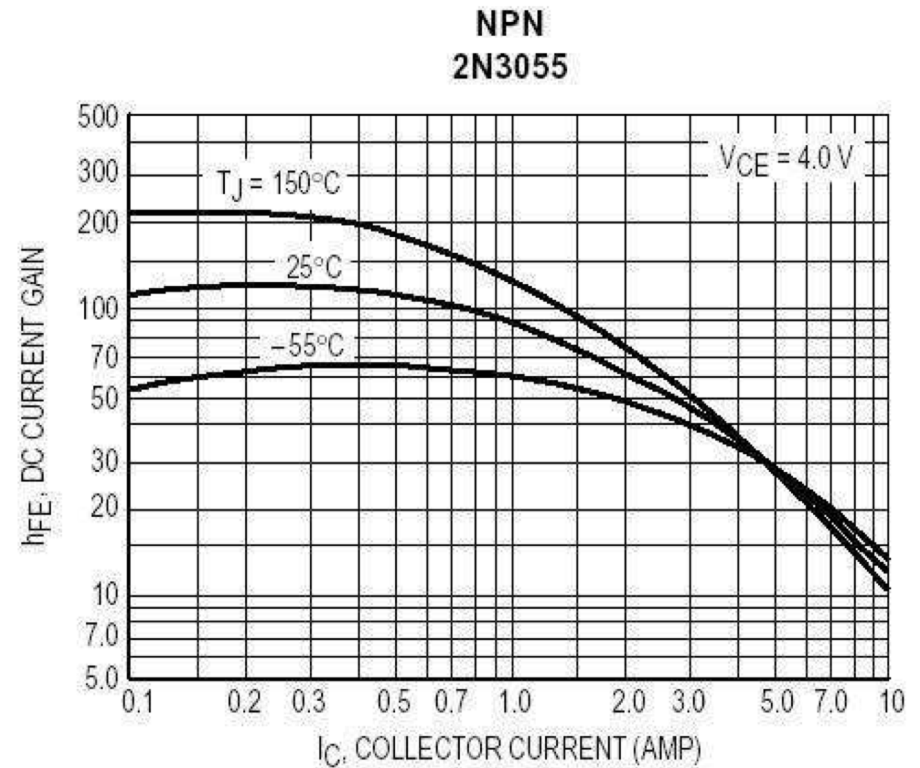 

Voltage rating

- The maximum (output) voltage limitation is determined by the onset of breakdown.
- Breakdown is a deleterious effect that occurs in the presence of high electric field.
- Causes high resistance elements to allow flow of high current.
- Typically an irreversible effect permanently damaging the element.


Avalanche Breakdown

Two types of breakdown occur in BJTs

- Avalanche breakdown in the reverse-biased base-collector junction (involves gain and breakdown at the p-n junction)
- Second breakdown – non-uniformities in current density which increase temperature in localized regions of the semiconductor.


Avalanche Breakdown

 - In reverse biased junctions a wide depletion region causes high electric field and tremendous acceleration.
- Very few electrons make it through depletion region with high velocity.
- These electrons collide with atoms in the depletion region and free more electrons (Process called Multiplication).
- Results in higher and higher current flow which cause permanent damage to the device.




Avalanche (Primary) Breakdown

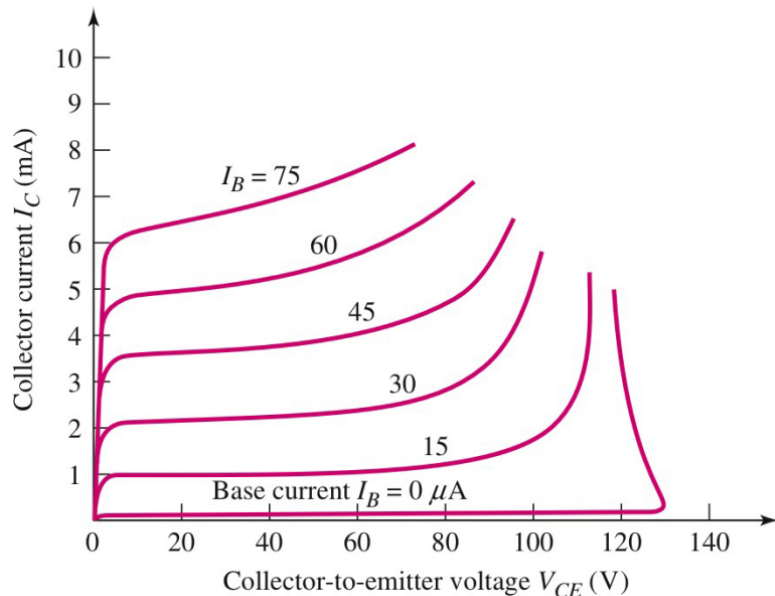- In a BJT in forward active mode the B-C junction is reverse biased. In an npn, as the V_{CE} increases, the voltage on the collector becomes significantly higher than the voltage on the base.
- A point is reached where avalanche occurs at the B-C junction.
- Thus the collector current dramatically increases.



- ✓ The breakdown voltage when the base terminal is open-circuited ($I_B=0$) is V_{CEO} , approx. 130V
- ✓ All the curves tend to merge to the same collector-emitter voltage, denoted as $V_{CE(sus)}$ once breakdown has occurred.
- ✓ $V_{CE(sus)}$ is the voltage necessary to sustain the transistor in breakdown.

Second-breakdown

 

Second-Breakdown occurs because current flow across the emitter–base junction is not uniform. Rather, the current density is greatest near the periphery of the junction (**current crowding**).

Second-Breakdown

- Locally dissipated power and hence temperature rise (at locations called **hot spots**).
- Since a temperature rise causes an increase in current, a localized form of **thermal runaway** can occur, leading to junction destruction.
- Thermal Runaway: Increase in temperature leads to higher current and power dissipation, which in turn increases the temperature further until the device is destroyed.

Dissipate power in a BJT

The average power dissipated in a BJT must be kept below a specified maximum value to ensure that the temperature of the device does not exceed the maximum allowable value.


The maximum rated power, P_T

$$P_T = V_{CE} I_C$$

The power handling ability of a BJT is limited by two factors, i.e. the maximum **junction temperature**, T_{Jmax} that the BJT can be operated at and **second-breakdown**.


Safe operating area (SOA)

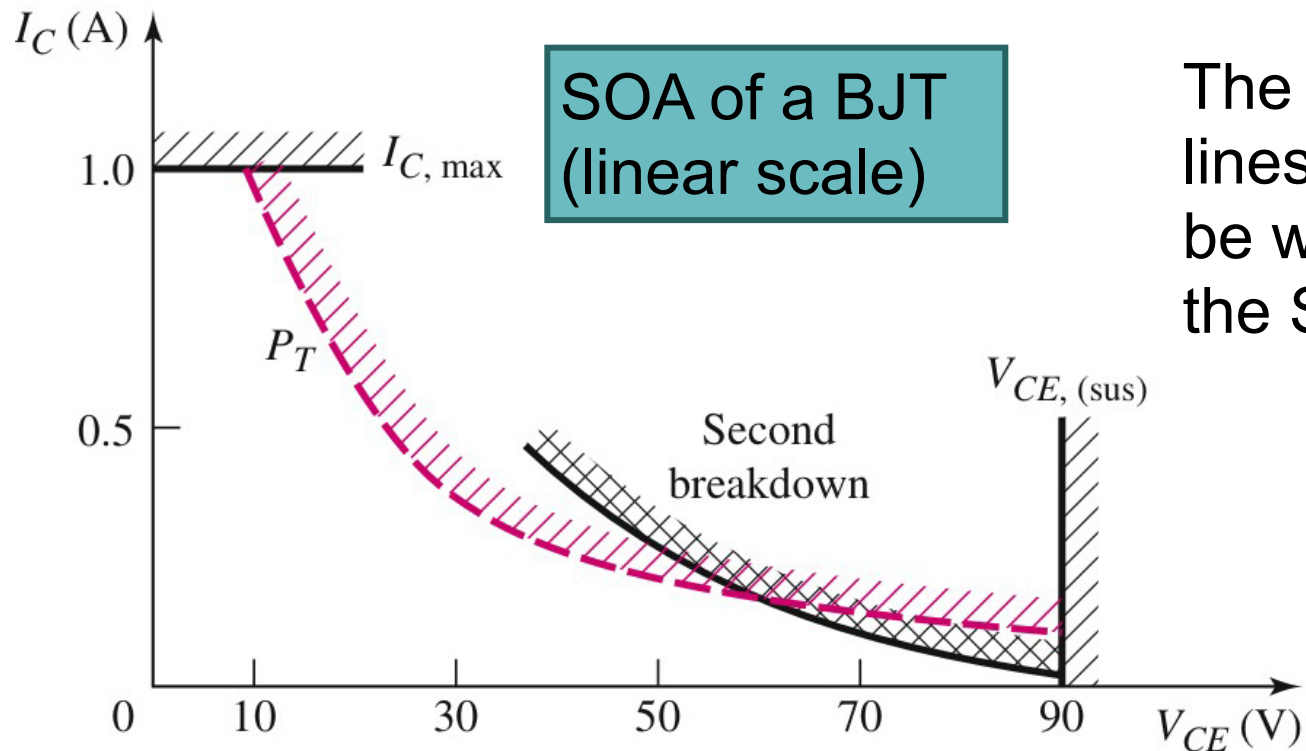The safe operating area (SOA) is **bounded by** $I_{C(\max)}$; $V_{CE(sus)}$ and maximum rated power curve, P_T and the transistor's second breakdown characteristics curve.





The load lines must be within the SOA

Safe operating area (SOA)

 

In-class problem 1

  Determine the required DC ratings (current, voltage and power) of the BJT.




In-class problem 1, solution

For $V_{CE} \cong 0$ the maximum collector current;

$$I_{C(\max)} = \frac{V_{CC}}{R_L} = \frac{24}{8} = 3 \text{ A}$$

For $I_C = 0$ the maximum collector-emitter voltage;


$$V_{CE(\max)} = V_{CC} = 24 \text{ V}$$

 

In-class problem 1, solution

$$P_T = V_{CE} I_C = (V_{CC} - I_C R_L) I_C = V_{CC} I_C - I_C^2 R_L$$


The maximum power occurs when $\frac{dP_T}{dI_C} = 0$

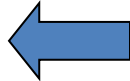i.e. when $V_{CC} - 2I_C R_L = 0$  Differentiating

or when $I_C = 1.5 \text{ A}$

At this point; $V_{CE} = V_{CC} - I_C R_L = 12 \text{ V}$

and; $P_T = V_{CE} I_C = 18 \text{ W}$

 

In-class problem 1, solution

Thus the transistor ratings are;

$$I_{C(\max)} = 3 \text{ A}$$
$$V_{CE(\max)} = 24 \text{ V}$$
$$P_T = 18 \text{ W}$$


In practice, to find a suitable transistor for a given application, safety factors are normally used. A transistor with $I_{C(\max)} > 3 \text{ A}$, $V_{CE(\max)} > 24 \text{ V}$, $P_T > 18 \text{ W}$ will be required.

In-class problem 1, solution

The load line equation is;

$$V_{CE} = V_{CC} - I_C R_L$$

The load line must be within the SOA

 

Take-home problem 1

The common-emitter circuit in Figure P8.2 is biased at $V_{CC} = 24$ V. The maximum transistor power is rated at $P_{Q,\max} = 25$ W. The other parameters of the transistor are $\beta = 60$ and $V_{BE}(\text{on}) = 0.7$ V. (a) Determine R_L and R_B such that the transistor is biased at the maximum power point. (b) For $V_p = 12$ mV, determine the average power dissipated in the transistor.

 


Figure P8.2

Take-home problem 1, solution

8.2

$$(a) \quad P_{Q,\max} = V_{CEQ} \cdot I_{CQ}$$

$$25 = \left(\frac{24}{2} \right) \cdot I_{CQ} \Rightarrow I_{CQ} = 2.083 \text{ A}$$

$$R_L = \frac{24 - 12}{2.083} = 5.76 \, \Omega$$

$$I_{BQ} = \frac{2.083}{60} = 0.03472 \text{ A}$$

$$R_B = \frac{24 - 0.7}{0.03472} = 671 \, \Omega$$

$$(b) \quad r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(60)(0.026)}{2.083} = 0.7489 \, \Omega$$

$$I_b = \frac{V_p}{r_\pi} = \frac{12 \text{ mV}}{0.7489} = 16.02 \text{ mA}$$

$$I_c = \beta I_b = (60)(0.01602) = 0.9614 \text{ A}$$

$$\overline{P}_{avg} = \frac{1}{2} I_c^2 R_c = \frac{1}{2} (0.9614)^2 (5.76) = 2.66 \text{ W}$$

For the transistor,


$$P_Q = 25 - 2.66 = 22.34 \text{ W}$$

Heat Flow From Device to Ambient

Power transistors dissipate large amounts of power. The dissipated power is converted into heat, which raises the junction temperature. However, the junction temperature T_J must not be allowed to exceed a specified maximum, $T_{J\max}$; otherwise the transistor could suffer permanent damage.

In a steady state in which the transistor is dissipating P_D watts, the temperature rise of the junction relative to the surrounding ambience can be expressed as


$$T_J - T_A = \theta_{JA} P_D$$

 

θ_{JA} : Thermal resistance between the junction and the ambient.

Power Derating Curve

 
Maximum allowable power dissipation versus ambient temperature for a BJT operated in free air. This is known as a “power-derating” curve.



$$P_{D,max} = \frac{T_{j,max} - T_A}{\theta_{jA}}$$

$$T_J - T_A = \theta_{JA} P_D$$
 
$$P_{D\max} = \frac{T_{J\max} - T_A}{\theta_{JA}}$$



A low thermal resistance is desired to efficiently remove heat from the junction, thereby increasing the power rating of the transistor

$$\theta_{JA} = \theta_{JC} + \theta_{CA}$$

$$\theta_{CA} = \theta_{CS} + \theta_{SA}$$

$$T_J - T_A = P_D (\theta_{JC} + \theta_{CS} + \theta_{SA})$$

θ_{JA} : Thermal resistance between the junction and the ambient.

θ_{JC} : Thermal resistance between the junction and the case.

θ_{CS} : Thermal resistance between the case and the heat sink.

θ_{SA} : Thermal resistance between the heat sink and the ambient.

Heat Sinks

 



Figure 8.11 Electrical equivalent circuit for heat flow from the device to the ambient

Without heat sink


$$T_{dev} - T_{amb} = P_D (\theta_{dev-case} + \theta_{case-amb})$$

With heat sink

 
$$T_{dev} - T_{amb} = P_D (\theta_{dev-case} + \theta_{case-snk} + \theta_{snk-amb})$$



(a)

 


(b)

 


(c)

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Heat Sinks

 

Examples of heat sinks

 

- (a) Tube of heat-sink compound.
- (b) Heat-sink.
- (c) TIP31 transistor.
- (d) shows the transistor smeared with heat-sink compound.
- (e) shows the transistor fitted to the heat-sink.

In-class problem 2

A BJT is specified to have $T_{j\max} = 150^\circ\text{C}$ and to be capable of dissipating maximum power as follows:

$$40 \text{ W at } T_C = 25^\circ\text{C}$$

$$2 \text{ W at } T_A = 25^\circ\text{C}$$

Above 25°C , the maximum power dissipation is to be derated linearly with $\theta_{JC} = 3.12^\circ\text{C/W}$ and $\theta_{JA} = 62.5^\circ\text{C/W}$. Find the following:

- (a) The maximum power that can be dissipated safely by this transistor when operated in free air at $T_A = 50^\circ\text{C}$.
- (b) The maximum power that can be dissipated safely by this transistor when operated at an ambient temperature of 50°C , but with a heat sink for which $\theta_{CS} = 0.5^\circ\text{C/W}$ and $\theta_{SA} = 4^\circ\text{C/W}$. Find the temperature of the case and of the heat sink.
- (c) The maximum power that can be dissipated safely if an *infinite heat sink* is used and $T_A = 50^\circ\text{C}$.

In-class problem 2, solution

(a)

$$P_{D\max} = \frac{T_{J\max} - T_A}{\theta_{JA}} = \frac{150 - 50}{62.5} = 1.6 \text{ W}$$

(b) With a heat sink, θ_{JA} becomes

$$\begin{aligned}\theta_{JA} &= \theta_{JC} + \theta_{CS} + \theta_{SA} \\ &= 3.12 + 0.5 + 4 = 7.62^\circ\text{C/W}\end{aligned}$$

Thus,

$$P_{D\max} = \frac{150 - 50}{7.62} = 13.1 \text{ W}$$

Figure 11.28 shows the thermal equivalent circuit with the various temperatures indicated.

 


Figure 11.28 Thermal equivalent circuit for Example 11.8.

- (c) An infinite heat sink, if it existed, would cause the case temperature T_C to equal the ambient temperature T_A . The infinite heat sink has $\theta_{CA} = 0$. Obviously, one cannot buy an infinite heat sink; nevertheless, this terminology is used by some manufacturers to describe the power-detrating curve of Fig. 11.27. The abscissa is then labeled T_A and the curve is called “power dissipation versus ambient temperature with an infinite heat sink.” For our example, with infinite heat sink,


$$P_{D\max} = \frac{T_{J\max} - T_A}{\theta_{JC}} = \frac{150 - 50}{3.12} = 32 \text{ W}$$

Take-home problem 2

A particular transistor is rated for a maximum power dissipation of 60 W if the case temperature is at 25 °C. Above 25 °C, the allowed power dissipation is reduced by 0.5W/°C. (a) Sketch the power derating curve. (b) What is the maximum allowed junction temperature? (c) What is the value of $\theta_{\text{dev-case}}$?

Take-home problem 2, solution

(a)

 

(b)
$$P_D = P_{D,\text{max}} - (\text{Slope})(T_j - 25)$$

At $P_D = 0$,
$$T_{j,\text{max}} = \frac{60}{0.5} + 25 \Rightarrow \underline{T_{j,\text{max}} = 145^{\circ}\text{C}}$$

(c)
$$P_{D,\text{max}} = \frac{T_{j,\text{max}} - T_{\text{case}}}{\theta_{\text{dev-amb}}} \quad \text{or} \quad \theta_{\text{dev-amb}} = \frac{145 - 25}{60} \Rightarrow \underline{\theta_{\text{dev-amb}} = 2^{\circ}\text{C}/\text{W}}$$