

ECE 322L

Electronics 2

02/25/20 - Lecture 10


Cascode Amplifiers

The Bipolar Junction Transistor

Updates and overview


- I have posted two handouts within Lecture 10 folder:
 - Handout about p-n junctions
 - Handout about the cascode amplifier.
- Cascode amplifiers (Neamen 4.8.2)
- The Bipolar Junction Transistor (BJT):
Structure, Operating regions, DC analysis,
Load lines (Neamen-From 5.1.1 to 5.1.5)

Multi-stage amplifiers

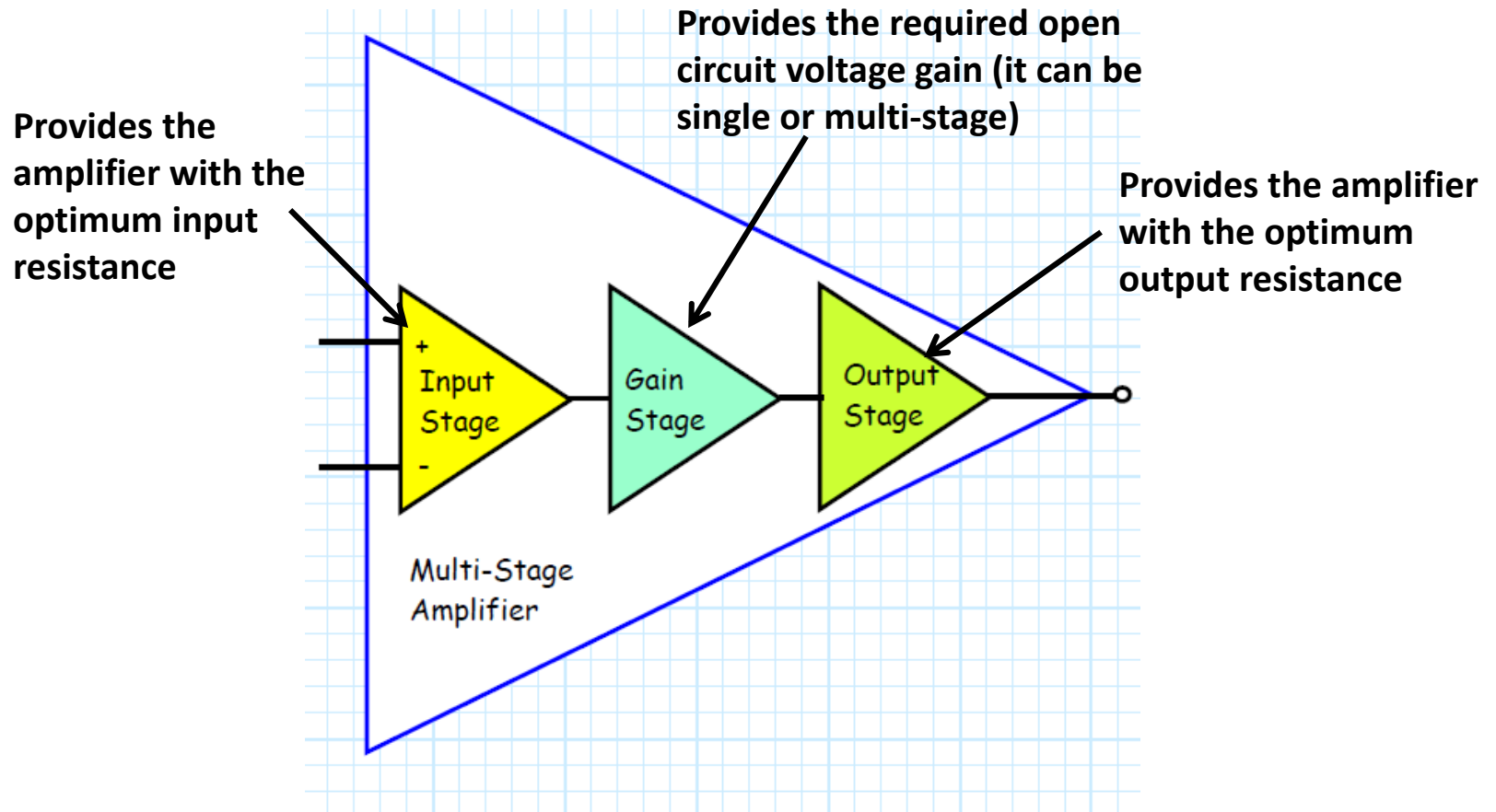


It is important to understand which basic configurations to select per each stage, and how placing two basic configurations in series affects their performance

Cascade amplifier


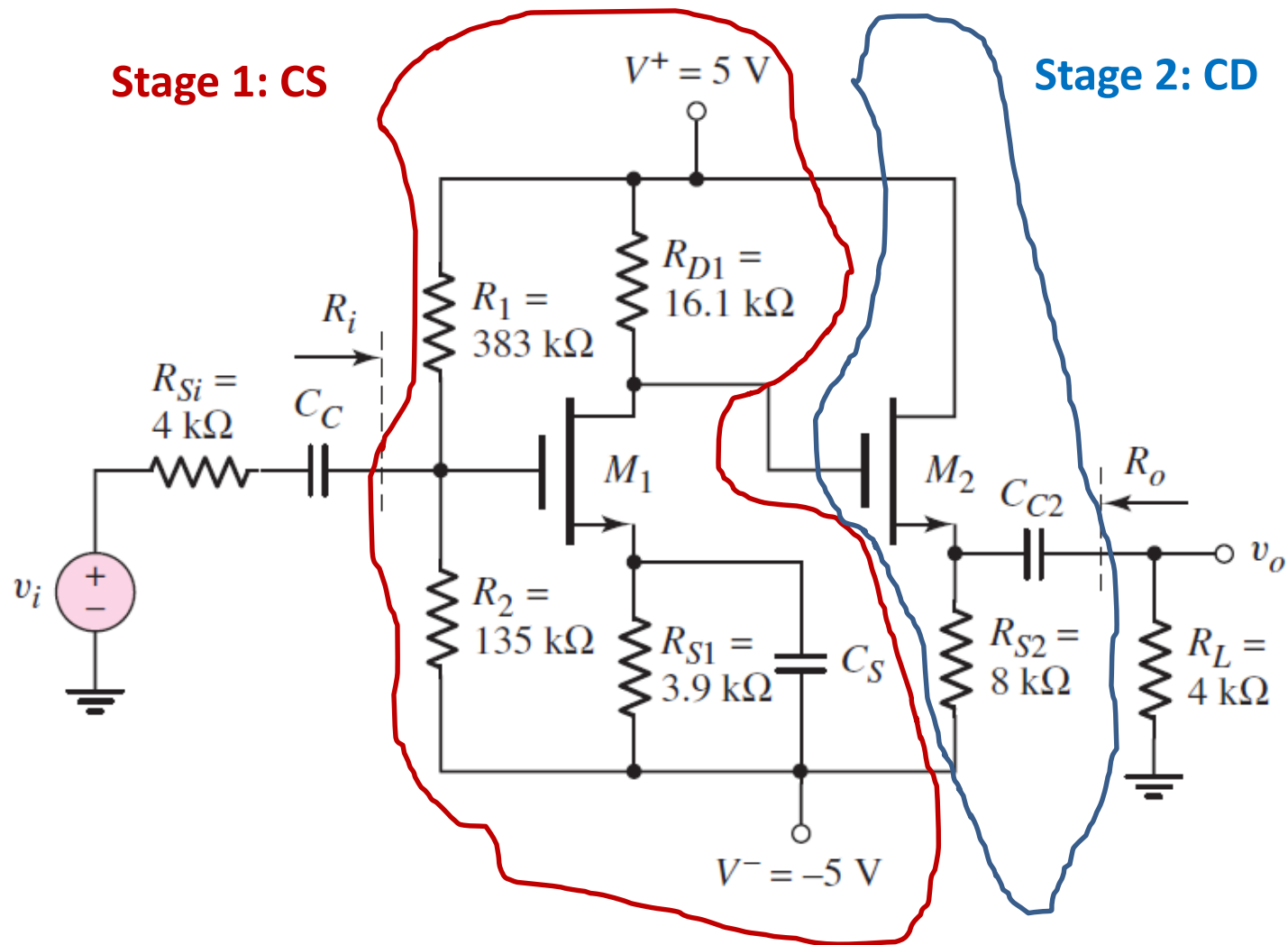


Cascode amplifier: conceptual circuit

Cascode Configuration

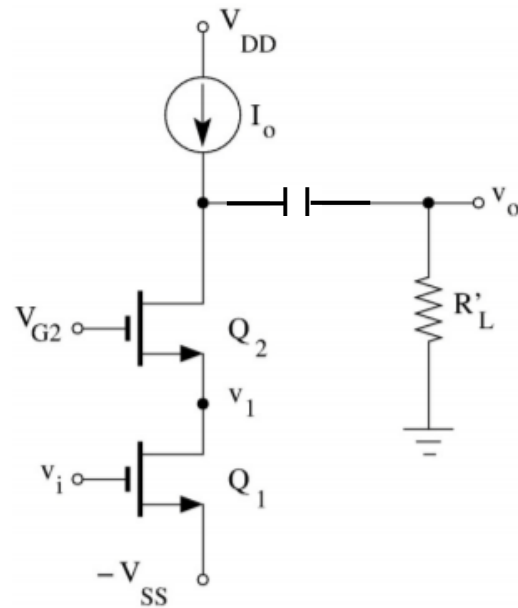


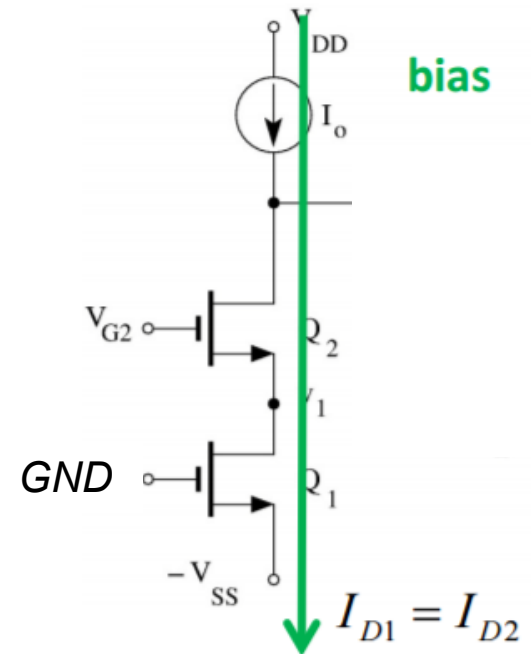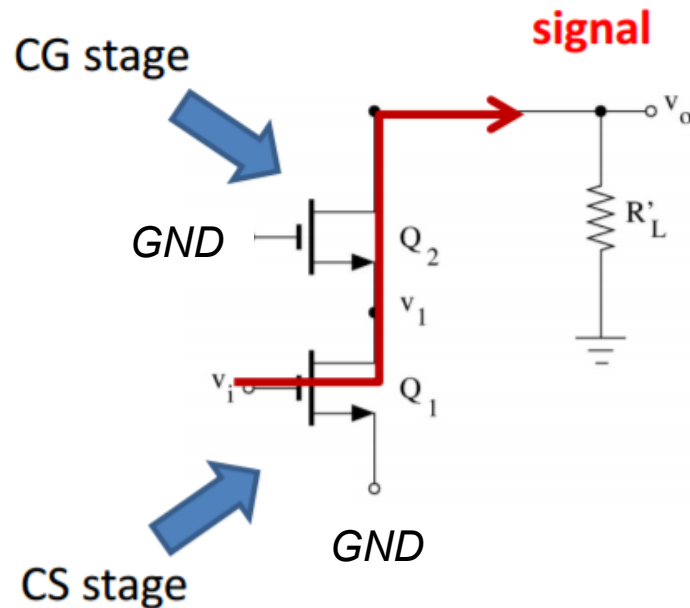Signal circuit: Current source becomes an open circuit




Cascode amplifier is a two-stage, CS-CG configuration


Cascode amplifier

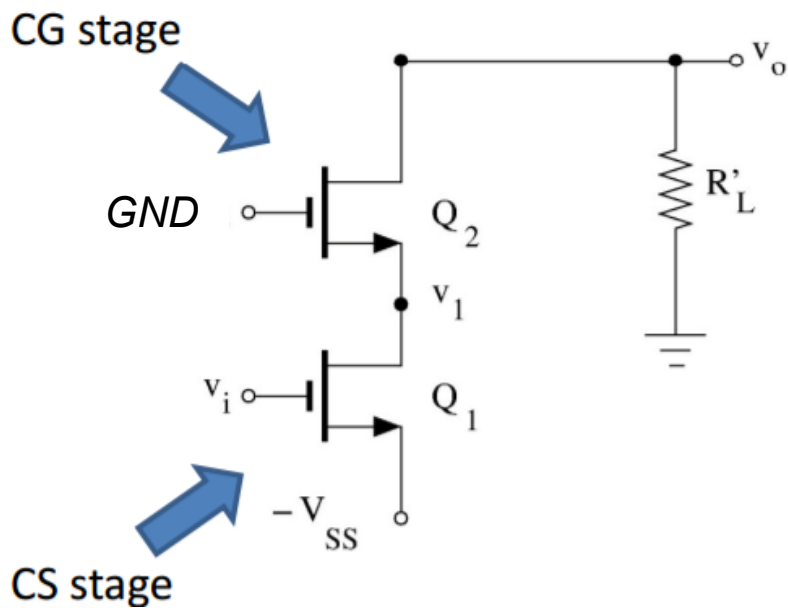

Small Signal Model

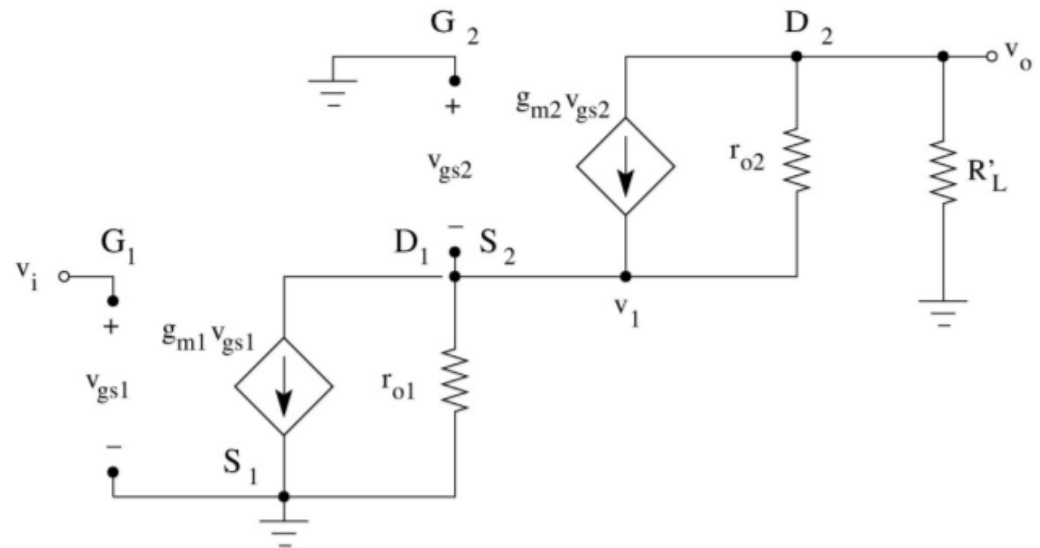

Cascode amplifier

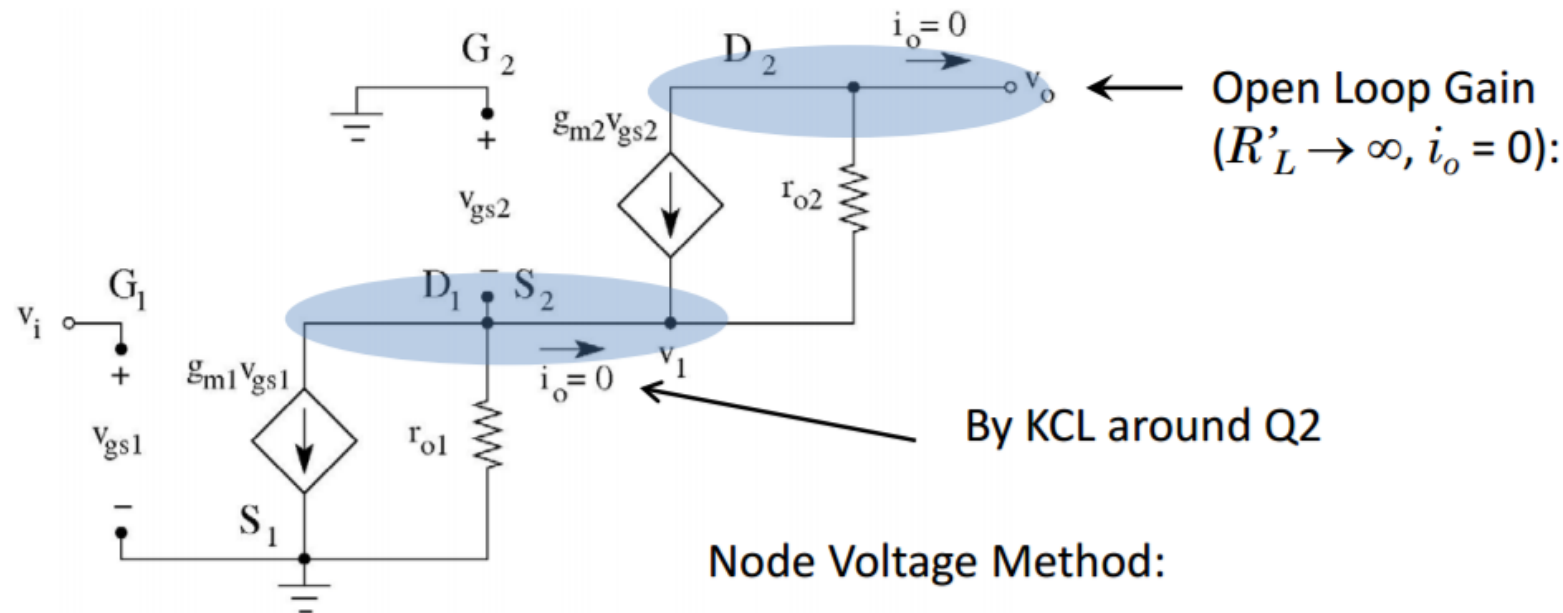

Node Voltage Method:


$$\text{Node } v_o: \quad \frac{v_o - v_1}{r_{o2}} - g_{m2}v_1 = 0 \quad \Rightarrow \quad v_o = (1 + g_{m2}r_{o2})v_1$$

$$\text{Node } v_1: \quad \frac{v_1}{r_{o1}} + g_{m1}v_i + 0 = 0 \quad \Rightarrow \quad v_1 = -g_{m1}r_{o1}v_i$$


$$A_{vo} = \frac{v_o}{v_i} = -g_{m1}r_{o1} \times (1 + g_{m2}r_{o2}) \approx -g_{m1}r_{o1}g_{m2}r_{o2}$$

Cascode amplifier

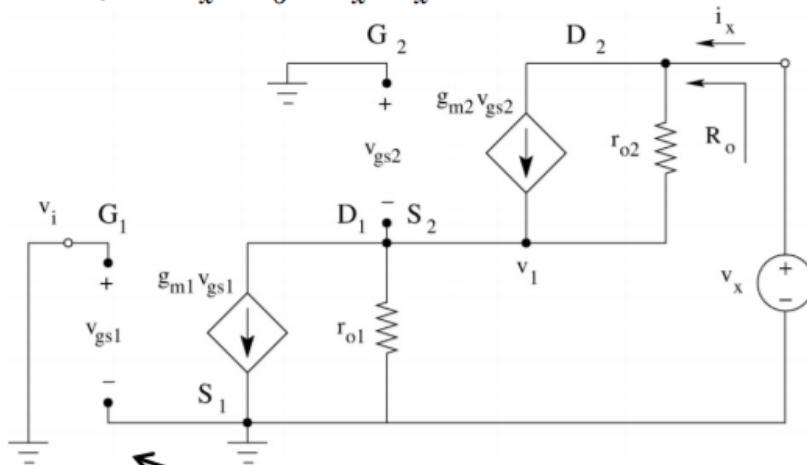Set $v_i = 0$, attach a voltage source v_x ,
compute i_x , $R_o = v_x / i_x$



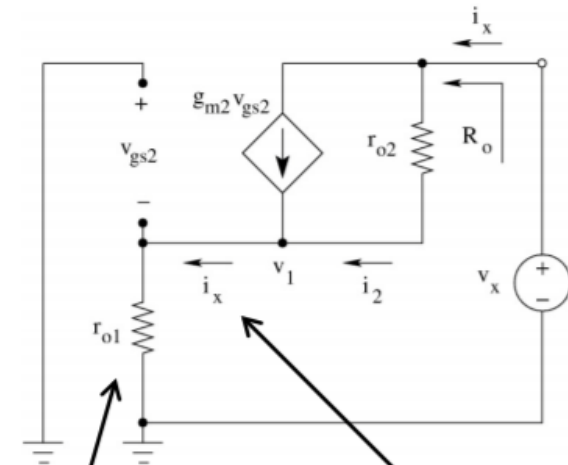$v_i = v_{gs1} = 0 \rightarrow g_{m1} v_{gs1}$ current source becomes open circuit



By KCL around Q2

$$\text{KVL : } v_{gs2} = -i_x r_{o1}$$

$$\text{KCL : } i_2 = i_x - g_{m2} v_{gs2} = i_x + i_x g_{m2} r_{o1} = i_x (1 + g_{m2} r_{o1})$$

$$\text{KVL : } v_x = i_2 r_{o2} + i_x r_{o1} = i_x (1 + g_{m2} r_{o1}) r_{o2} + i_x r_{o1}$$


$$v_x = i_x [(1 + g_{m2} r_{o1}) r_{o2} + r_{o1}]$$

$$R_o = \frac{v_x}{i_x} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}$$

$$\text{Note: } A_v = A_{vo} \times \frac{R'_L + R_o}{R'_L}$$


Cascode amplifier

CG stage

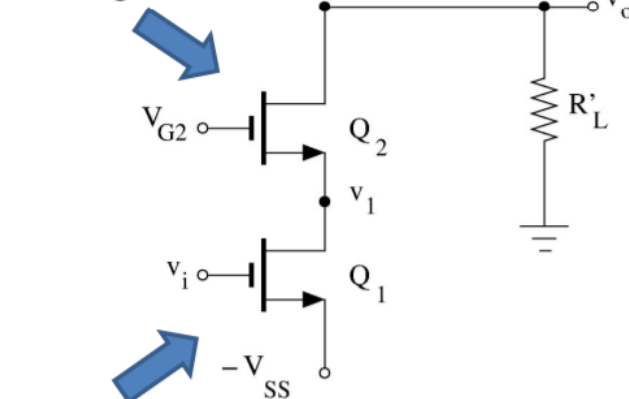

CS stage

Small Signal Model

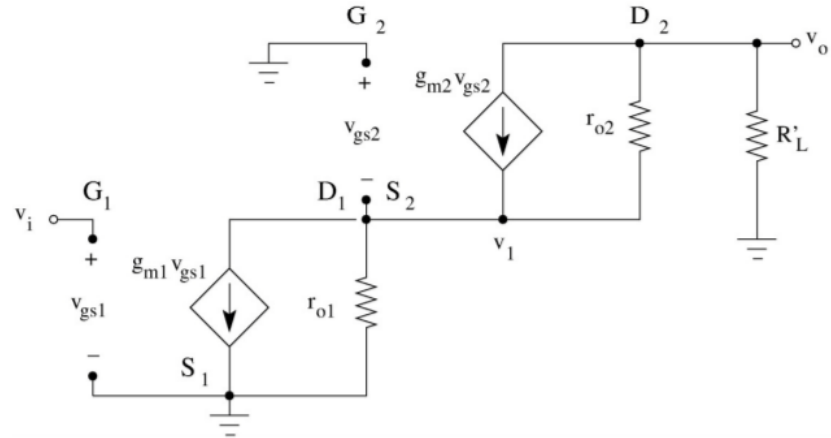

$$A_{v2} = g_{m2} (r_{o2} \parallel R'_L)$$

$$R_{L1} = R_{i2} = \frac{r_{o2} + R'_L}{1 + g_{m2} r_{o2}}$$

$$A_{v1} = -g_{m1} (r_{o1} \parallel R_{i2})$$


$$R_o \approx g_{m2} r_{o1} r_{o2}$$

For simplicity assume $r_{o1} = r_{o2} = r_o$ and $g_{m1} = g_{m2} = g_m$

$\frac{R'_L}{\infty}$	$\frac{A_{v2}(\text{CG})}{g_m r_o}$	$\frac{R_{i2} = R_{L1}}{\infty}$	$\frac{A_{v1}(\text{CS})}{-g_m r_o}$	$\frac{A_v = A_{v1} A_{v2}}{-(g_m r_o)^2}$
				Max. Gain

*The cascode provides a high gain to large loads (i.e., loads that are comparable to or larger than r_o). Later on we'll see that the cascode configuration provides a high bandwidth.


Cascode amplifier: practical circuit

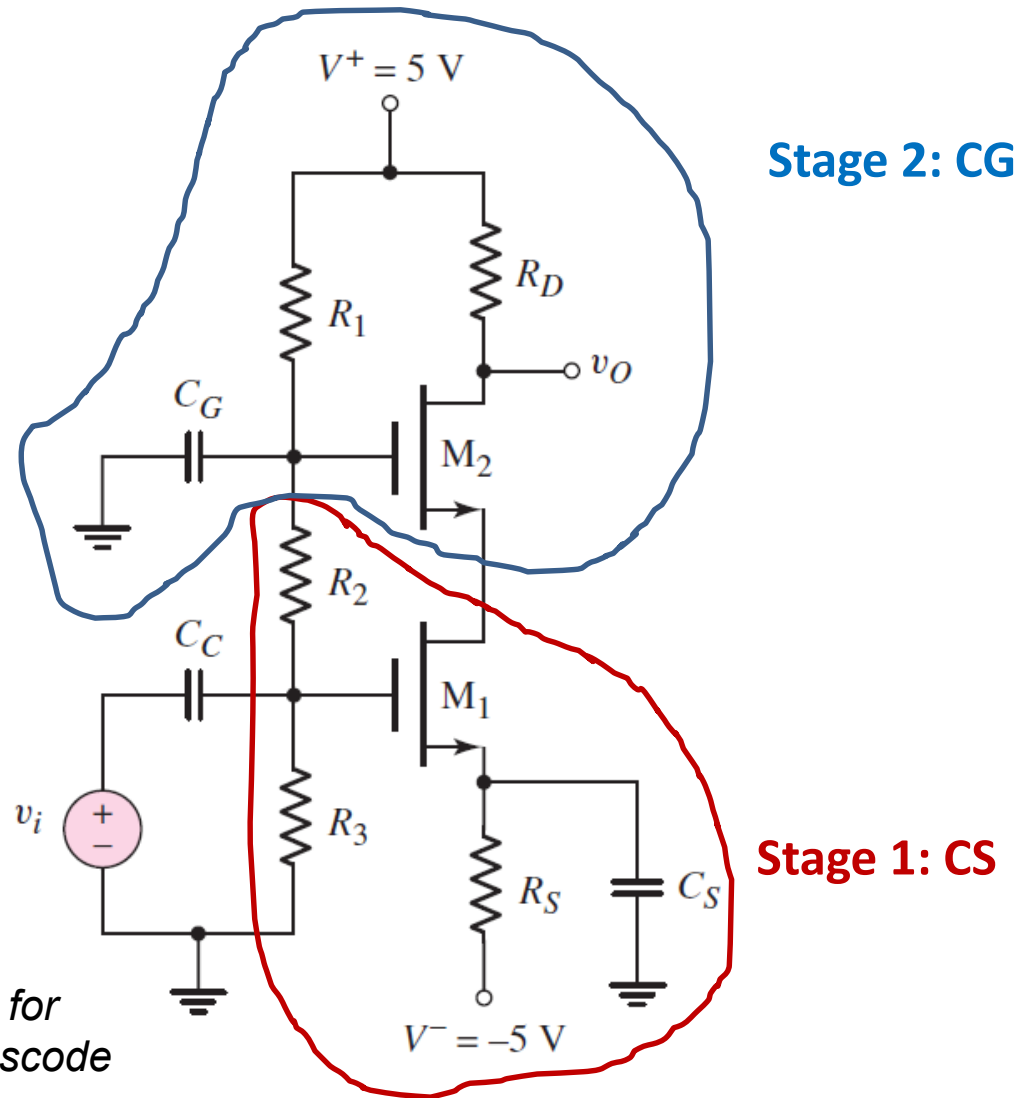

**See handout in Lec 10 folder for additional details about the cascode circuit analysis.*


Take-home problem 1

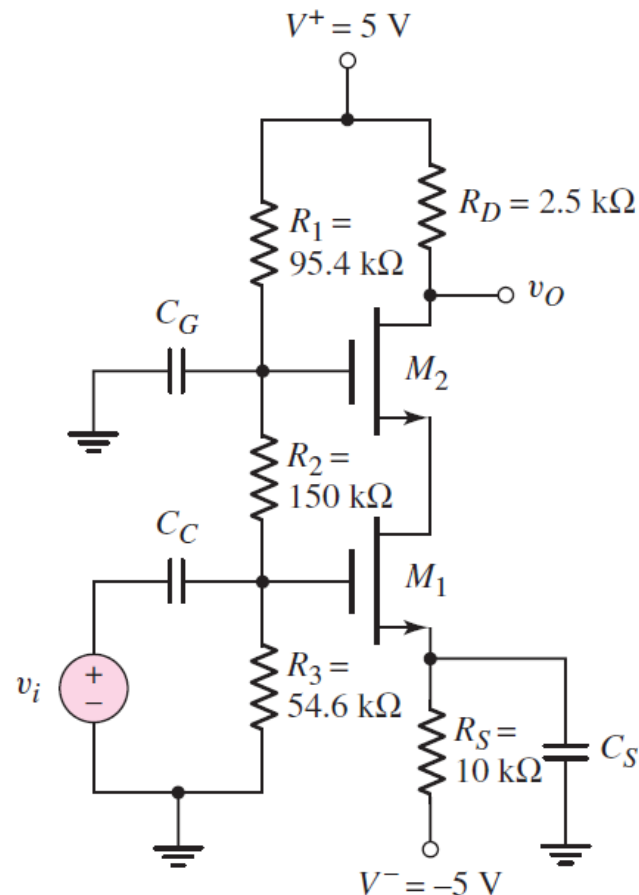The transistor parameters of the NMOS cascode circuit below are $V_{TN1}=V_{TN2}=0.8$ V, $K_{n1}=K_{n2}=3$ mA/V², $\lambda_1=\lambda_2=0.02$ V⁻¹. The coordinates of the Q point are the following: $I_{DQ}=0.471$ mA, $V_{DSQ1}=2.5$ V, $V_{DSQ2}=1.61$ V. Calculate the small-signal voltage gain of stage 1 and 2 when isolated and when connected.




Take-home problem 1, Sol


AC CIRCUIT

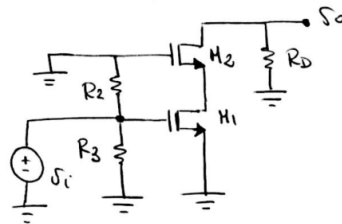

SMALL-SIGNAL MODEL (I)

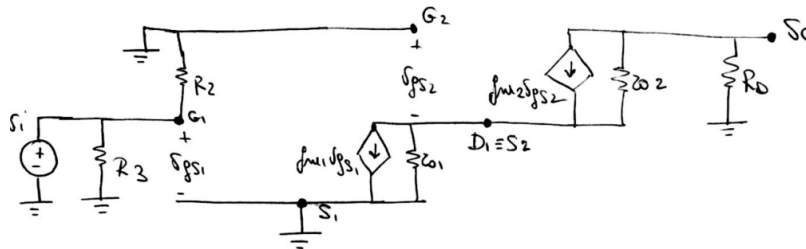

SMALL-SIGNAL MODEL (II)

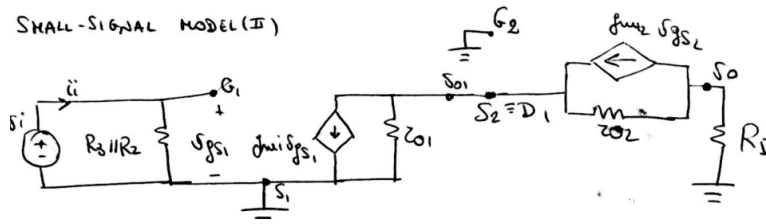

$$R_1 = \frac{v_i}{i_i} = R_3 \parallel R_2 = 40 \text{ K}\Omega$$

To calculate the gain we can replace R_D as a load and model the amplifier as a generic voltage amplifier



$$v_o = A_v v_i \frac{R_D}{R_o + R_D}$$

$$A_v = \frac{v_o}{v_i} = A_{v_o} \cdot \frac{R_D}{R_o + R_D}$$

Take-home problem 1, Sol

$$A_{Vo} = \left. \frac{v_o}{v_i} \right|_{R_D = \infty}$$

Node v_o : $\frac{v_o}{z_o} + g_{m2} v_{gs2} = 0 \quad v_{gs2} = -v_o$

$$\frac{v_o - v_{o1}}{z_o} - g_{m2} v_{o1} = 0 \Rightarrow v_o = (1 + g_{m2} z_o) v_{o1} \quad (1)$$

Node v_{o1} : $\frac{v_{o1}}{z_{o1}} + g_{m1} v_{gs1} = 0$

$$\frac{v_{o1}}{z_{o1}} + g_{m1} v_i = 0 \Rightarrow v_{o1} = -g_{m1} z_{o1} v_i \quad (2)$$

Combining (1) and (2) & obtain


$$v_o = -g_{m1} z_{o1} (1 + g_{m2} z_o) v_i$$

Hence

$$A_{Vo} = \left. \frac{v_o}{v_i} \right|_{R_D = \infty} = -g_{m1} z_{o1} (1 + g_{m2} z_o) \approx -g_{m1} g_{m2} z_{o1} z_o =$$

$$= -g_m^2 z_o^2$$

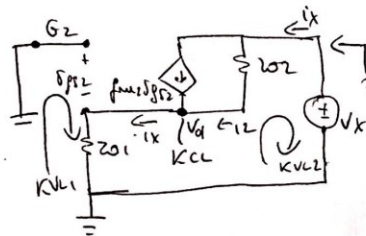To calculate the output resistance we set $v_i = 0 \Rightarrow v_{gs1} = 0 \Rightarrow g_{m1} v_{gs1} = 0$



$$R_o = \frac{v_x}{i_x}$$

KVL 1: $v_{gs2} = -i_x z_{o1}$

KCL: $i_2 = i_x - g_{m2} v_{gs2} = i_x + i_x g_{m2} z_{o1} = i_x (1 + g_{m2} z_{o1})$

KVL 2: $v_x = i_2 z_o + i_x z_{o1} =$

$$= i_x (1 + g_{m2} z_{o1}) z_o + i_x z_{o1}$$

$$R_o = i_x [(1 + g_{m2} z_{o1}) z_o + z_{o1}]$$

Take-home problem 1, Sol

$$R_o = \frac{v_x}{i_x} = z_{o1} + z_{o2} + g_{m2} z_{o1} z_{o2} \approx g_{m2} z_{o2}^2$$

$$A_v = -g_{m2} z_{o2}^2 \frac{R_D}{R_D + g_{m2} z_{o2}^2}$$



$$g_m = 2\sqrt{k_{n1,2} I_{DQ}} = 2\sqrt{3\text{mA} \cdot 0.471\text{mA}} = 2.3\text{mA/V}$$

$$z_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{0.02 \cdot 0.471\text{mA}} = 106\text{k}\Omega$$




$$A_v = - (2.3\text{mA})^2 (106\text{k})^2 \cdot \frac{2.5\text{k}}{2.5\text{k} + (2.3\text{mA})(106\text{k})^2} \approx -5.75$$

$$R_o = 25.8\text{k}\Omega$$



Bipolar junction transistor: structure

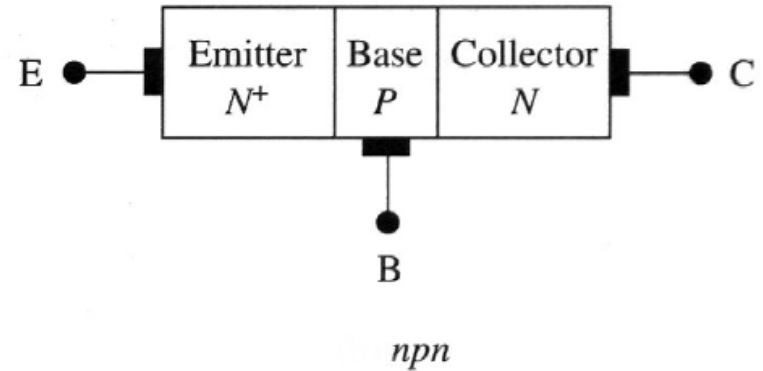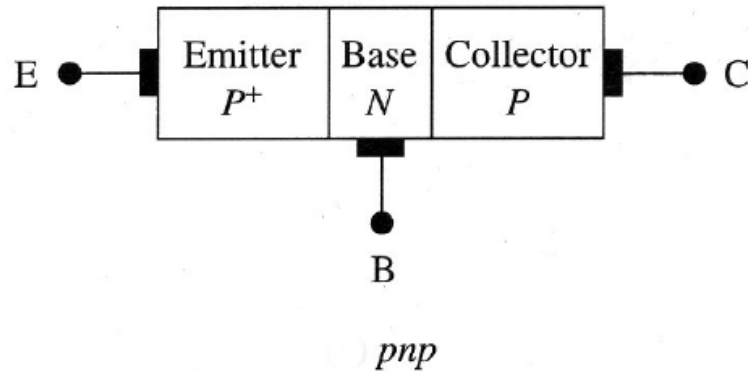

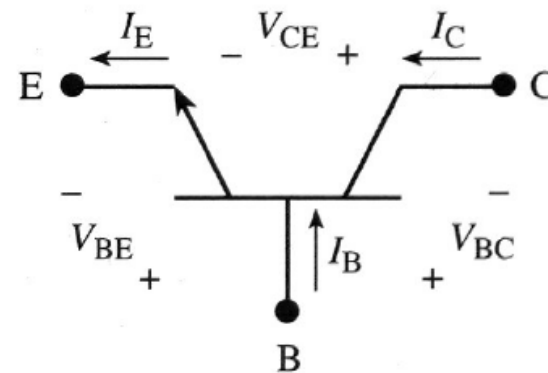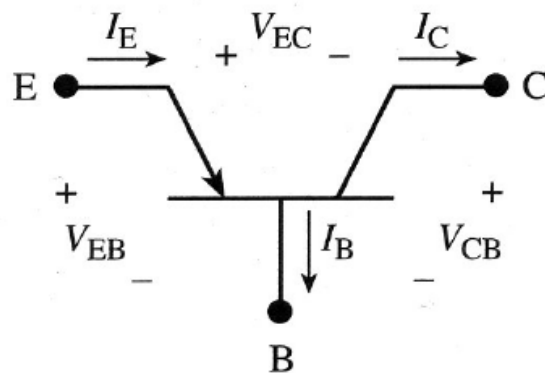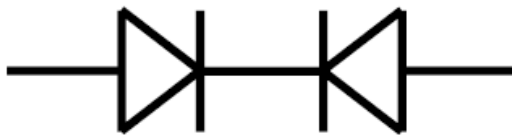Looks sort of
like two diodes
back to back



Bipolar junction transistor: structure

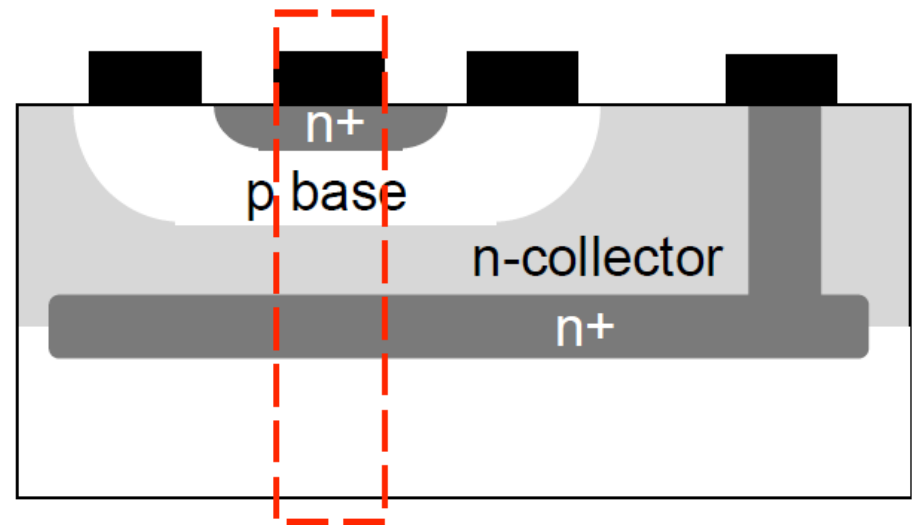
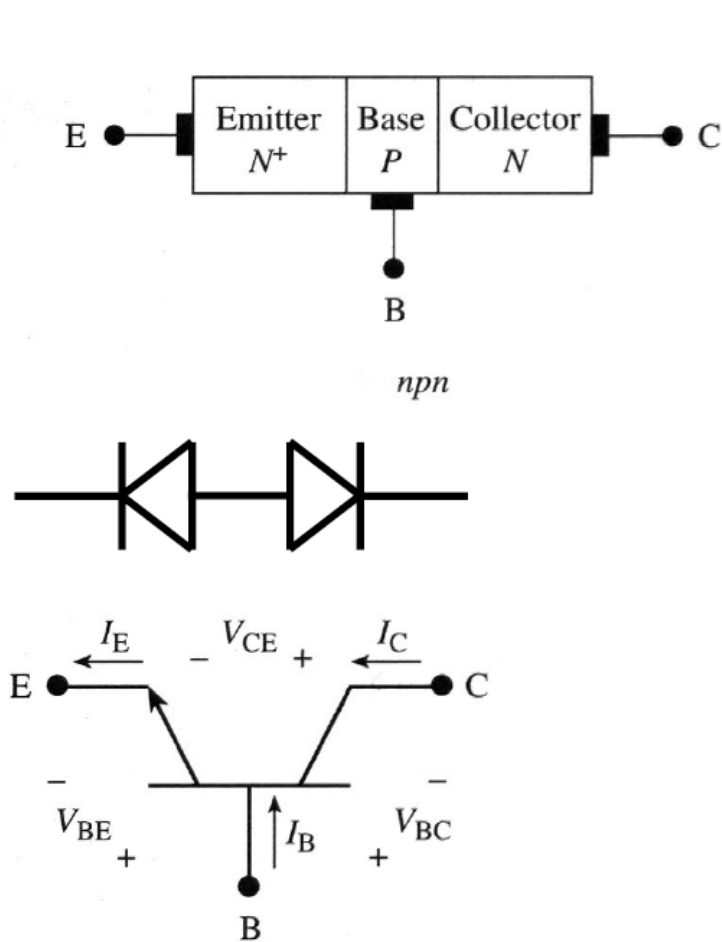


- Base is narrow ($< 10 \mu\text{m}$) so the two p-n junctions can interact ($W_B \ll L_n$).
- Doping decreases from the emitter to the collector so that switching the polarity of the two ends will lead to a drastically different behavior




W_B : Width of the quasi-neutral region in the base
 L_n : Diffusion length of minority carriers in the base

Bipolar junction transistor: operation

<i>Biasing Mode</i>	<i>Biasing Polarity E–B Junction</i>	<i>Biasing Polarity C–B Junction</i>
Saturation	Forward	Forward
Active	Forward	Reverse
Inverted	Reverse	Forward
Cutoff	Reverse	Reverse

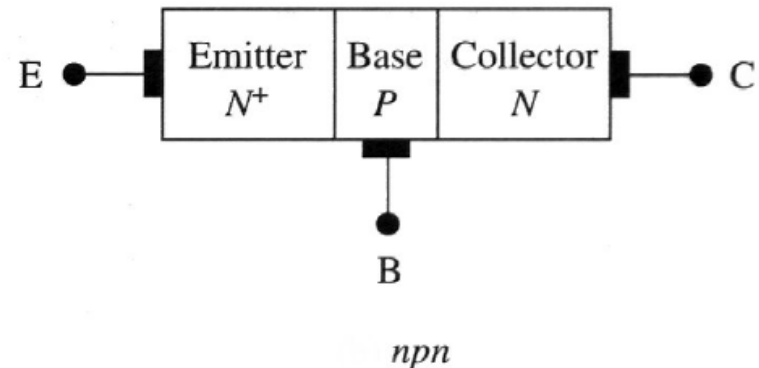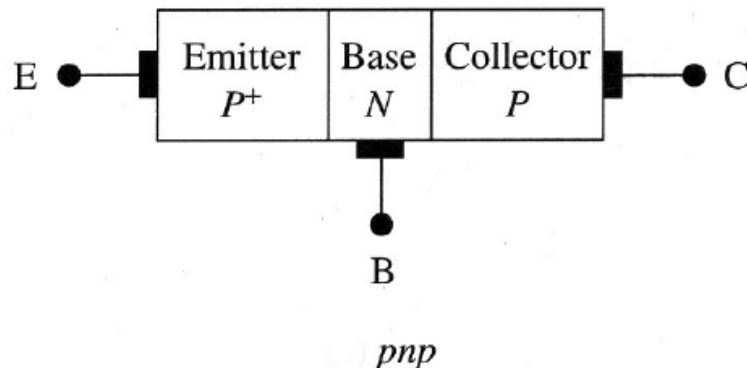


Bipolar junction transistor: operation

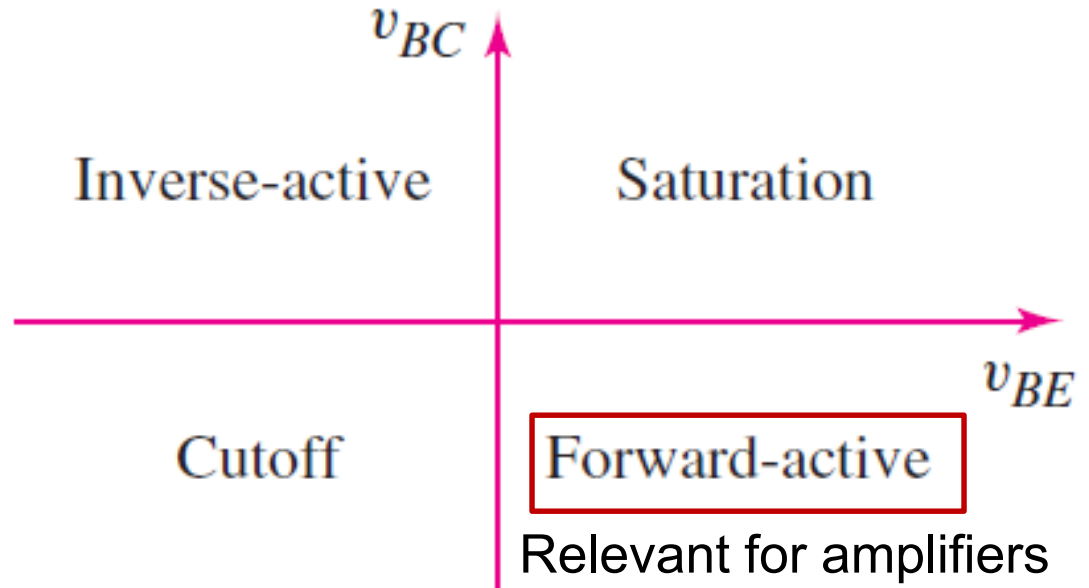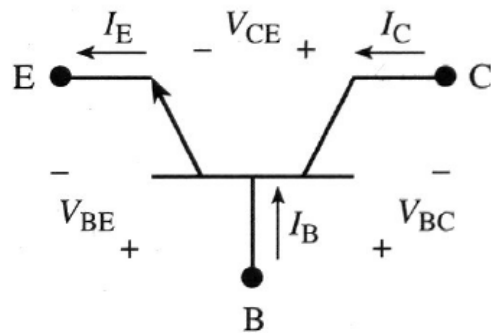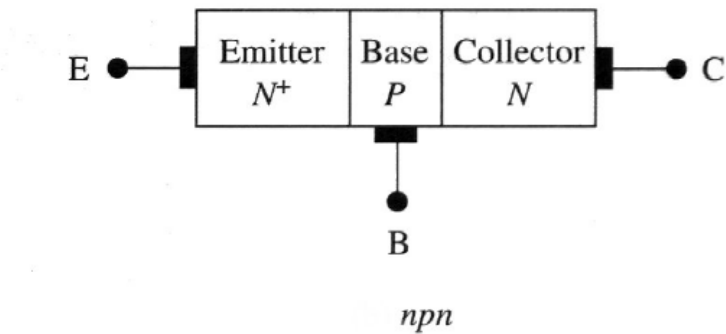

Note: Replace v_{BC} by v_{CB} and v_{BE} by v_{EB} for pnp transistor


BJT in forward-active mode

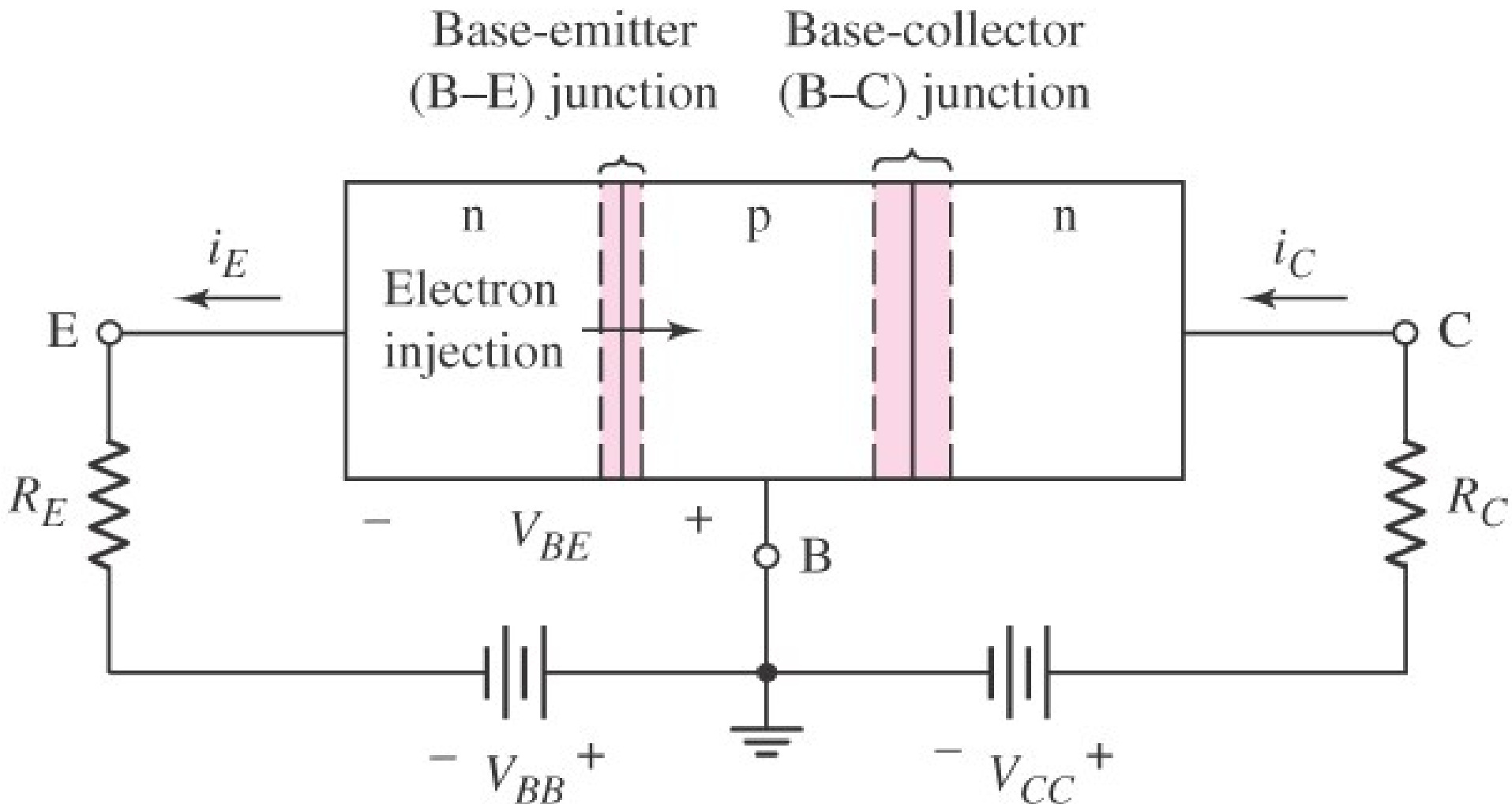Operation in forward-active region or mode



BJT in forward active mode: currents

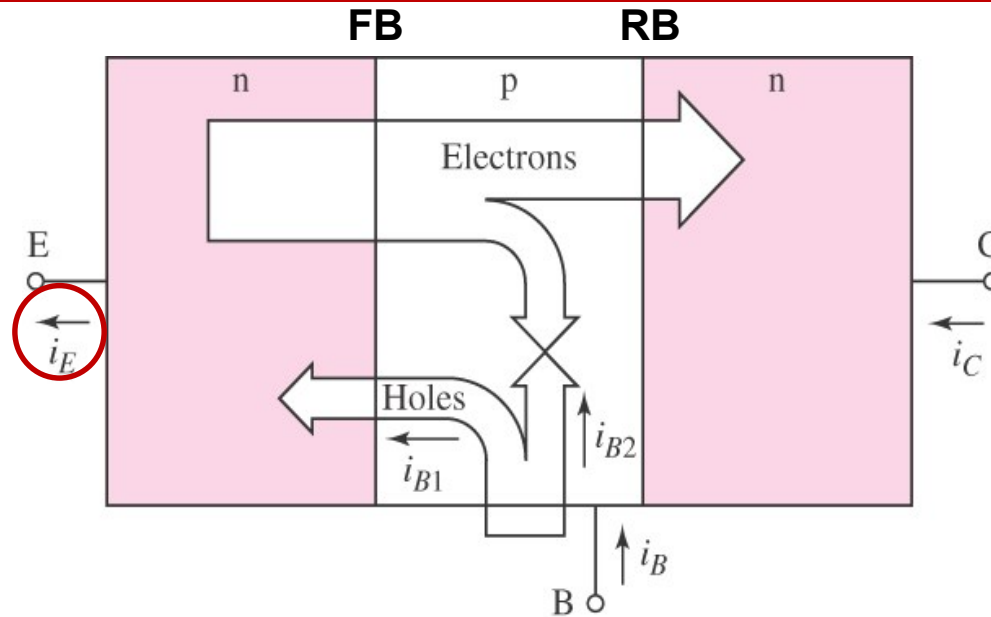The direction of the current follows the flow of positive charges



Emitter current :

Holes injected from B to E + Electrons injected from E to B. The latter is dominant as the emitter is more highly doped than the base

Base current :


Holes injected from B to E + Holes recombining with electrons injected from E to B

Collector current:


Holes drifting from C to B + Electrons injected from E to B, diffusing across the base and swept towards C by the high electric field across the B-C junction. The latter is dominant as the collector is lightly doped.

The Bipolar Junction Transistor (BJT)

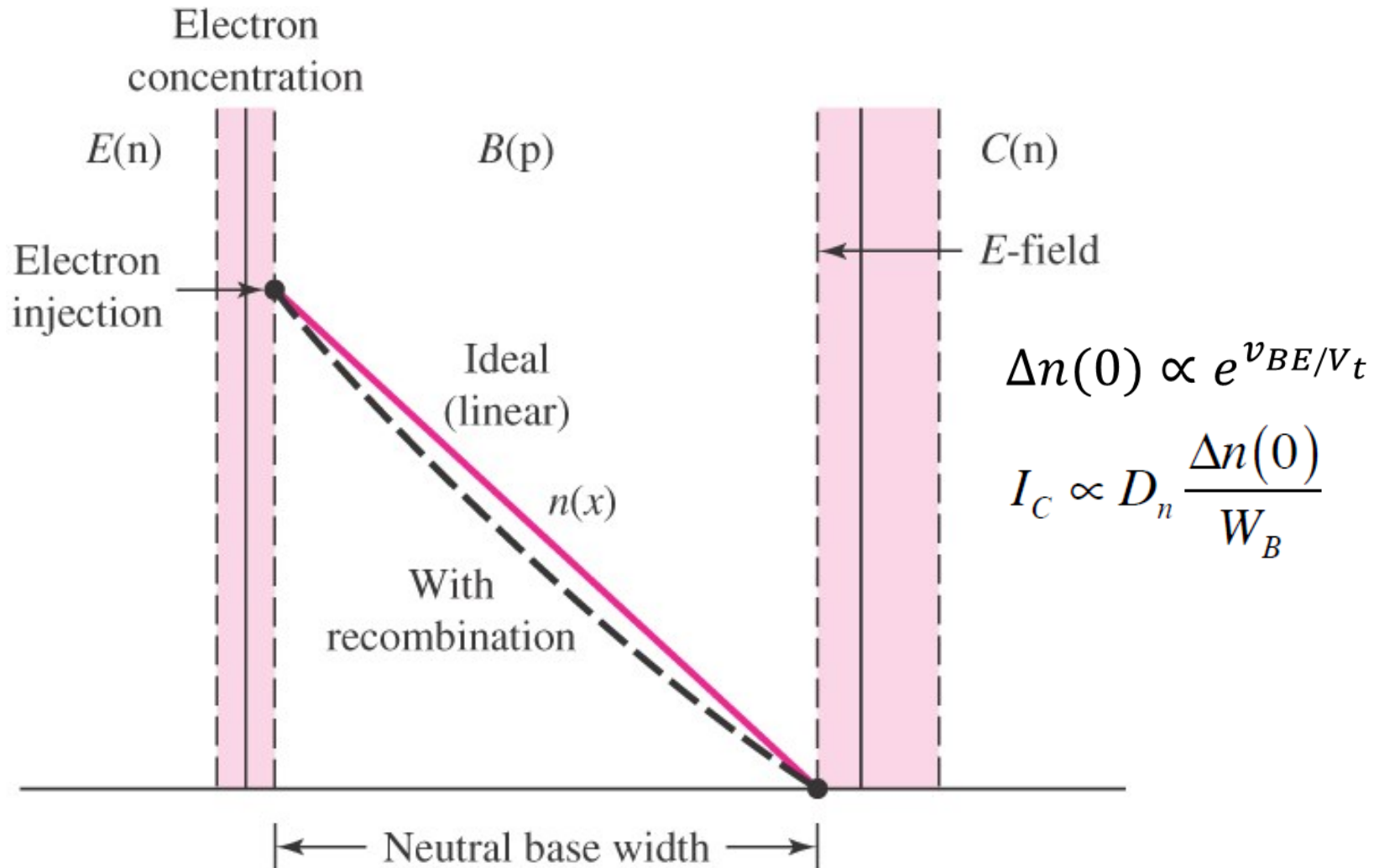Operation in forward active region or mode



BJT in forward active mode: currents

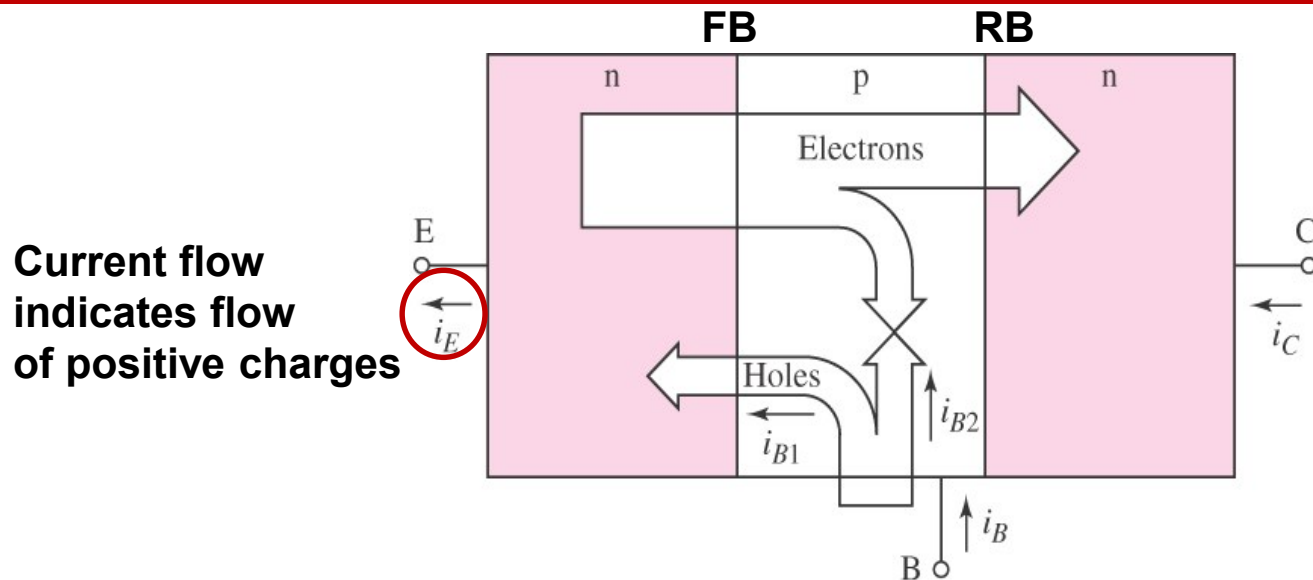

Current flow indicates flow of positive charges

Notes:

- The base current is much smaller than the emitter and the collector current.
- I_{EO} , I_{BO} , and I_S depend on doping levels, device geometry, and temperature.

Emitter current :

$$i_E = I_{EO}[e^{v_{BE}/V_T} - 1] \cong I_{EO}e^{v_{BE}/V_T} \quad v_{BE} \gg V_T$$

Base current :

$$i_B = i_{B1} + i_{B2}; i_{B1} \propto e^{v_{BE}/V_T} \quad i_{B2} \propto e^{v_{BE}/V_T} \quad i_B = I_{BO}e^{v_{BE}/V_T}$$

Collector current:

$$i_C = I_S e^{v_{BE}/V_T}$$

BJT in forward-active mode: currents

As all terminal currents in a BJT have an exponential dependence on V_{BE} , they will be linearly related.

$$\frac{i_C}{i_B} = \beta \quad (\beta = I_s / I_{B0} \text{ varies with transistor parameters and temperature})$$

$$i_E = i_C + i_B$$


$$i_E = (1 + \beta)i_B$$

$$i_C = \left(\frac{\beta}{1 + \beta} \right) i_E \quad i_C = \alpha i_E$$

$$\alpha = \frac{\beta}{1 + \beta}$$

β : Common-emitter current gain- $50 < \beta < 300$

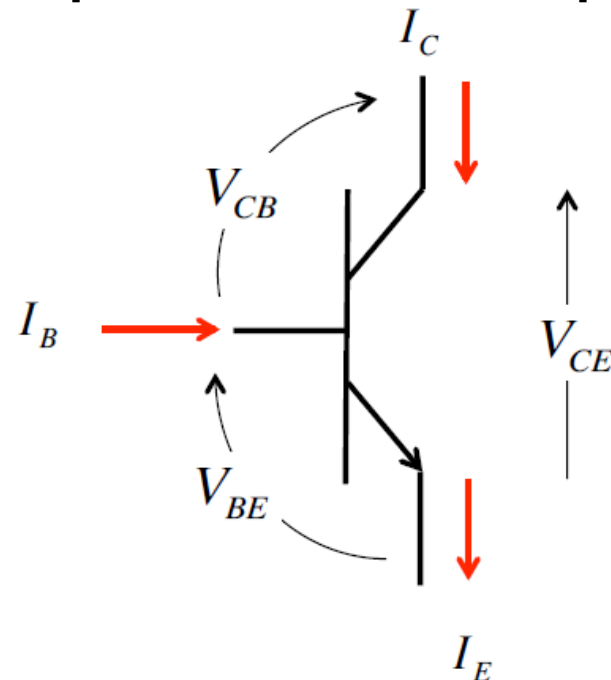α : Common-base current gain- $\alpha \approx 0.99$



BJT in forward-active mode

Current-voltage relationships in the forward-active operating region*

Table 5.1


Summary of the bipolar current-voltage relationships in the active region

npn	pnp
$i_C = I_S e^{v_{BE}/V_T}$	$i_C = I_S e^{v_{EB}/V_T}$
$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{BE}/V_T}$	$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{EB}/V_T}$
$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T}$	$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{EB}/V_T}$
For both transistors	
$i_E = i_C + i_B$	$i_C = \beta i_B$
$i_E = (1 + \beta) i_B$	$i_C = \alpha i_E = \left(\frac{\beta}{1 + \beta} \right) i_E$
$\alpha = \frac{\beta}{1 + \beta}$	$\beta = \frac{\alpha}{1 - \alpha}$


* The Early effect is neglected here

BJT in forward active mode

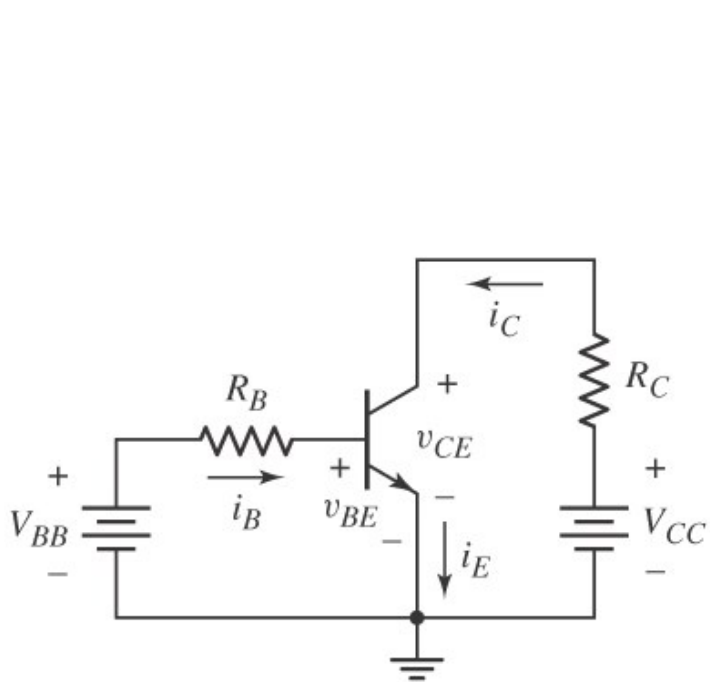Current-voltage relationships in the forward-active operating region





Common emitter configuration

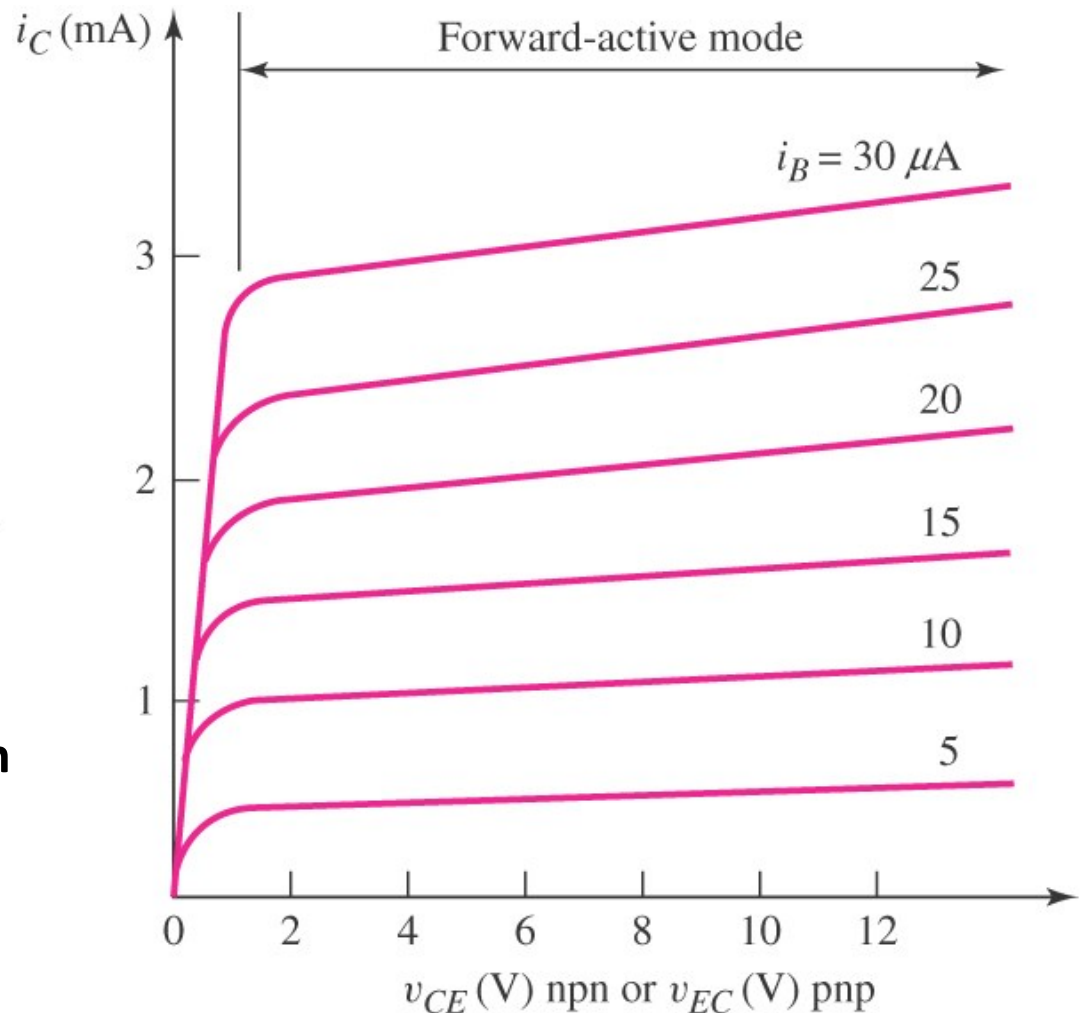

BJT current-voltage characteristics (Active mode):

Early effect

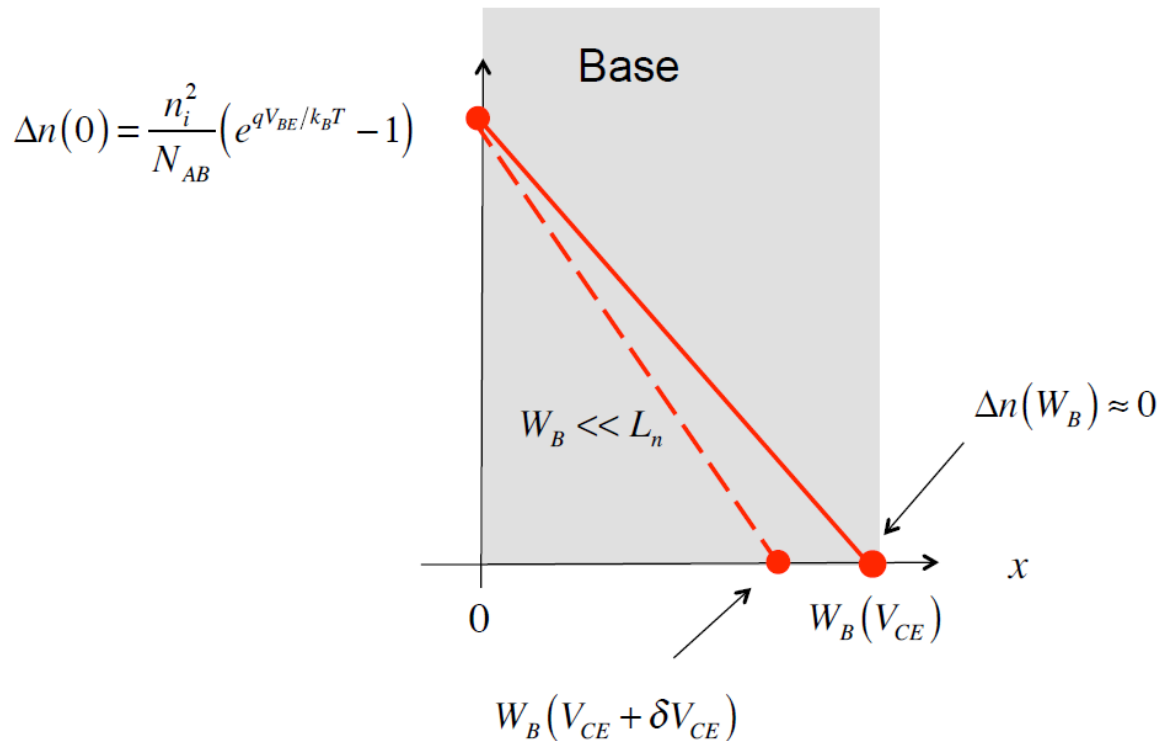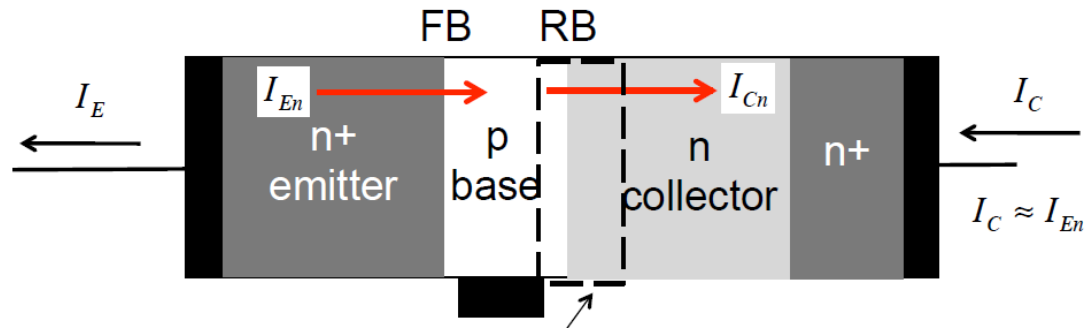

$$I_C \propto D_n \frac{\Delta n(0)}{W_B}$$



BJT in forward active mode: DC model

Common emitter configuration (npn) (w/ Early effect)



$$i_C = I_S(e^{v_{BE}/V_T}) \cdot \left(1 + \frac{v_{CE}}{V_A}\right)$$

$$\frac{1}{r_o} = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{v_{BE}=\text{const.}}$$



$$r_o \cong \frac{V_A}{I_C}$$

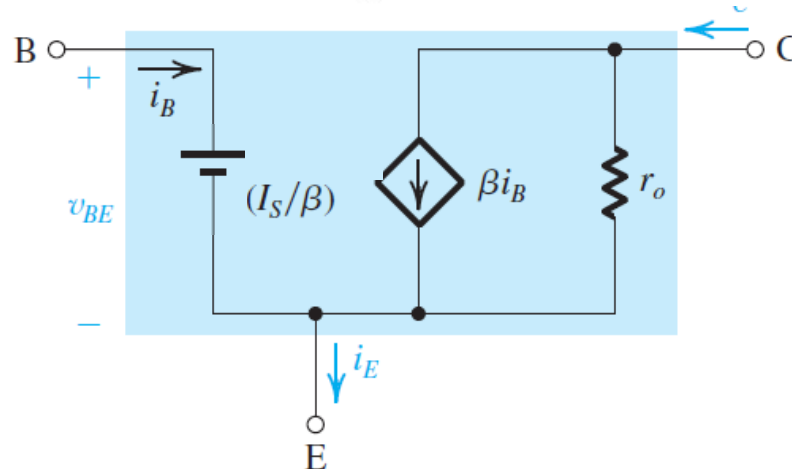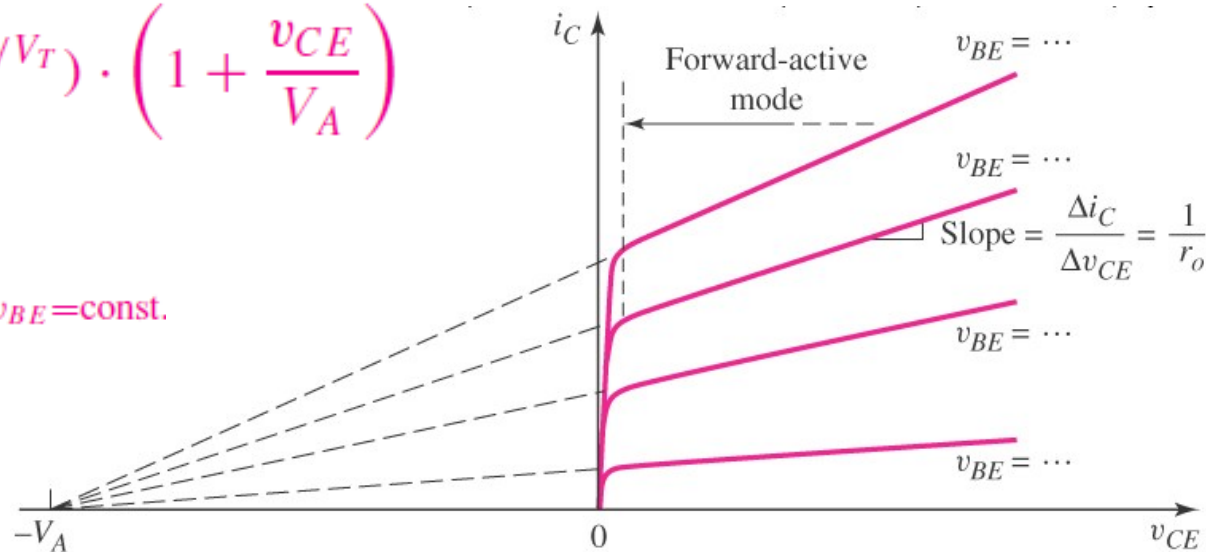

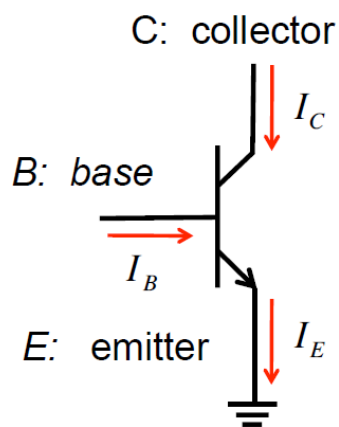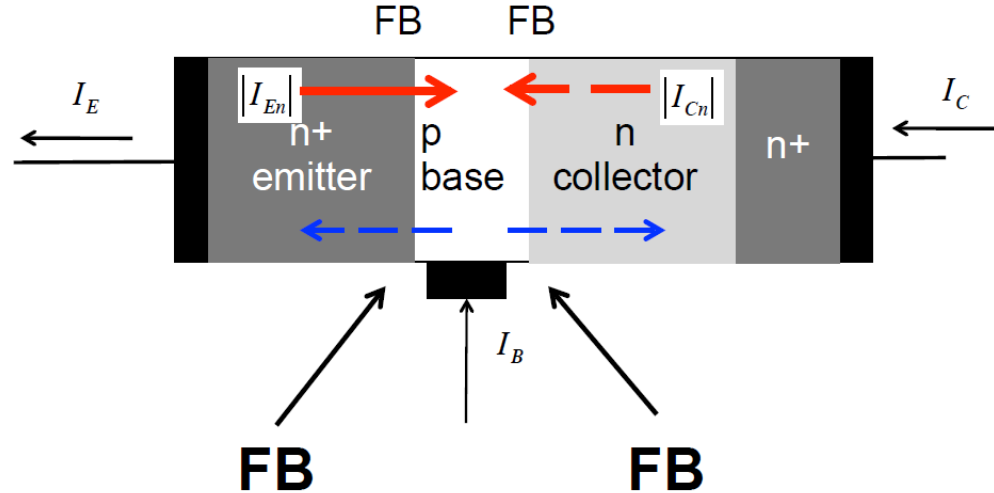
BJT in saturation: characteristics and DC model



NPN BJT

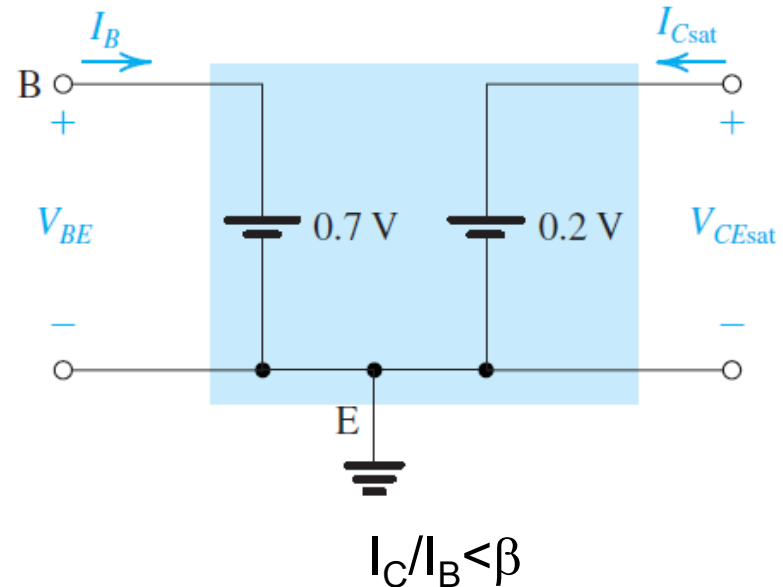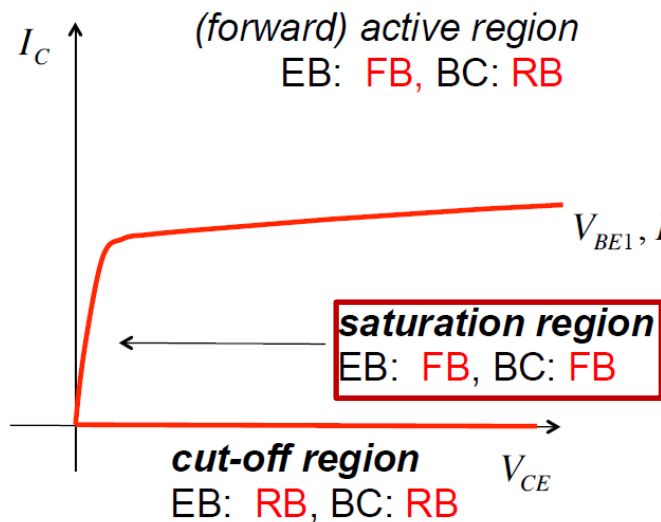


BJT in cut-off: DC model

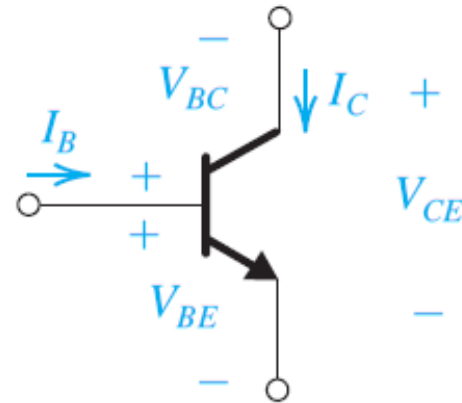

Cutoff

EJB: Reverse Biased



CBJ: Reverse Biased

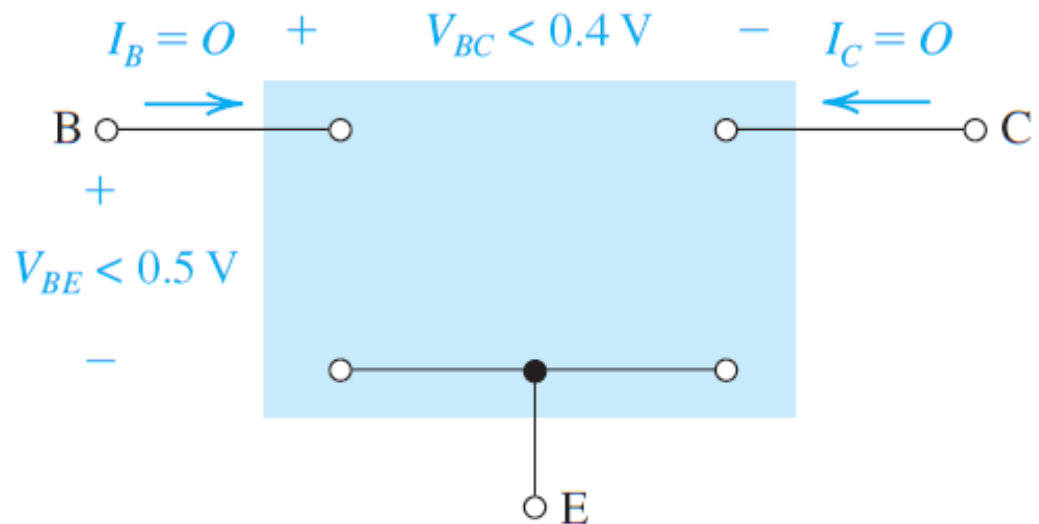

BJT: DC models-Summary



Cutoff

EJB: Reverse Biased
CBJ: Reverse Biased

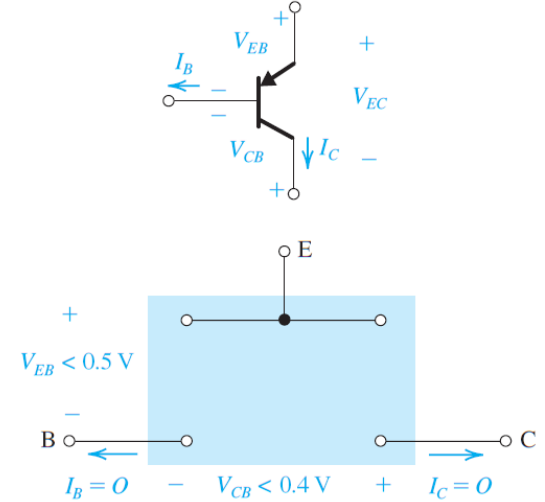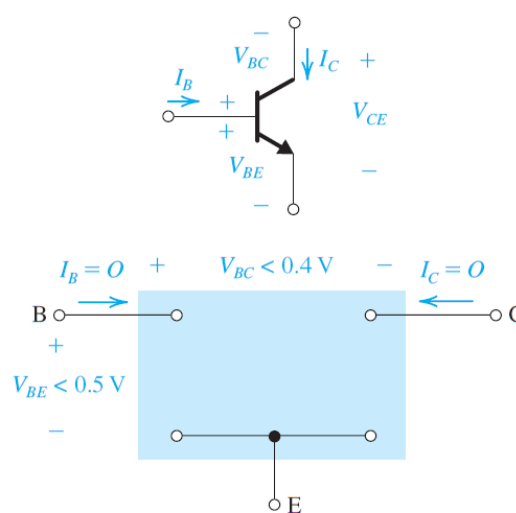



Active

EJB: Forward Biased
CBJ: Reverse Biased

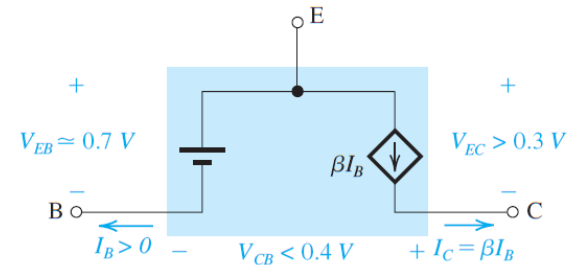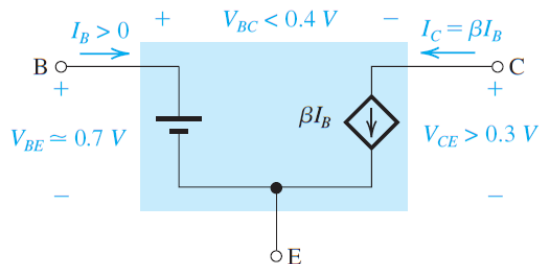

Saturation


EJB: Forward Biased
CBJ: Forward Biased

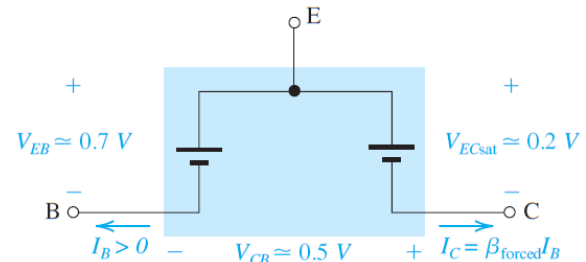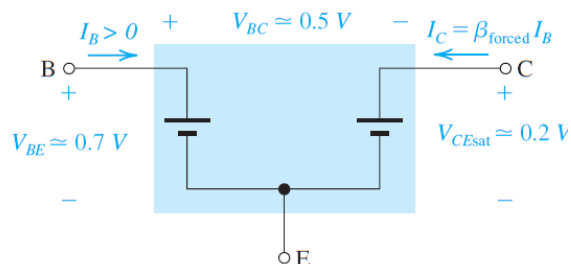

Condition for forward-active mode


B-E junction in forward bias & B-C junction in reverse bias
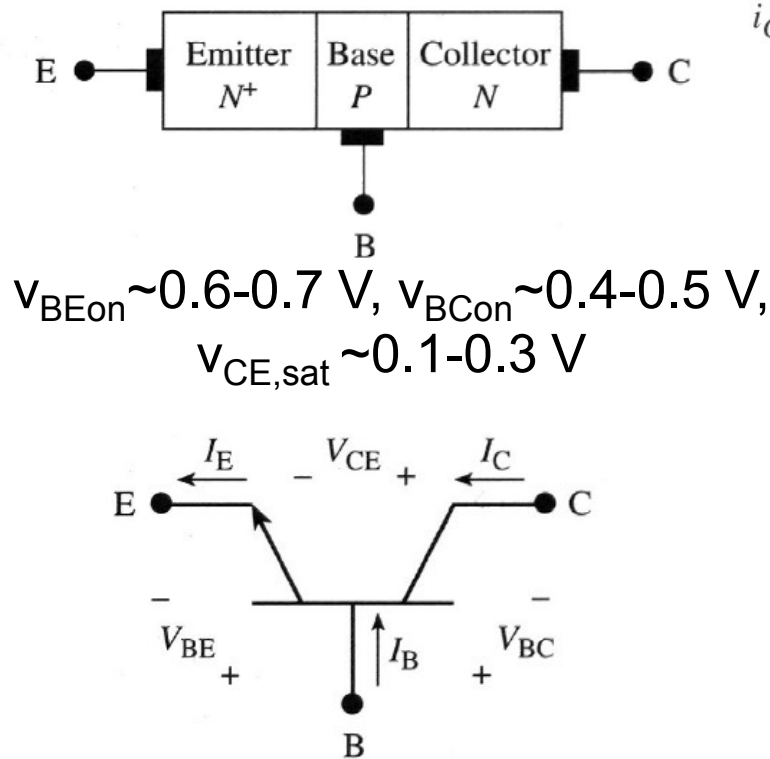
$$V_{BE} > V_{BEon}, V_{BC} < V_{BCon}, V_{CE} > V_{CESAT} = V_{BEon} - V_{BCon}$$




$$I_B > 0, \text{ and } I_C = \beta I_B$$

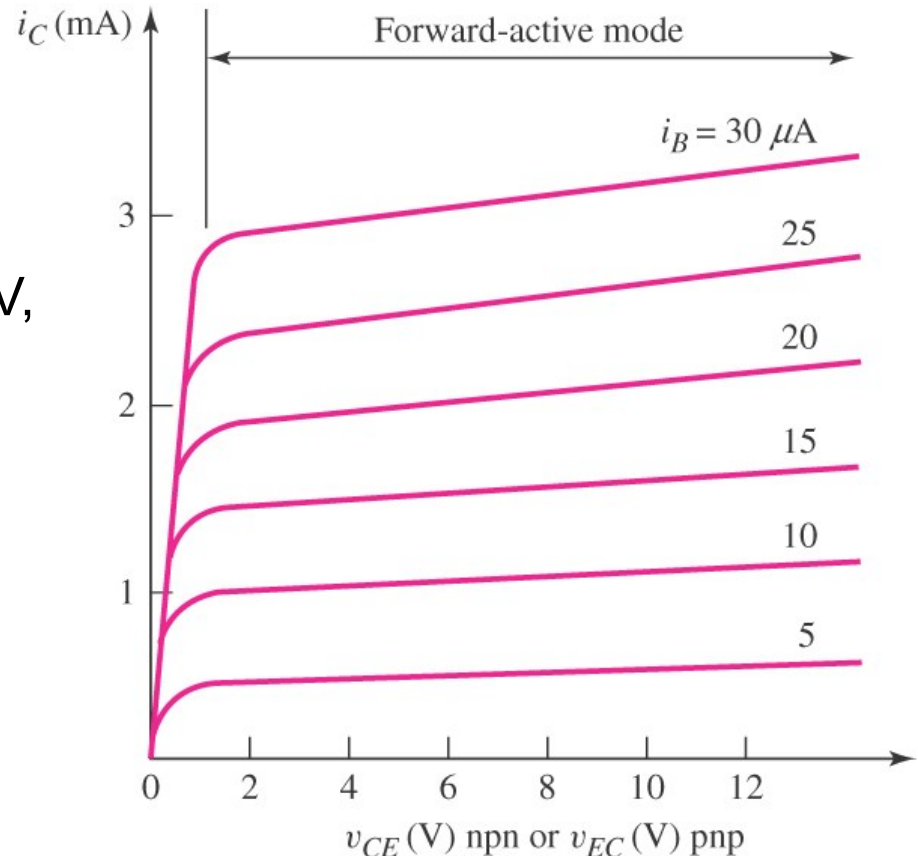Additional conditions for active operation




*Practice writing the conditions for FA operation of a pnp

BJTs configurations

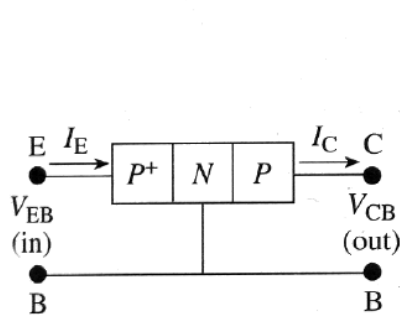


Common base

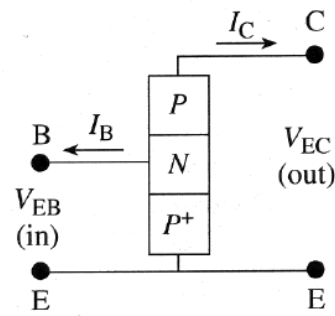Both the input and output share the base “in common”



Common emitter

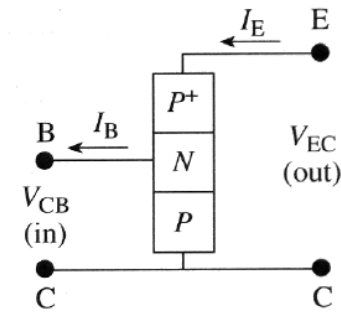Both the input and output share the emitter “in common”





Common collector


Both the input and output share the Collector “in common”

I/O current-voltage characteristics


Common Emitter

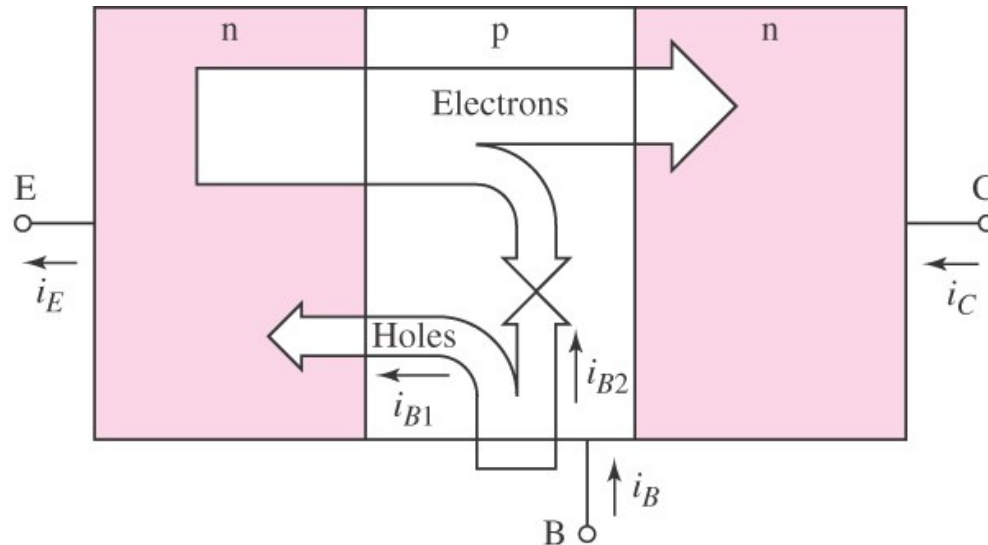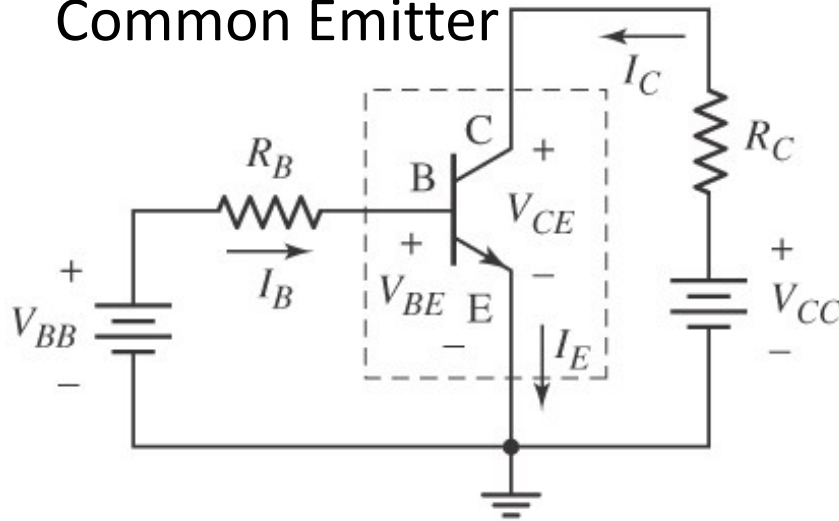

Input characteristics

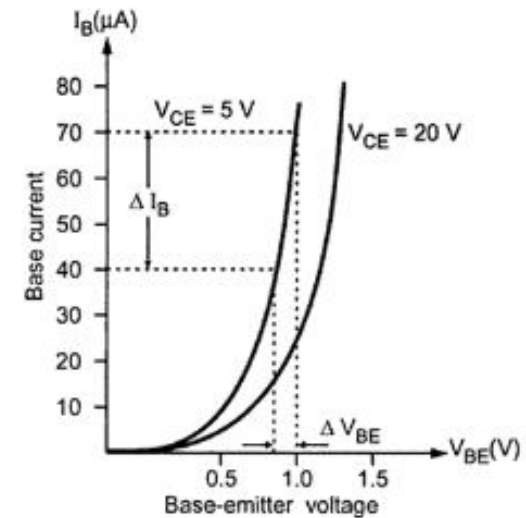


Output characteristics

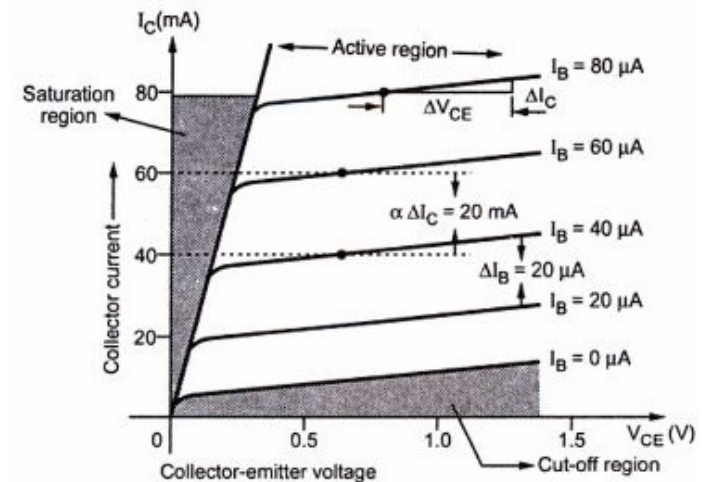


I/O current-voltage characteristics



Common Base

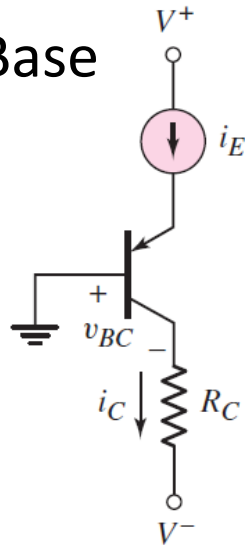

Input characteristics

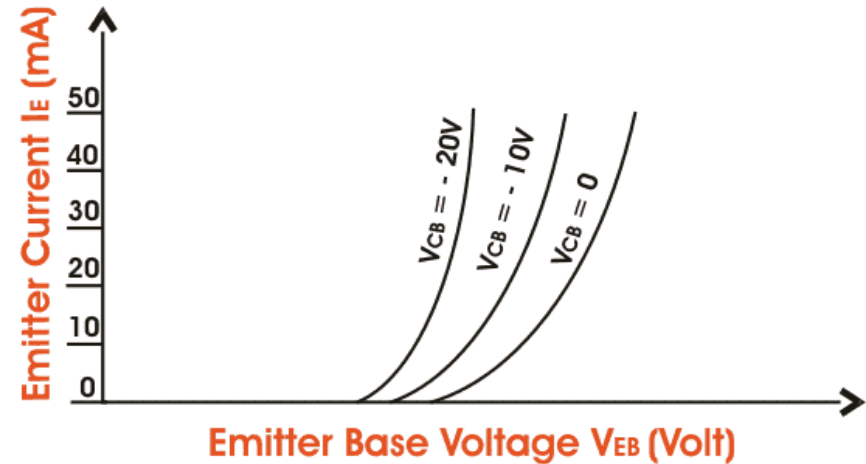

Output characteristics

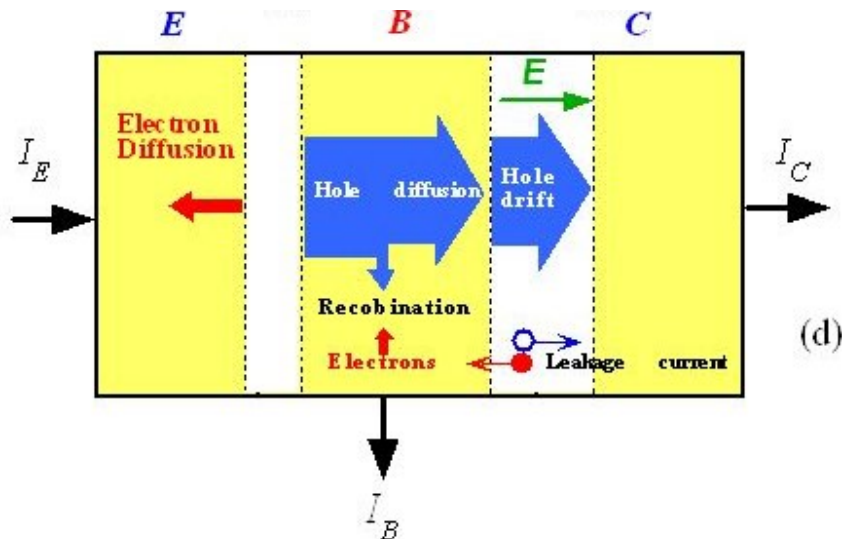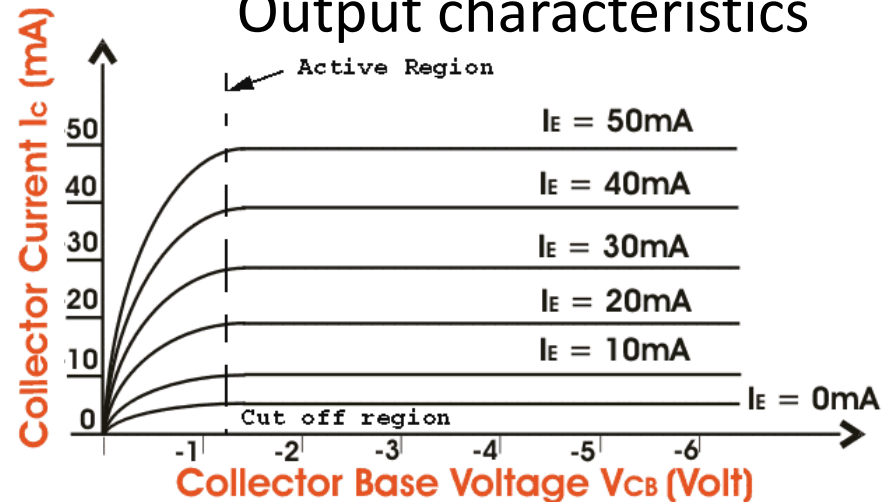

Overview of lecture 11

- Lecture 11-
- The Bipolar Junction Transistor (BJT):
Structure, Operating regions, DC analysis,
Load lines (Neamen-From 5.1.1 to 5.1.5)