

ECE322L -Homework 8 (100 points)
Assigned on Thursday, 03/26/2020-11 am
Due on Thursday, 04/09/2020-11 am

Calculate the output resistance of the amplifier below. Note that V_A is infinite for Q_1 and Q_2 . What application would be most advantageous to use the amplifier below for? Justify your answer.

