

ECE 322L

Electronics 2

01/30/20 - Lecture 4


Biasing configurations 2

Updates and overview

- Homework 1 is online (Both soft and hard copies will be accepted). The TA will create a link for you to upload the homework.
- Lab 2 will be online tomorrow
- More examples of biasing circuits (Neamen 3.2,3.4, S&S 5.3, 5.4, 5.7)

Biasing circuits

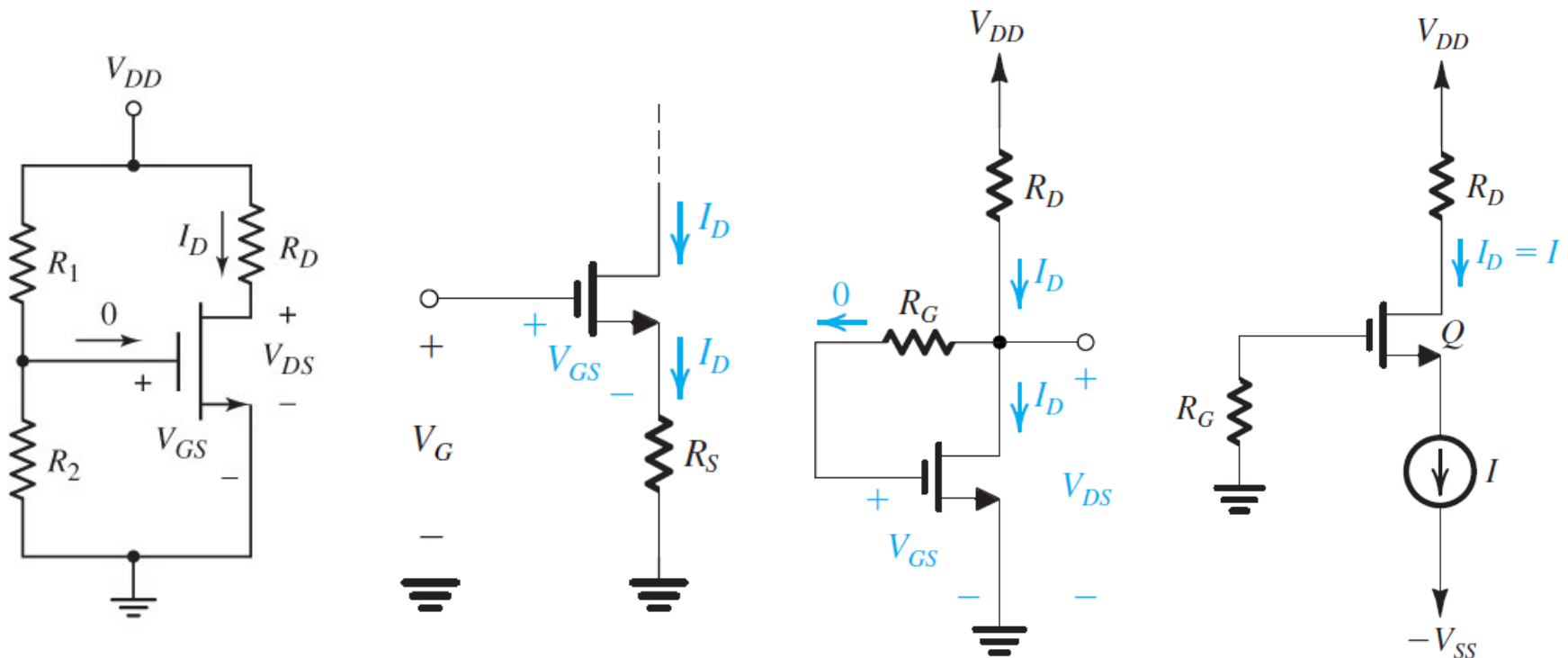
A well-designed biasing circuit for an amplifier should force a **stable and predictable V_{GS} , I_D , and V_{DS}** that ensure operation in the **saturation** region for all expected input signal levels.



Four possible biasing circuits or configurations

Biasing by a drain-to-gate feedback resistor

Condition: very large R_G (M Ω)

 

$$V_{GS} = V_{DS} = V_{DD} - R_D I_D \Rightarrow I_D = \frac{V_{DD} - V_{GS}}{R_D}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$


$$\frac{V_{DD} - V_{GS}}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$V_{GS} = V_{DS} = f(V_{DD}, R_D)$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

Biasing by a drain-to-gate feedback resistor

 R_D implements a feedback loop which keeps I_D relatively stable




A high R_D is preferable to ensure stability

Trade off: High R_D will reduce V_{DS} and move the Q point towards triode

In class problem 1

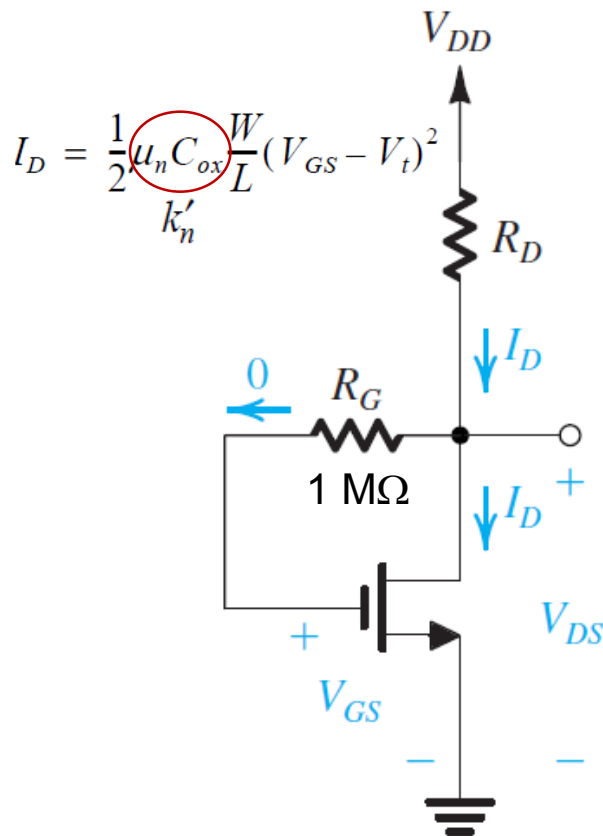D5.35 Design the circuit in Fig. 5.54 to operate at a dc drain current of 0.5 mA. Assume $V_{DD} = +5$ V, $k'_n W/L = 1 \text{ mA/V}^2$, $V_t = 1$ V, and $\lambda = 0$. Use a standard 5% resistance value for R_D , and give the actual values obtained for I_D and V_D .



| Standard Resistor Values ($\pm 5\%$) | | | | | | |
|--|----|-----|------|-----|------|------|
| 1.0 | 10 | 100 | 1.0K | 10K | 100K | 1.0M |
| 1.1 | 11 | 110 | 1.1K | 11K | 110K | 1.1M |
| 1.2 | 12 | 120 | 1.2K | 12K | 120K | 1.2M |
| 1.3 | 13 | 130 | 1.3K | 13K | 130K | 1.3M |
| 1.5 | 15 | 150 | 1.5K | 15K | 150K | 1.5M |
| 1.6 | 16 | 160 | 1.6K | 16K | 160K | 1.6M |
| 1.8 | 18 | 180 | 1.8K | 18K | 180K | 1.8M |
| 2.0 | 20 | 200 | 2.0K | 20K | 200K | 2.0M |
| 2.2 | 22 | 220 | 2.2K | 22K | 220K | 2.2M |
| 2.4 | 24 | 240 | 2.4K | 24K | 240K | 2.4M |
| 2.7 | 27 | 270 | 2.7K | 27K | 270K | 2.7M |
| 3.0 | 30 | 300 | 3.0K | 30K | 300K | 3.0M |
| 3.3 | 33 | 330 | 3.3K | 33K | 330K | 3.3M |
| 3.6 | 36 | 360 | 3.6K | 36K | 360K | 3.6M |
| 3.9 | 39 | 390 | 3.9K | 39K | 390K | 3.9M |
| 4.3 | 43 | 430 | 4.3K | 43K | 430K | 4.3M |
| 4.7 | 47 | 470 | 4.7K | 47K | 470K | 4.7M |
| 5.1 | 51 | 510 | 5.1K | 51K | 510K | 5.1M |
| 5.6 | 56 | 560 | 5.6K | 56K | 560K | 5.6M |
| 6.2 | 62 | 620 | 6.2K | 62K | 620K | 6.2M |
| 6.8 | 68 | 680 | 6.8K | 68K | 680K | 6.8M |
| 7.5 | 75 | 750 | 7.5K | 75K | 750K | 7.5M |
| 8.2 | 82 | 820 | 8.2K | 82K | 820K | 8.2M |
| 9.1 | 91 | 910 | 9.1K | 91K | 910K | 9.1M |

Figure 5.54 Biasing the MOSFET using a large drain-to-gate feedback resistance, R_G .

Biasing by a Current Source

1) Current source forces:

$$I_D = I$$


2) $V_D = V_{DD} - R_D I_D$

3) V_{GS} is set by


$$I_D = 0.5 \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

4) $V_S = V_G - V_{GS} = -V_{GS}$


5) $V_{DS} = V_D - V_S$

 

Biasing by a Current Source (IC)

 

(a)

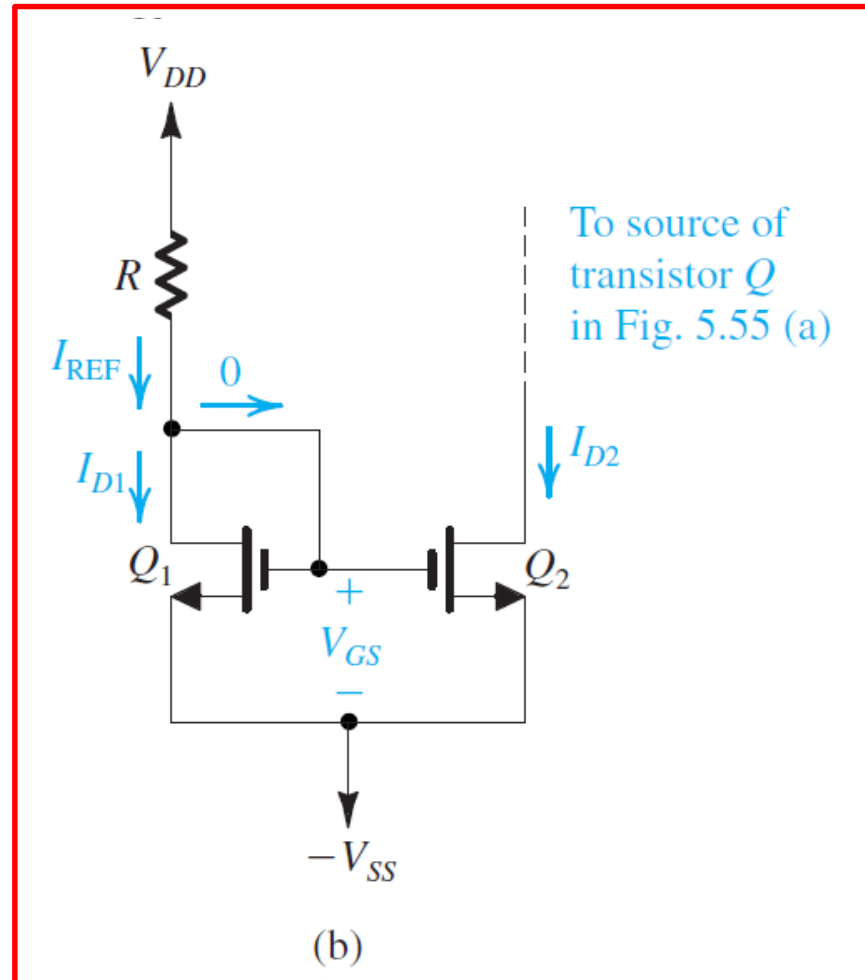


(b)

Current mirror

Current Mirror

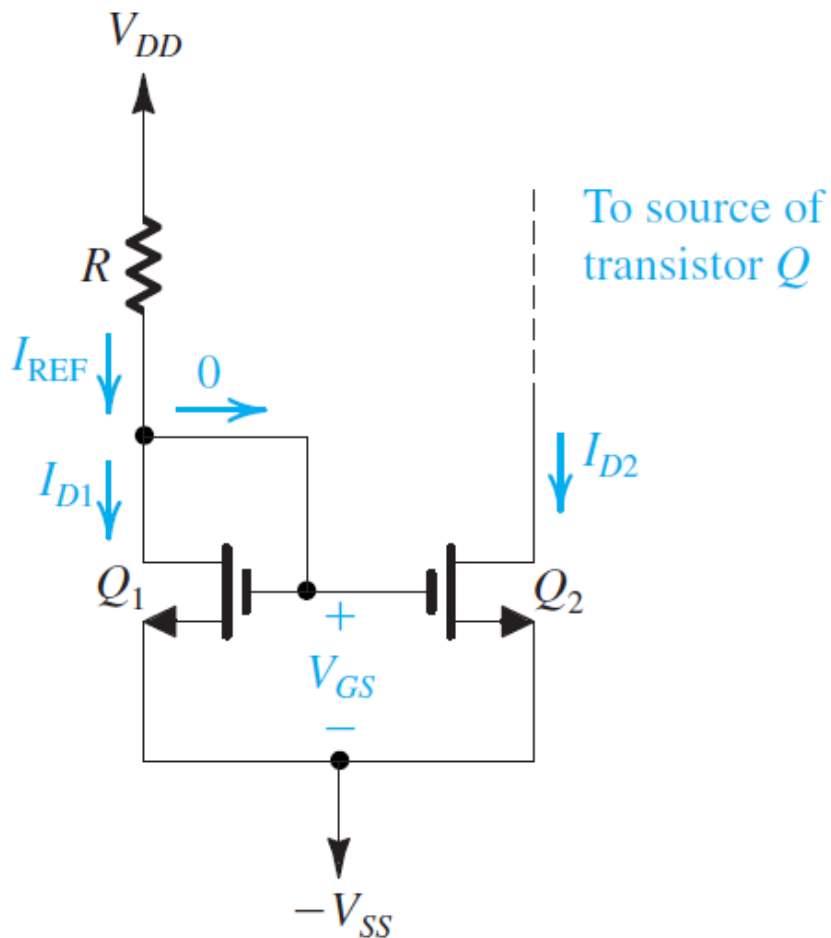Assumptions: k_n' and V_t are the same for Q_1 and Q_2



$$I = I_{D2} = \frac{1}{2}k_n' \left(\frac{W}{L}\right)_2 (V_{GS} - V_t)^2$$

$$I_{D1} = \frac{1}{2}k_n' \left(\frac{W}{L}\right)_1 (V_{GS} - V_t)^2$$

$$I_{D1} = I_{REF} = \frac{V_{DD} + V_{SS} - V_{GS}}{R}$$


$$I = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$

Q2 needs to be in saturation for mirroring to occur

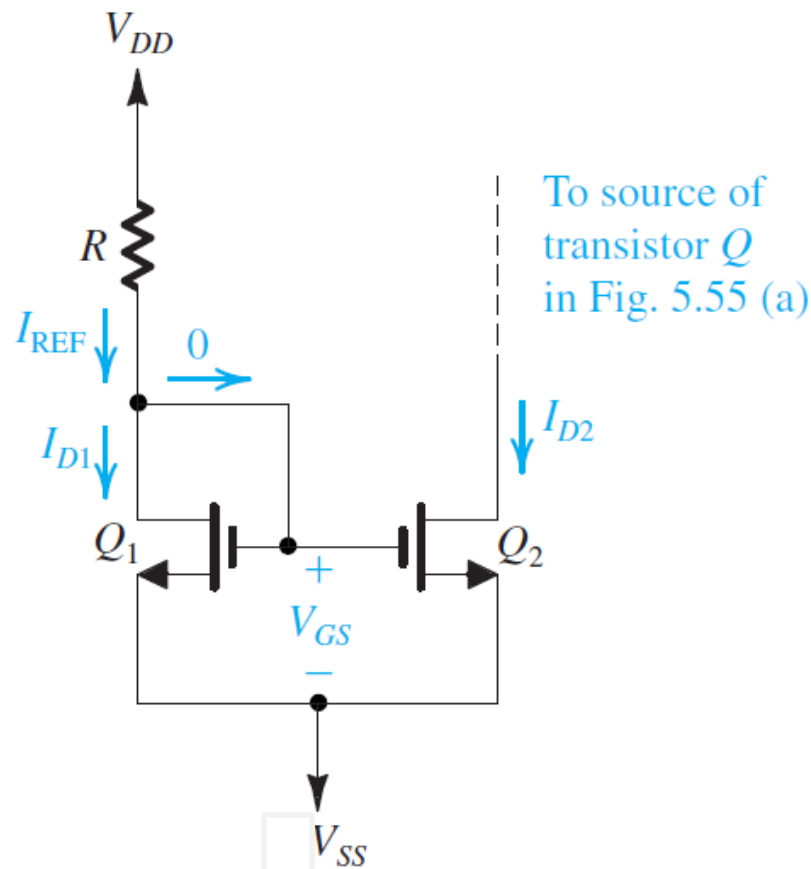Q1 is in saturation because $V_{DS} = V_{GS}$

In class problem 2

D5.36 Using two transistors Q_1 and Q_2 having equal lengths but widths related by $W_2/W_1 = 5$, design the circuit of Fig. 5.55(b) to obtain $I = 0.5$ mA. Let $V_{DD} = -V_{SS} = 5$ V, $k'_n(W/L)_1 = 0.8$ mA/V², $V_t = 1$ V, and $\lambda = 0$. Find the required value for R . What is the voltage at the gates of Q_1 and Q_2 ? What is the lowest voltage allowed at the drain of Q_2 while Q_2 remains in the saturation region?



$$I_D = \frac{1}{2} \frac{\mu_n C_{ox} W}{k'_n L} (V_{GS} - V_t)^2$$

$$I = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$

Overview of lecture 5

- More on current mirrors
- (Neamen 3.2,3.4, S&S 5.3, 5.4, 5.7)
- FETs as amplifiers; total components and small signal analysis
(Neamen 4.1.1, 4.1.2- S&S from 5.5.1 to 5.5.6)