


$V_{AB} \Rightarrow DC$

$$\sqrt{AB} \Rightarrow DC + AC$$

$$N_{ab} \rightarrow AC$$

Assuming small-signals
is what we are dealing with

$$\sqrt{AB} = \sqrt{AB} + \sqrt{ab}$$

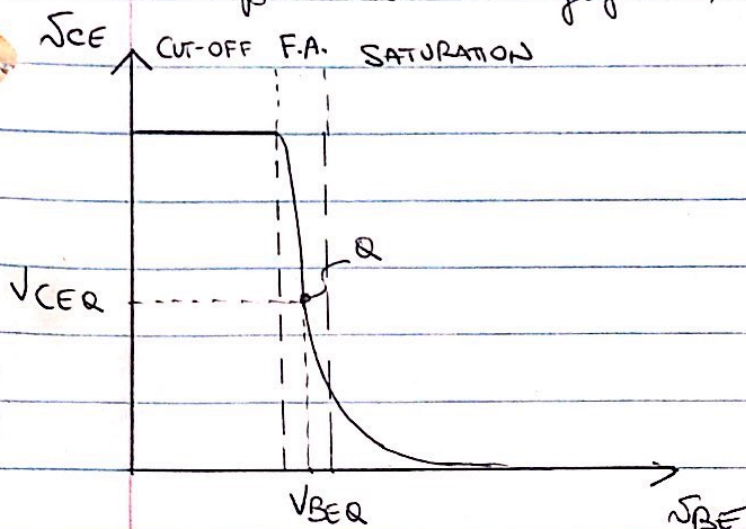

$$\frac{A_5 = d_{SCE}}{d_{SBE}} \quad (1)$$

1) Doing a KVL @ the loop M and considering the DC+AC signals, we obtain

$$-V_{EE} + R_E i_E + \beta R_{CE} + R_{CE} i_C - V_{CC} = 0 \quad (2)$$

$$V_{CE} = V_{CC} + V_{EE} - (R_E + R_C) i_C \quad (i_E \approx i_C)$$

(2)

$$i_c = I_S e^{v_{BE}/V_T} \quad (4)$$

$$v_{BE} = V_{BEQ} + v_{be} \quad (5)$$

$$v_{CE} = V_{CC} + V_{EE} - (R_C + R_E) \cdot I_S e^{v_{BEQ}/V_T} e^{v_{be}/V_T} \quad (6)$$

$$A_S = \left. \frac{dv_{CE}}{dv_{BE}} \right|_{v_{BE}=V_{BEQ}} = - \frac{R_C + R_E}{V_T} I_S e^{v_{BEQ}/V_T} e^{v_{be}/V_T} \quad (7)$$

$v_{BE} = V_{BEQ}$

$$A_S = - \frac{R_C + R_E}{V_T} I_S e^{(V_{BEQ} + v_{be})/V_T} \bigg|_{v_{BE}=V_{BEQ}} = - \frac{R_C + R_E}{V_T} \cdot I_S e^{v_{be}/V_T} \quad (8)$$

$v_{BE} = V_{BEQ}$

$$A_S = - \frac{R_C + R_E}{V_T} \underbrace{I_S e^{V_{BEQ}/V_T}}_{I_{CQ}} = - \frac{R_C + R_E}{V_T} \cdot I_{CQ} \quad (9)$$

$$|A_S| = \frac{R_C + R_E}{V_T} \cdot I_{CQ} \quad (10)$$

As V_T and I_{CQ} are fixed, in order to maximize the gain, we need to maximize $(R_C + R_E)$.

At this point let's consider the requirement about the swing: $-2 \leq v_O \leq 2$ (11) (* $v_O = v_O + v_{be}$)

The (11) translates into the condition below:

The BJT is to remain in forward active mode for $v_O \pm 2$.

The BJT will remain in forward active mode as long as $v_{CE} > v_{CE,sat}$ and $v_{CE} < v_{CE,cut-off}$.

$$0.3 \leq v_{CE} \leq 15 \quad (12) \quad (* v_{CE,sat} = 0.3V; v_{CE,cut-off} = V_{CC} + V_{EE})$$

Now if we consider that $v_{CE} = v_C - v_E = v_O - v_E$

$$0.3 \leq v_O - v_E \leq 15 \quad (15)$$

Remember that

③

$$v_o = v_o + v_o \quad \text{and} \quad v_e = v_e + v_e$$

(DC) (ac) (DC) (ac)

Thus, we can write

$$0.3 \leq v_o + v_o - (v_e + v_e) \leq 15$$

We can then utilize the condition on the maximum swing for the output voltage

$$v_o - 2 - (v_e + v_e) \geq 0.3 \text{ V}$$

$$v_o + 2 - (v_e + v_e) \leq 15 \text{ V}$$

$$v_o = v_c = V_{CC} - R_C I_C$$

$$v_e = -V_{EE} + R_E I_E$$

$$V_{CC} - R_C I_C - 2 + V_{EE} - R_E I_E - v_e \geq 0.3 \text{ V}$$

$$V_{CC} - R_C I_C + 2 + V_{EE} - R_E I_E - v_e \leq 15 \text{ V}$$

$$10 - (R_C + R_E) I_C + 5 - 2 - v_e \geq 0.3 \text{ V}$$

$$10 - (R_C + R_E) I_C + 5 + 2 - v_e \leq 15 \text{ V}$$

$$13 - (R_C + R_E) I_C - v_e \geq 0.3 \text{ V}$$

$$17 - (R_C + R_E) I_C - v_e \leq 15 \text{ V}$$

(4)

$$-(R_C + R_E) I_C \geq 0.3V - 13V + \cancel{5e}$$

$$-(R_C + R_E) I_C \leq 15 - 17 + \cancel{5e}$$

$$(R_C + R_E) I_C \leq -0.3 + 13 - \cancel{5e}$$

$$(R_C + R_E) I_C \geq -15 + 17 - \cancel{5e}$$

$$(R_C + R_E) \leq \frac{12.7 - \cancel{5e}}{I_C}$$

$$(R_C + R_E) \geq \frac{2 - \cancel{5e}}{I_C}$$

The value of $\cancel{5e}$ can be neglected w.r.t. 12.7, given that $\cancel{5e}_{pp} = 0.04V$.
Thus $R_C + R_E$ is limited by the condition below

$$(R_C + R_E) \leq \frac{12.7}{I_C} \quad I_C = 1mA$$

$$R_C + R_E \leq 12.7 \text{ K}\Omega$$

As we wish to maximize the gain, we will select

$$R_C + R_E = 12.7 \text{ K}\Omega.$$

We can now determine R_E from a KVL @ the input loop and applying the condition of bias-stable design.

$$I_E = \frac{V_{EE} - V_{BE(ON)}}{R_E + \frac{R_B}{\beta+1}} \approx \frac{V_{EE}}{R_E} = \frac{5}{R_E}$$

$$I_E \approx I_C = 1mA$$

Thus

(5)

$$R_E = 5k\Omega$$

$$R_C = 12.7k\Omega - 5k\Omega = 7.7k\Omega$$

When it comes to the resistor on the base, we can select it based on the need for forward active operation of the transistor.

$$V_{BE} = V_{BE(on)} = 0.7V$$

$$V_B - V_E = 0.7V$$

$$V_B = R_B I_B = R_B \frac{I_C}{\beta}$$

$$R_B \frac{I_C}{\beta} - (-V_{EE} + R_E I_E) = 0.7V$$

$$R_B \frac{I_C}{\beta} + 5 - 5k \cdot I_C = 0.7V$$

$$R_B \frac{I_C}{\beta} = 0.7V$$

$$R_B = \frac{0.7 \cdot 200}{1m} = 140k\Omega \rightarrow$$

This value of R_B is small enough to satisfy the condition of a bias-stable design or $R_B \ll (\beta+1)R_E$

$$(\beta+1)R_E = 201 \cdot 5k \approx 1M\Omega$$

⑥
Finally let's calculate the V_{CE} to verify that the BJT is in forward-active region

$$V_{CE} = V_C - V_E$$

$$V_E = 0$$

$$V_C = V_{CC} - R_C I_C = 10 - 7.7 \text{ k}\Omega \cdot 1 \text{ mA} = 2.3 \text{ V}$$

$$V_{CE} > V_{CE, \text{SAT}}$$

The Q point is close to the saturation region, within the forward active mode operating region as the center of the active region corresponds to a $V_{CE} \approx \frac{V_{CC} + V_{EE}}{2} = 7.5 \text{ V}$