

# ECE 322L

## Electronics 2

02/04/20 - Lecture 5

Total components and small signal  
analysis


---

# Updates and Overview

- Lab reports may be submitted via e-mail to the TA after each lab. The TA will provide informal feedback on the lab reports upon request.
- Office hours 9-11 am on Wed (CHTM 110B). Please, double check UNM learn before heading to CHTM on Wed as last-minute changes of the office hours may occur.
- Lecture 5: IC current mirrors, FETs as amplifiers; total components and small signal analysis (Neamen 4.1.1, 4.1.2- S&S from 5.5.1 to 5.5.6).


# Biasing by a Current Source (IC)

Also implemented  
using a transistor

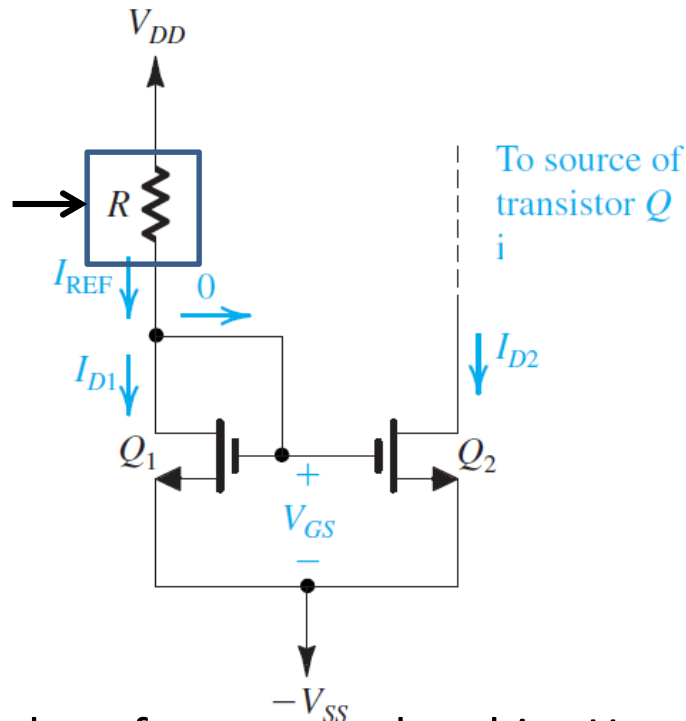

- Resistors which take a lot of space on the chip. Hence they need to be replaced with a different component.
- On a multistage amplifier IC chip, a constant dc current source is generated at one location and is then reproduced at different locations for biasing the various amplification stages. As a result the biasing of the multiple stages track each other in case of parameter changes, such as voltage supply or temperature fluctuations.

# Biasing in IC

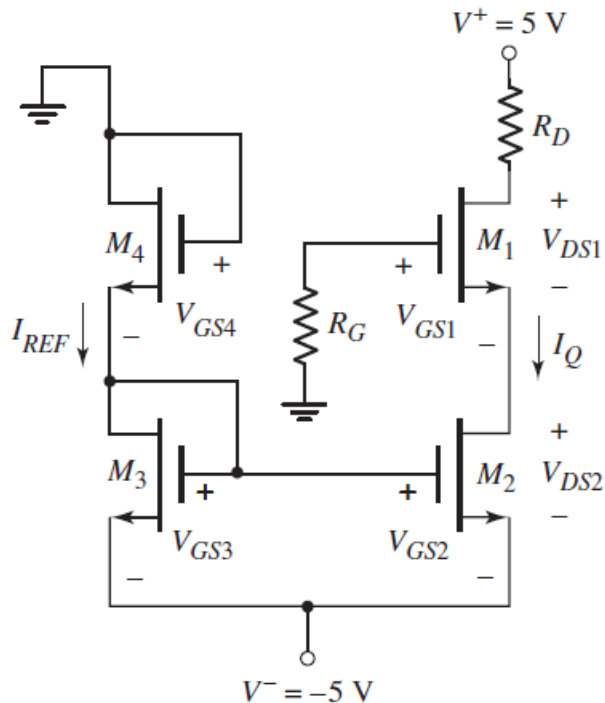




$$V_{GS3} = \frac{\sqrt{\frac{K_{n4}}{K_{n3}}} [(-V^-) - V_{TN4}] + V_{TN3}}{1 + \sqrt{\frac{K_{n4}}{K_{n3}}}}$$

$$I_Q = K_{n2}(V_{GS3} - V_{TN2})^2$$


Figure 3.50 Implementation of a MOSFET constant-current source

Design parameters are the threshold voltages of  $M_3$  and  $M_4$  and the ratio  $K_{n4}/K_{n3}$ .

# Amplifiers

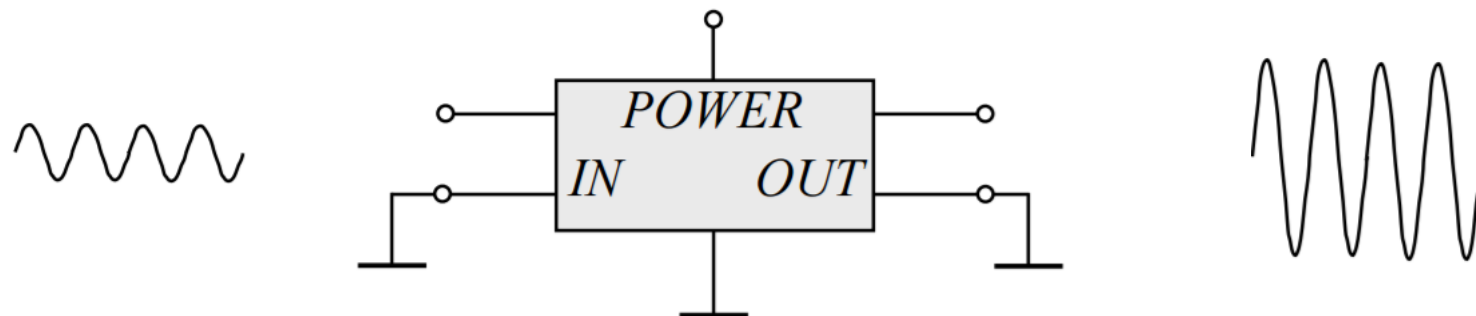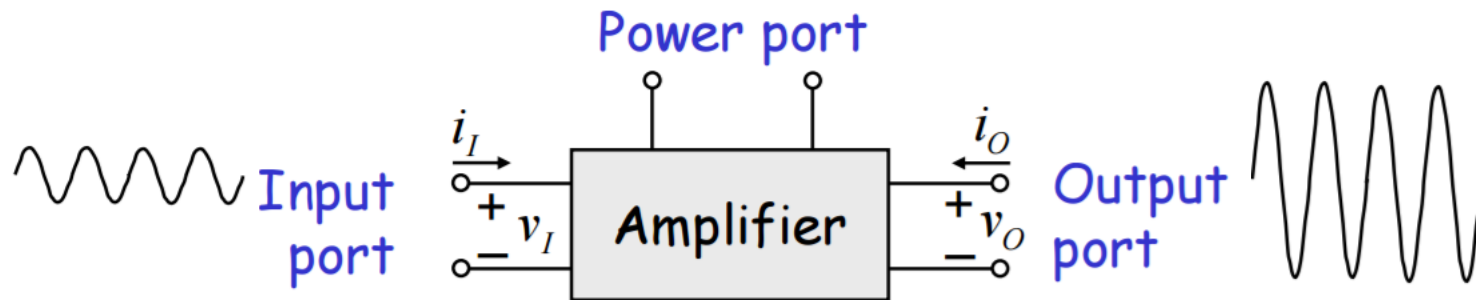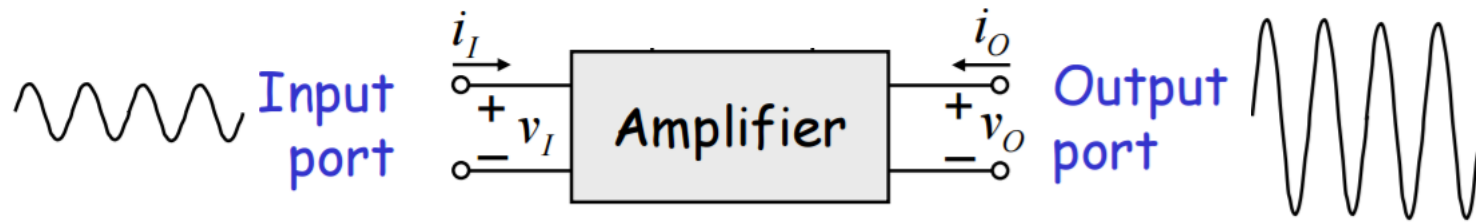

# FET-based Amplifiers

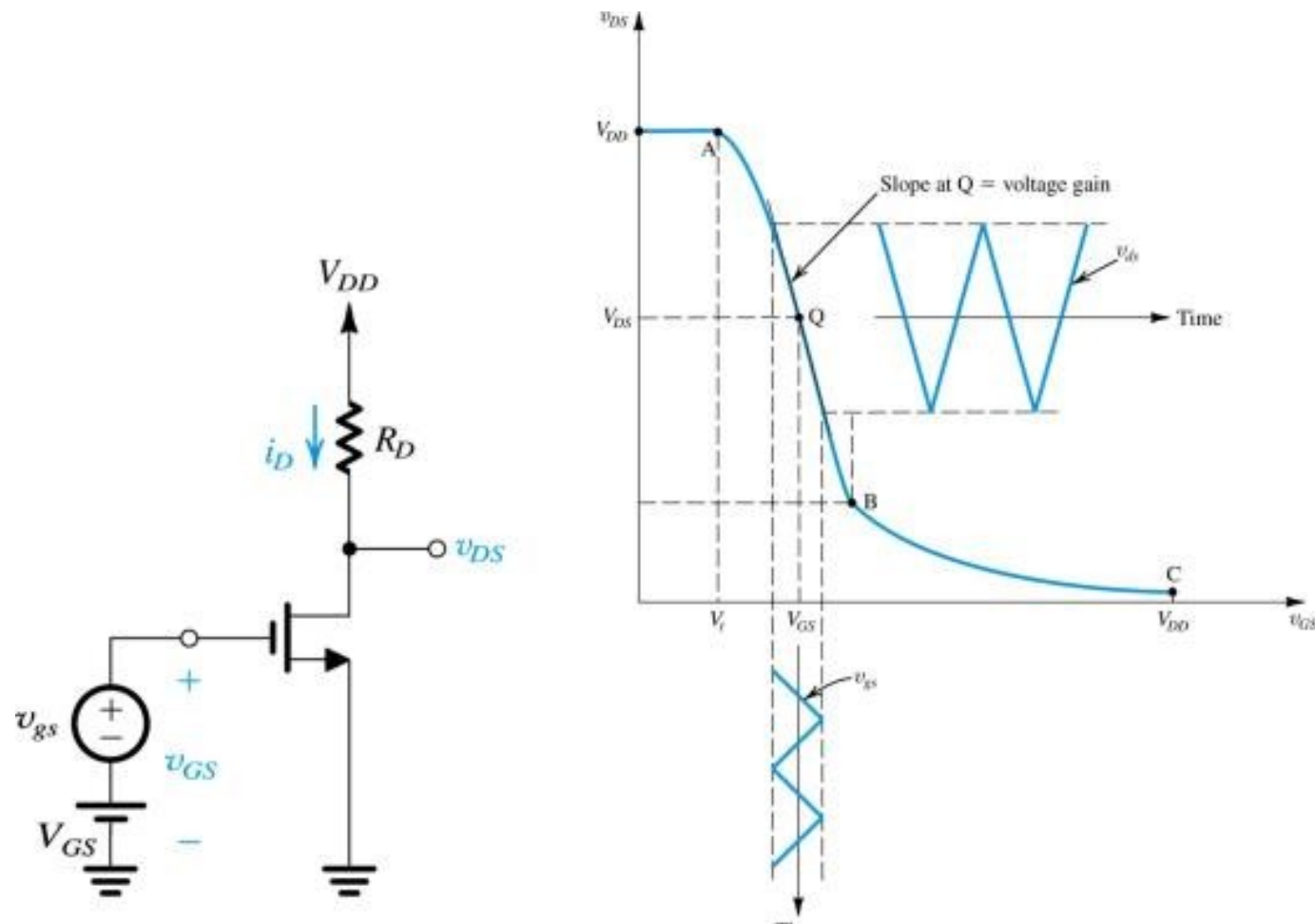

Notation:


$V_A$ : DC signal

$v_a$ : AC signal


$v_A$ : DC+AC signal

1. Determine the Q point of the transistor (DC analysis)
2. Determine the response of the circuit to an input signal (DC&AC analysis)

# FET-based Amplifiers-Analysis

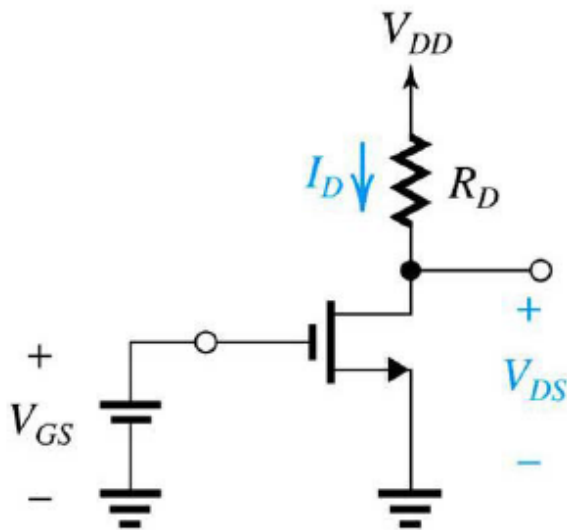


DC circuit

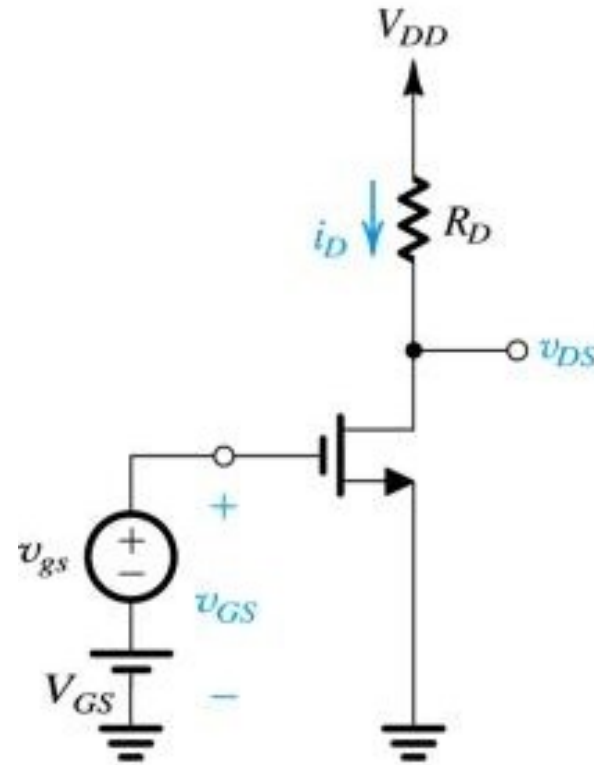

Total components circuit

1. Determine the Q point of the transistor (DC analysis)
2. Determine the response of the circuit to an input signal (DC&AC analysis)

# DC Analysis

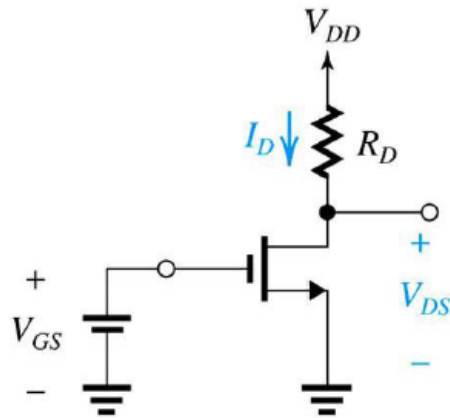


Bias

$$\begin{cases} I_D = \frac{1}{2} \frac{\epsilon_0 \times \mu_n}{t_{ox}} \frac{W}{L} (V_{GS} - V_T)^2 \\ V_{DS} = V_{DD} - R_D I_D \end{cases}$$



To ensure saturation:

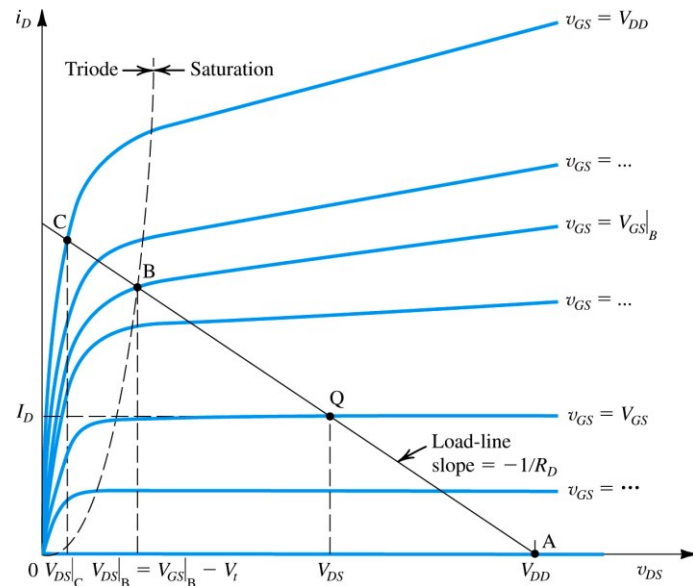
$$\begin{cases} V_{GS} > V_T \\ V_{DS} > V_{GS} - V_T \end{cases}$$



From the equations above we can find the coordinates of the Q point, namely  $I_{DQ}$ ,  $V_{DSQ}$ , and  $V_{GSQ}$



# Total Components Analysis (1)

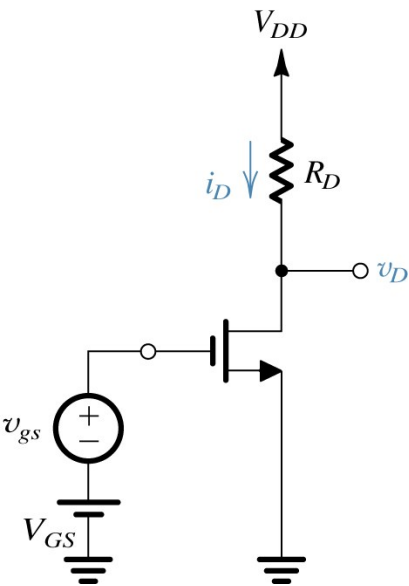

Bias (DC) + signal (AC) analysis

$$v_{GS} = V_{GS} + v_{gs}$$



$$i_D = \frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{GS} + v_{gs} - V_T)^2 =$$

$$= \frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{GS} - V_T)^2 + \quad \leftarrow \text{DC BIAS CURRENT}$$

$$+ \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{GS} - V_T) v_{gs} + \quad \leftarrow \text{CURRENT COMPONENT DIRECTLY PROPORTIONAL TO THE INPUT SIGNAL } v_{gs}$$

$$+ \frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} v_{gs}^2 \quad \leftarrow \text{NON LINEAR DISTORTION}$$

# Distortion in Large Signals

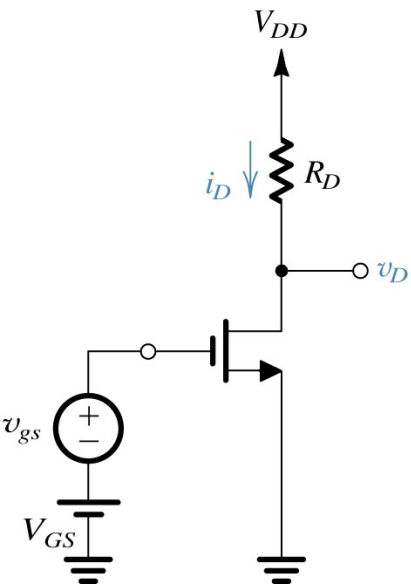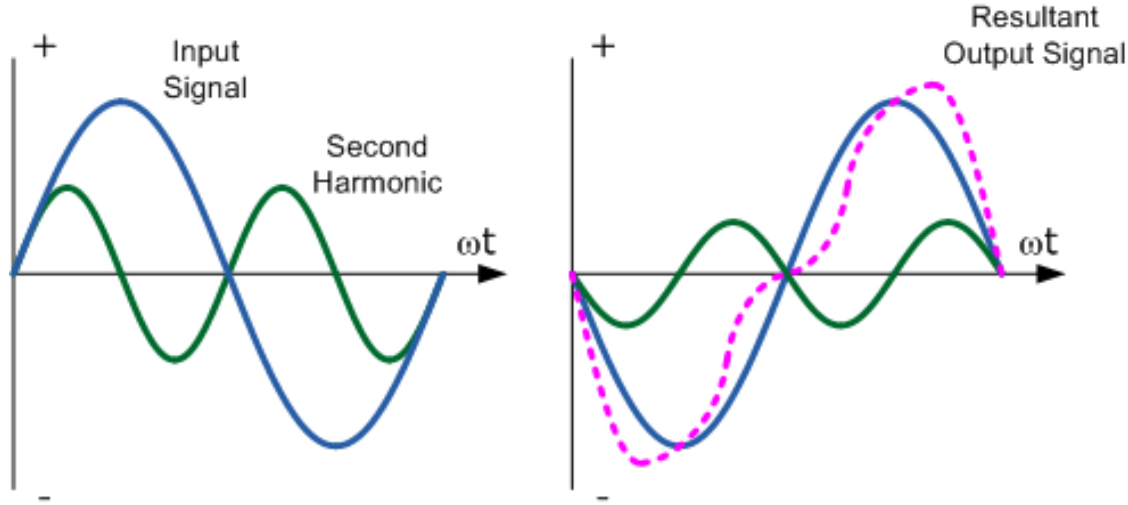

$$v_{GS} = V_{GS} + v_{gs}$$

$$i_D = \frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{GS} + v_{gs} - V_T)^2 =$$

$$= \frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{GS} - V_T)^2 + \quad \leftarrow \text{DC BIAS CURRENT}$$

$$+ \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{GS} - V_T) v_{gs} + \quad \leftarrow \text{CURRENT COMPONENT DIRECTLY PROPORTIONAL TO THE INPUT SIGNAL } v_{gs}$$

$$+ \frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} v_{gs}^2 \quad \leftarrow \text{NON LINEAR DISTORTION}$$

# Small Signal Approximation

If the input signal is kept small so that:

$$\frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} v_{gs}^2 \ll \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{gs} - V_T) v_{gs}$$

$$v_{gs} \ll 2(V_{gs} - V_T)$$

"SMALL  
SIGNAL  
CONDITION"

we can neglect the last term and express:

$$\hat{i}_D \approx I_D + \hat{i}_d$$

$$I_D = \frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{gs} - V_T)^2$$


$$\hat{i}_d = \underbrace{\frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{gs} - V_T)}_{g_m} v_{gs}$$

# Small Signal Analysis


$$g_m = \frac{\hat{i}_d}{\hat{v}_{gs}} = \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{gs} - V_T) \quad g_m = 2\sqrt{K_n I_{DQ}}$$

MOSFET TRANSCONDUCTANCE

$$g_m = \left. \frac{\partial i_D}{\partial V_{gs}} \right|_{V_{gs} = V_{gs}}$$

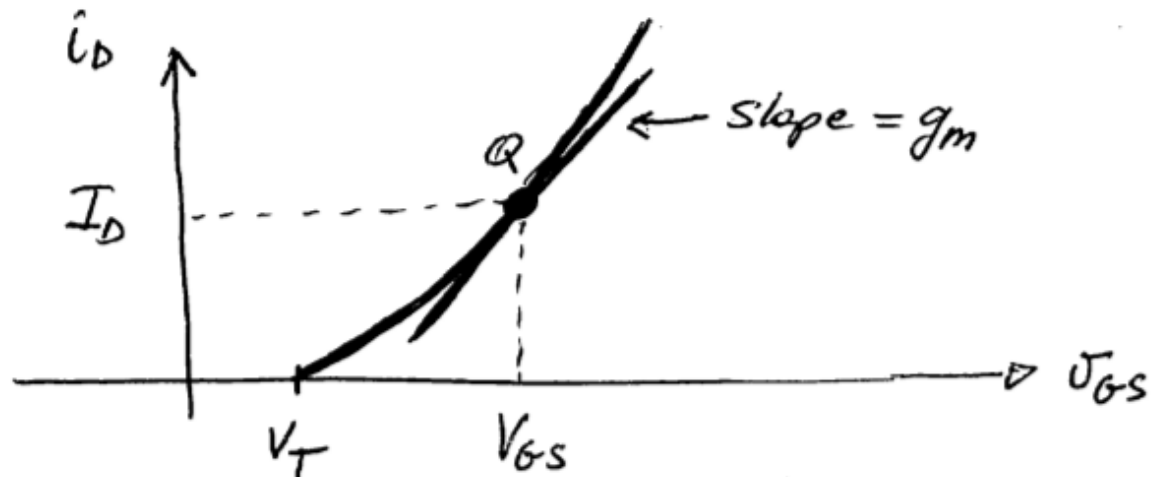

# Small Signal Analysis

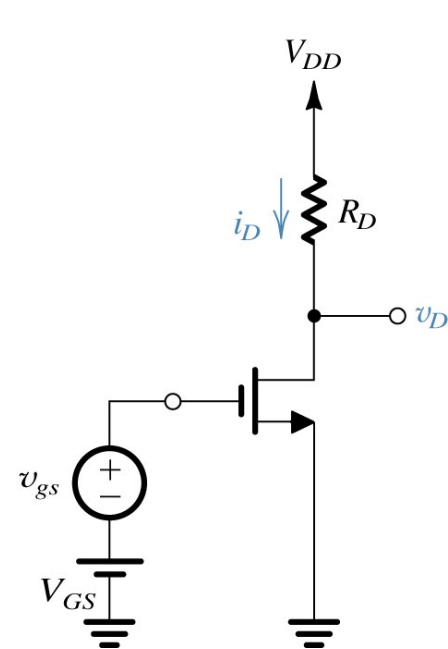

$$v_{DS} = V_{DD} - R_D i_D \rightarrow$$

$$v_{DS} \approx V_{DD} - R_D (I_D + i_d) \rightarrow$$

SMALL SIGNAL  
CONDITION

$$v_{DS} = \underbrace{V_{DD} - R_D \cdot I_D}_{V_{DS}} - R_D \cdot i_d \rightarrow$$


$$\underbrace{v_{DS} - V_{DS}}_{v_{ds}} = - R_D \cdot i_d \rightarrow$$

$$v_{ds} = - R_D \cdot i_d = - R_D \cdot g_m v_{gs}$$


$$\frac{v_{ds}}{v_{gs}} = - g_m R_D$$

← VOLTAGE  
GAIN

# Strategy for Small Signals

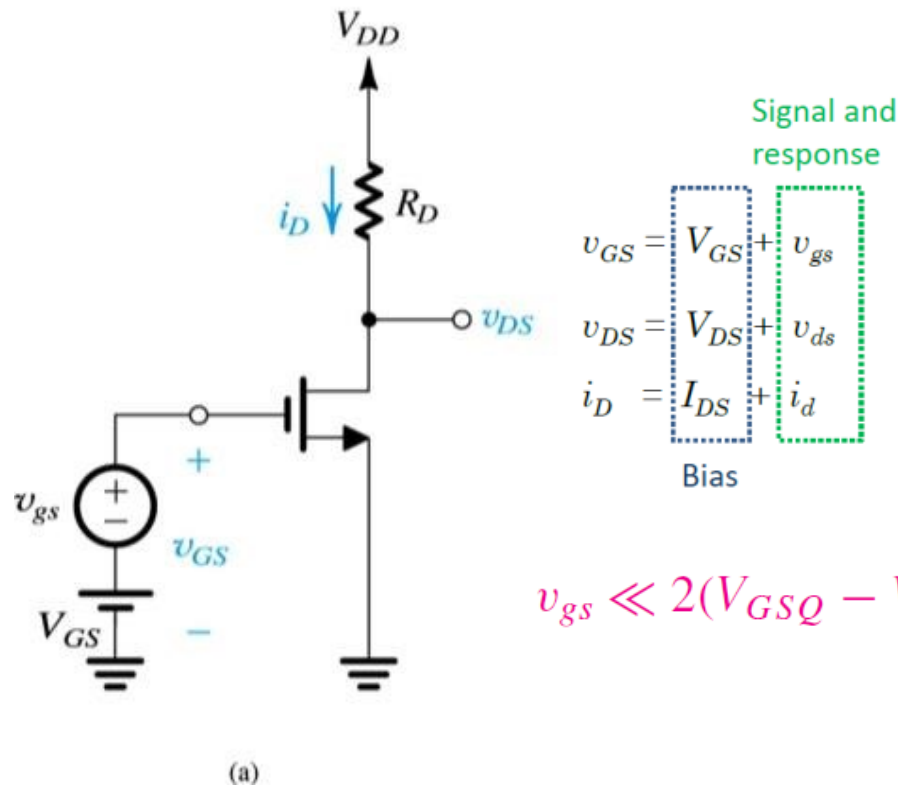


$$v_{gs} \ll 2(V_{GSQ} - V_{TN})$$

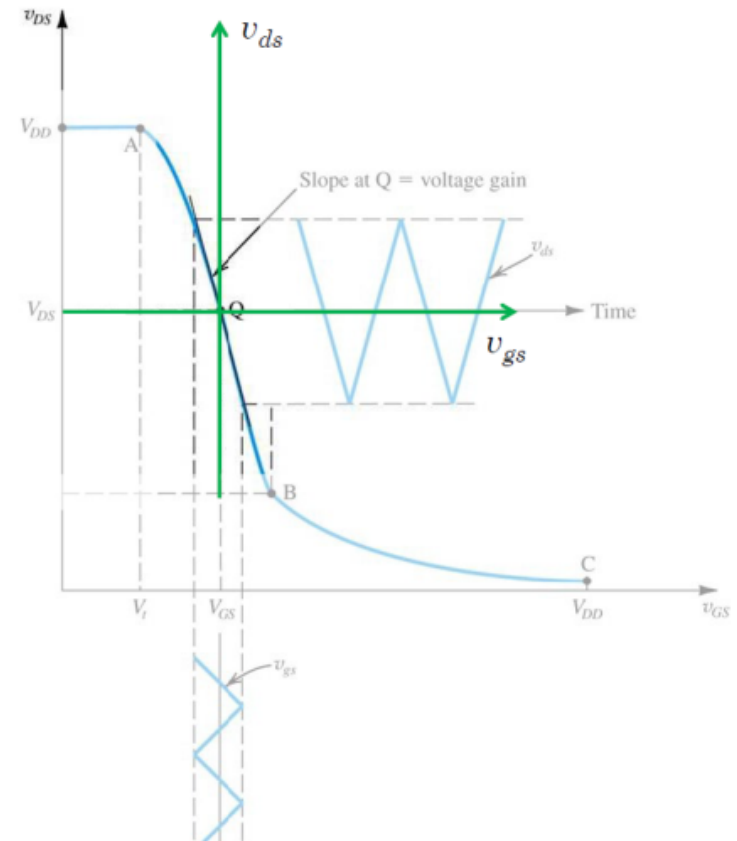

1. Determine the operating point (DC)
2. Determine response to the input (AC)
3. Perform superposition of the AC and DC responses
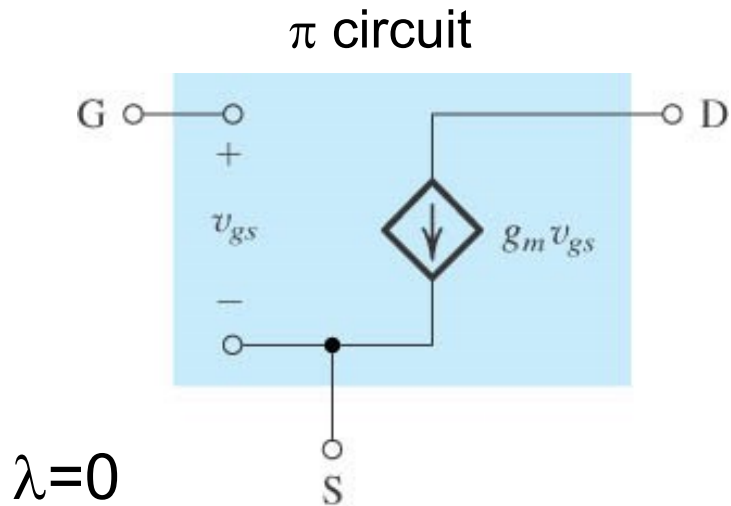
# Small-signal equivalent circuit (NMOS)


The circuit below is valid at low enough frequency for the gate capacitance to act as an open circuit



$$\hat{i}_D \simeq I_D + \hat{i}_d$$

$$I_D = \frac{1}{2} \frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{GS} - V_T)^2$$

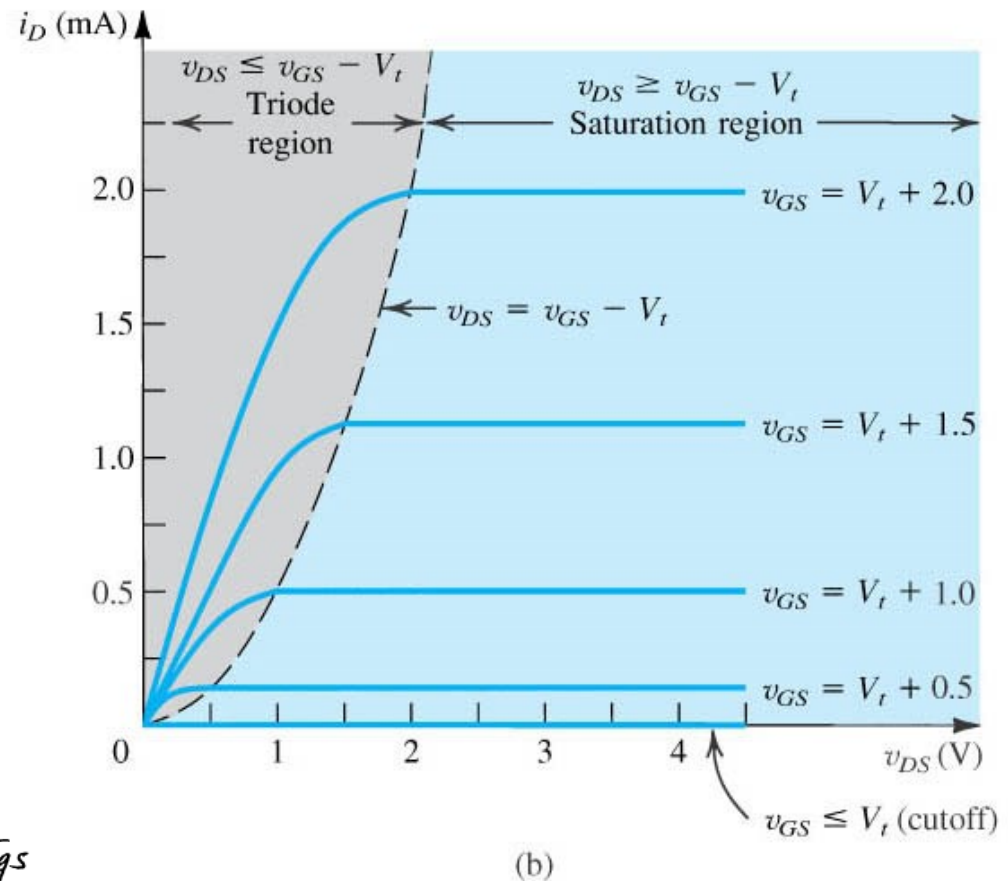
$$\hat{i}_d = \underbrace{\frac{\epsilon_{ox}}{t_{ox}} \mu_n \frac{W}{L} (V_{GS} - V_T)}_{g_m} \hat{v}_{gs}$$



$$v_{gs} \ll 2(V_{GSQ} - V_{TN})$$


# Channel modulation effect in MOSFETs

$\pi$  circuit

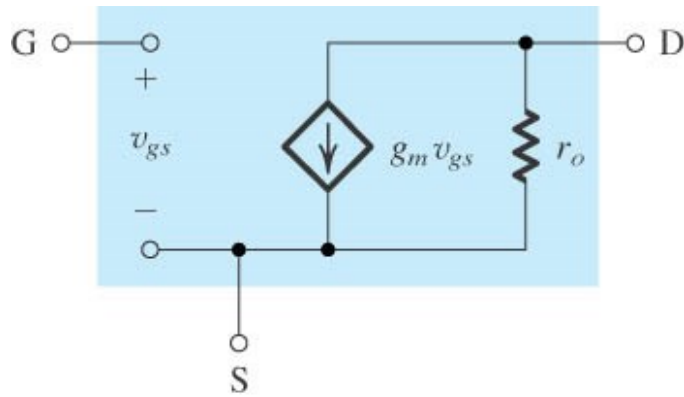

$\lambda \neq 0$

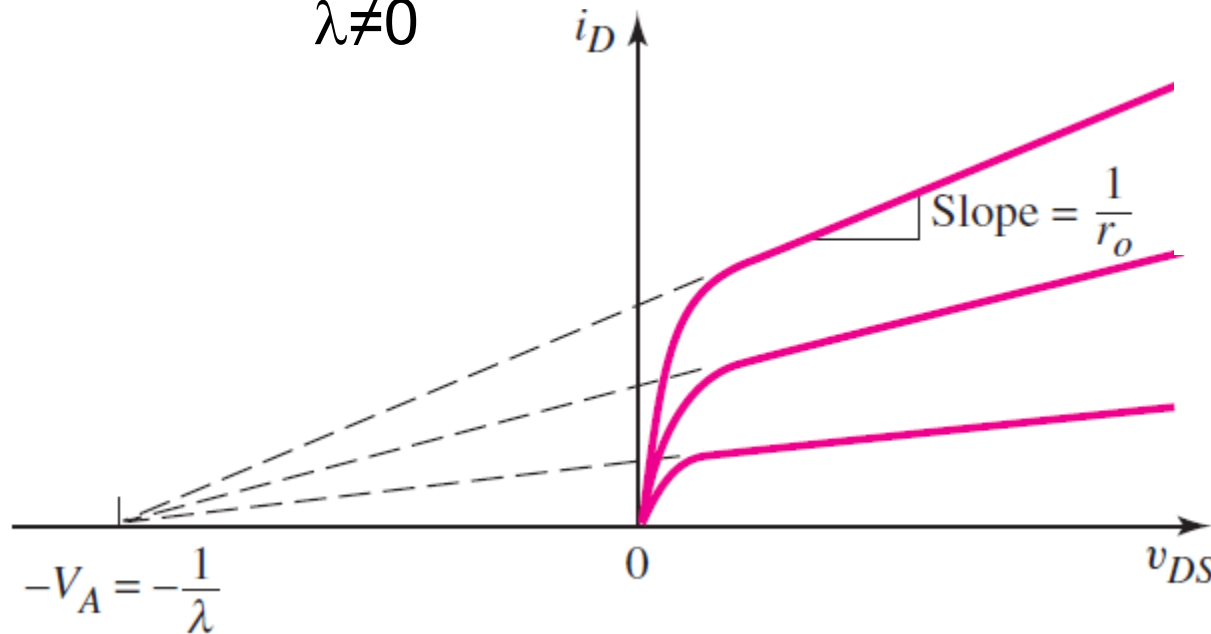This small signal equivalent circuit is valid at low enough frequency for the gate capacitance to act as an open circuit



$$i_D = K_n[(v_{GS} - V_{TN})^2(1 + \lambda v_{DS})]$$

$$r_o = \left( \frac{\partial i_D}{\partial v_{DS}} \right)^{-1} \bigg|_{v_{GS}=\text{const.}}$$


$$r_o = [\lambda K_n (V_{GSQ} - V_{TN})^2]^{-1}$$

$$r_o \cong [\lambda I_{DQ}]^{-1} = \frac{1}{\lambda I_{DQ}} = \frac{V_A}{I_{DQ}}$$


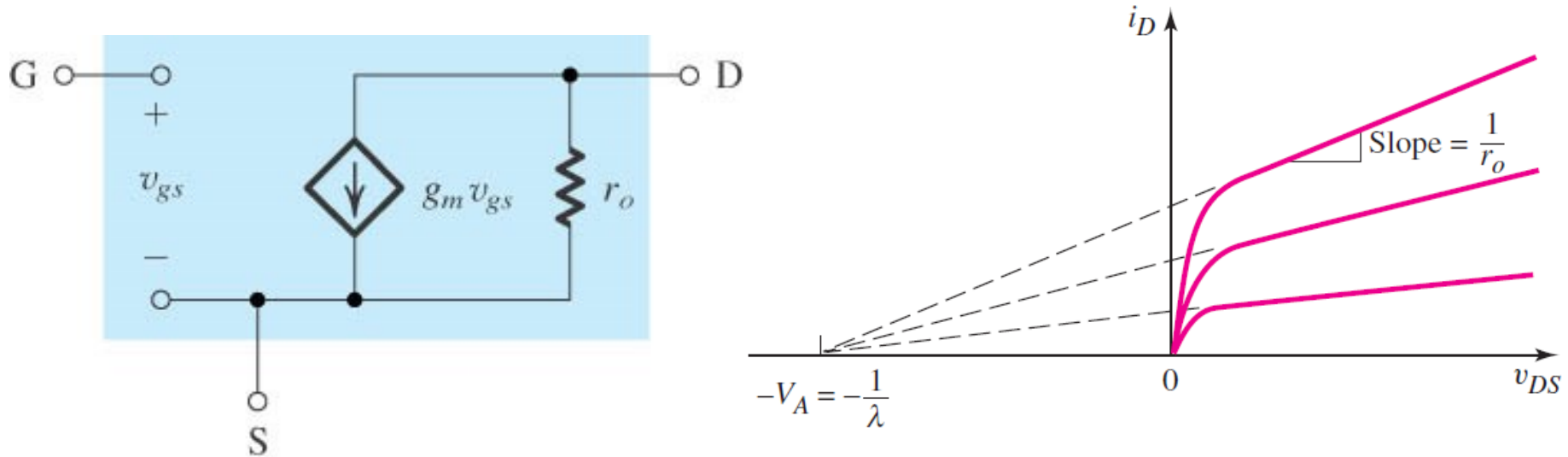
# Small-signal equivalent circuit (NMOS)

This small signal equivalent circuit is valid at low enough frequency for the gate capacitance to act as an open circuit




$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GSQ}=\text{const.}} = 2K_n(V_{GSQ} - V_{TN}) \quad r_o = \left. \left( \frac{\partial i_D}{\partial v_{DS}} \right)^{-1} \right|_{v_{GS}=\text{const.}}$$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong [\lambda I_{DQ}]^{-1} = \frac{1}{\lambda I_{DQ}} = \frac{V_A}{I_{DQ}}$$

# Small-signal equivalent circuit (PMOS)

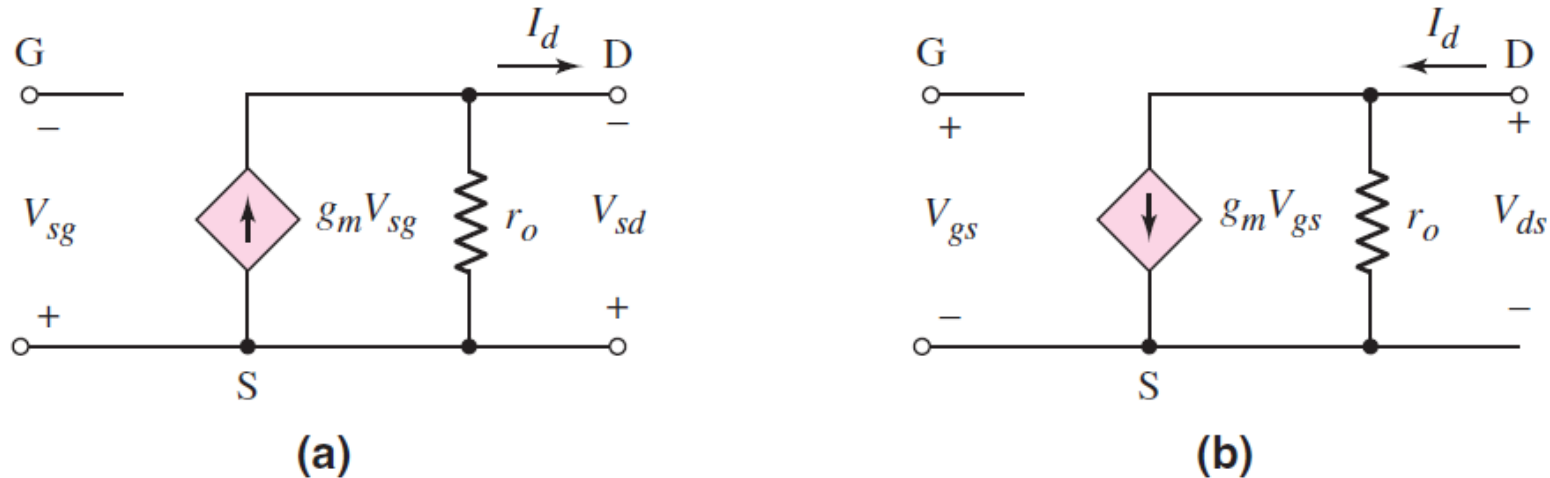

**Figure 4.11** Small signal equivalent circuit of a p-channel MOSFET showing (a) the conventional voltage polarities and current directions and (b) the case when the voltage polarities and current directions are reversed.


# In class problem 1

**TYU 4.3** For the circuit in Figure 4.1, the circuit and transistor parameters are given in Exercise TYU 4.2. If  $v_i = 25 \sin \omega t$  (mV), determine  $i_D$  and  $v_{DS}$ .

$$V_{TN} = 0.4 \text{ V}, K_n = 0.5 \text{ mA/V}^2, \text{ and } \lambda = 0.02 \text{ V}^{-1}$$

$$V_{DD} = 3.3 \text{ V} \text{ and } R_D = 8 \text{ k}\Omega.$$

$$I_{DQ} = 0.15 \text{ mA}$$

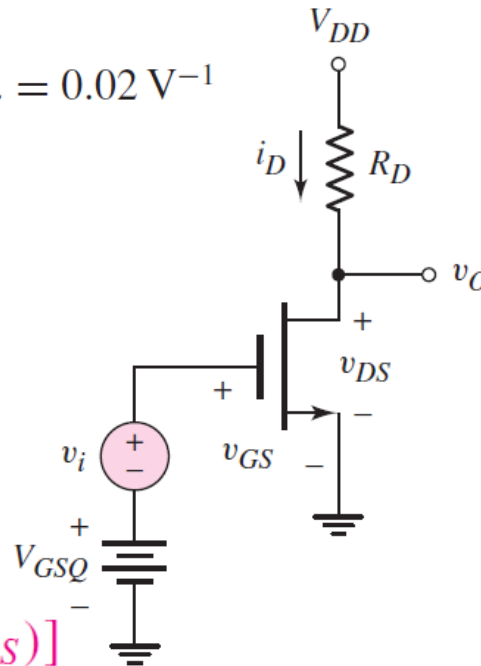

$$i_D = K_n[(v_{GS} - V_{TN})^2(1 + \lambda v_{DS})]$$

$$r_o \cong [\lambda I_{DQ}]^{-1} = \frac{1}{\lambda I_{DQ}} = \frac{V_A}{I_{DQ}}$$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

# Overview of lecture 6

- Amplifiers: Models and Characteristics  
(S&S 1.5.1, 1.5.3, 1.5.5, 5.6.2)
- FET amplifiers configurations: overview  
(Neamen 4.2, S&S 5.6.1)
- Common source (CS) amplifier configurations  
(Neamen 4.3, S&S 5.6.3, 5.6.4)